

The background features several large, stylized, overlapping swirls in light green, light blue, and light purple. Scattered throughout are numerous small, yellow, starburst-like shapes of varying sizes.

Lecture 11


Operational Amplifiers



Topics


- Ideal op Amplifiers
- Ideal OPA circuits analysis
- Non-ideal op amplifiers
- Non-ideal OPA circuit analysis

Ideal operational amplifier

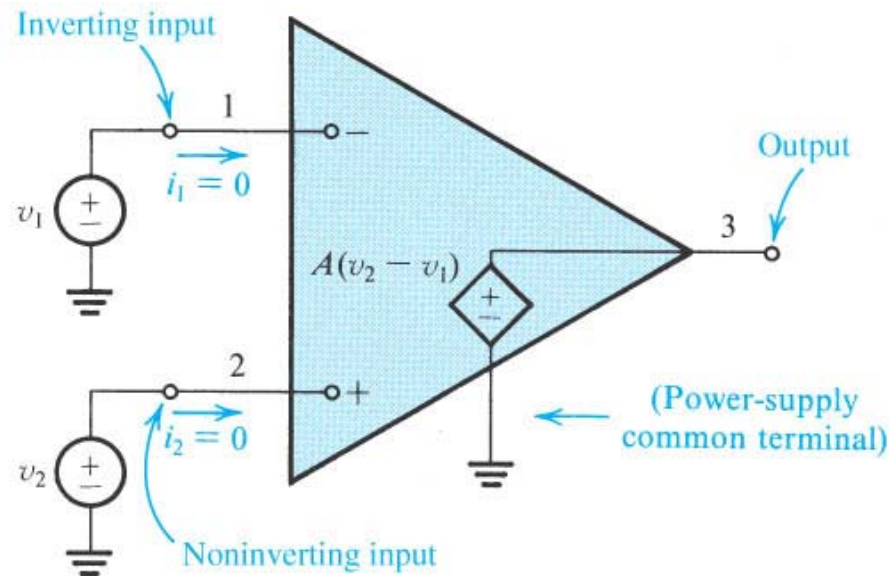


Ideal OPA characters

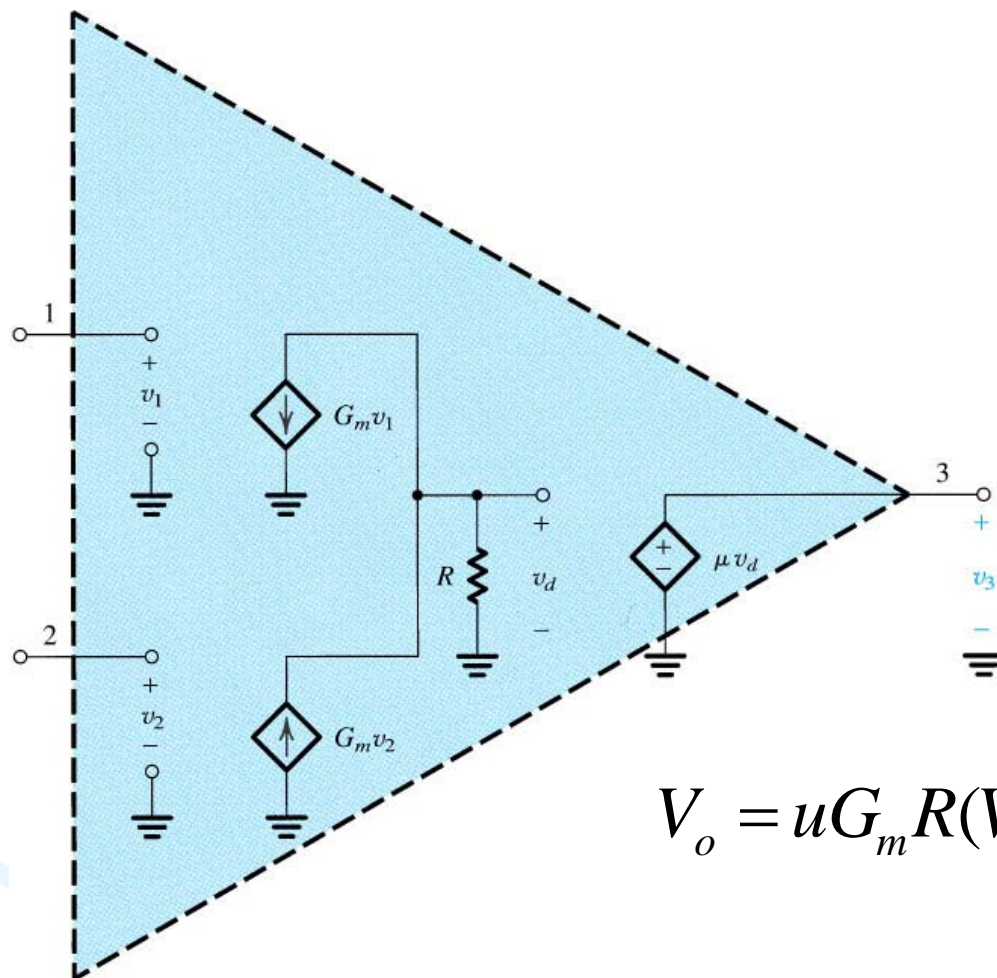
1. Infinite input impedance
2. Zero output impedance
3. Infinite bandwidth
4. Infinite open-loop gain
5. Zero common-mode gain (infinite CMRR)



$$V_o = u G_m R (V_+ - V_-)$$

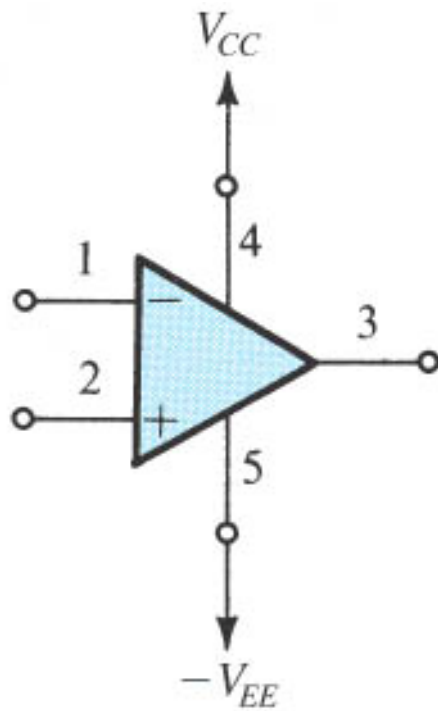


(a)

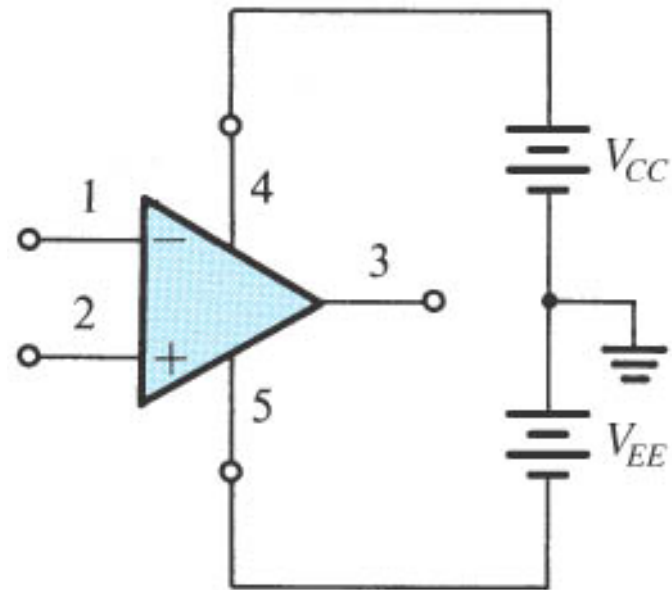

(b)

Negative feedback

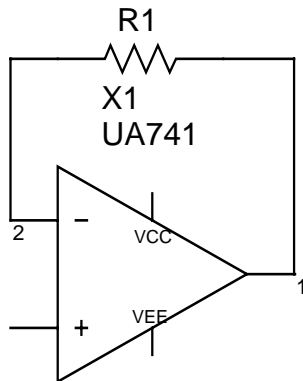


$$V_- = IR + V_o$$

$$V_o = A(V_+ - V_-)$$

$$V_o \uparrow \Rightarrow V_- \uparrow \Rightarrow V_o \downarrow = A(V_+ - V_- \uparrow)$$

$$V_o \downarrow \Rightarrow V_- \downarrow \Rightarrow V_o \uparrow \Rightarrow \text{stable}$$

Positive feedback

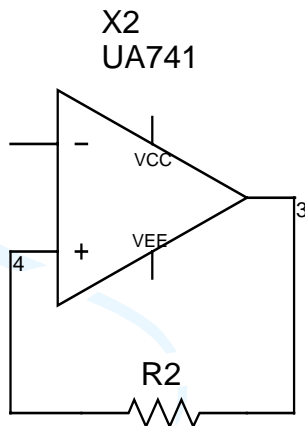

$$V_+ = IR + V_o$$

$$V_o = A(V_+ - V_-)$$

$$V_o \uparrow \Rightarrow V_+ \uparrow \Rightarrow V_o \uparrow \Rightarrow +V_{sat}$$

$$V_o \downarrow \Rightarrow V_+ \downarrow \Rightarrow V_o \downarrow \Rightarrow -V_{sat} \Rightarrow \text{unstable}$$



Ideal OPA characters

$$R_{in} \rightarrow \infty \Rightarrow (i_+ = i_- = 0)$$

$$R_o \rightarrow 0$$

$$A \rightarrow \infty \Rightarrow (V_+ = V_-)$$

$$BW \rightarrow \infty$$

$$CMRR \rightarrow \infty$$

Non-ideal cases

$$R_{in} \neq \infty$$


$$R_o \neq 0$$

$$A \neq \infty$$

$$BW \neq \infty$$

$$CMRR \neq \infty$$

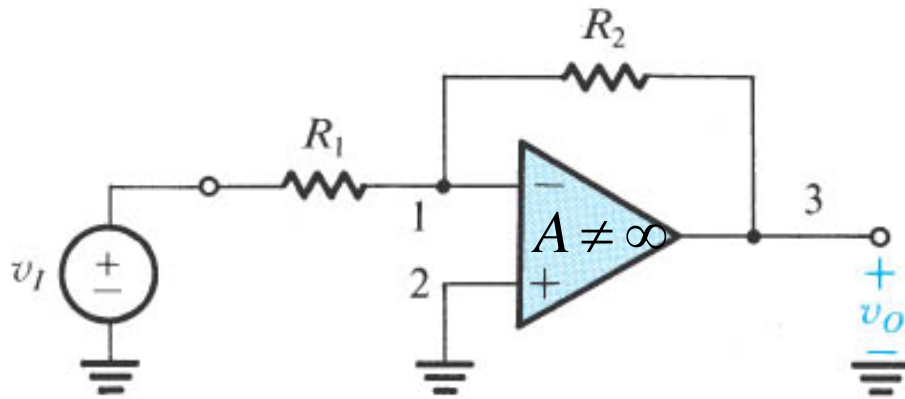Consider finite open-loop gain $A \neq \infty$



$$\because A \neq \infty$$

$$\therefore v_1 \neq v_2$$

$$\Rightarrow \frac{v_- - v_i}{R_1} + \frac{v_- - v_o}{R_2} = 0 \dots (1)$$

$$v_o = A(v_+ - v_-) = -Av_- \dots (2)$$


$$\frac{v_o}{v_i} = \frac{-R_2 / R_1}{1 + (1 + R_2 / R_1) / A}$$

$$\text{if } A \rightarrow \infty$$

$$\frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

Input and output resistance

Example 2.1

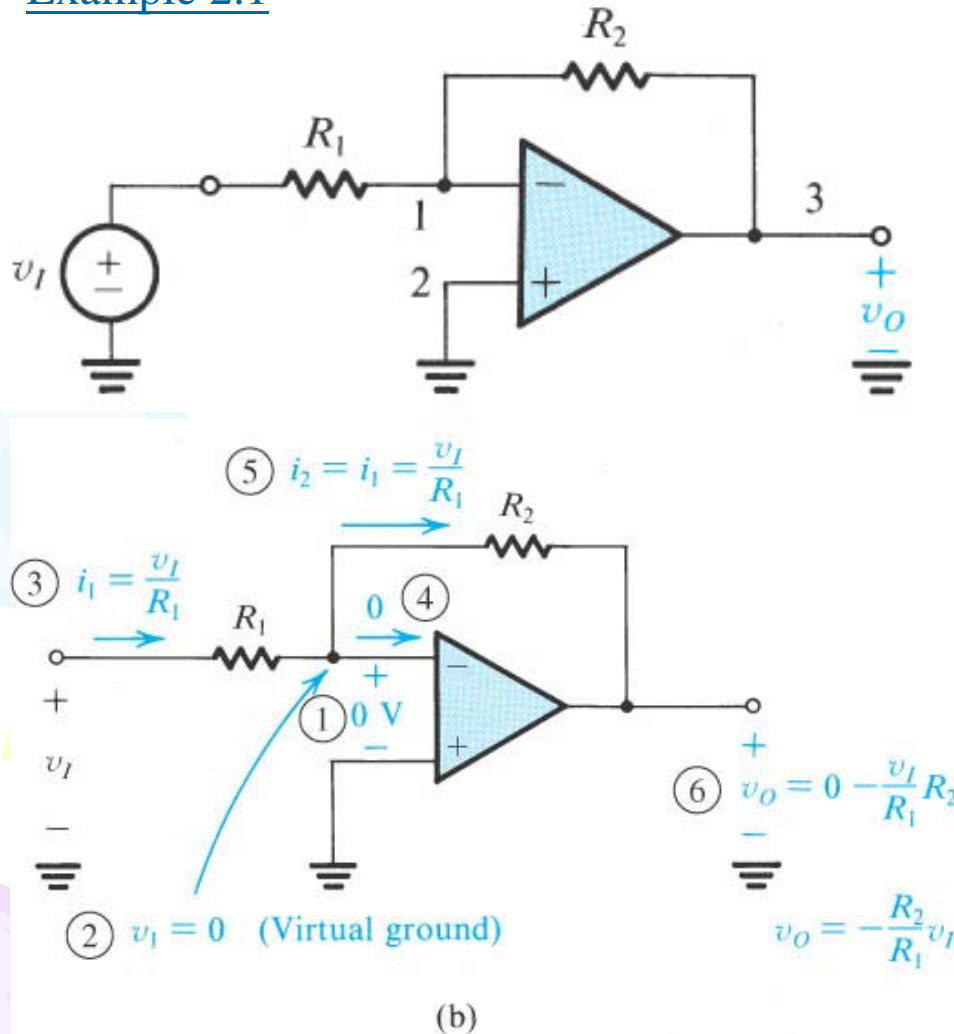

$$R_{in} = \frac{v_i}{i_i} = R_1$$

$$G_{ain} \equiv \frac{v_O}{v_I}$$

$$\frac{0 - v_I}{R_1} + \frac{0 - v_O}{R_2} = 0$$

$$\Rightarrow G_{ain} = \frac{v_O}{v_I} = -\frac{R_2}{R_1}$$



$$\text{if } R_1 = 1M$$

$$R_2 = 100M$$


An impractically large value

So we may have the problem of input resistance.


Output resistance

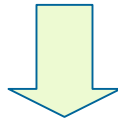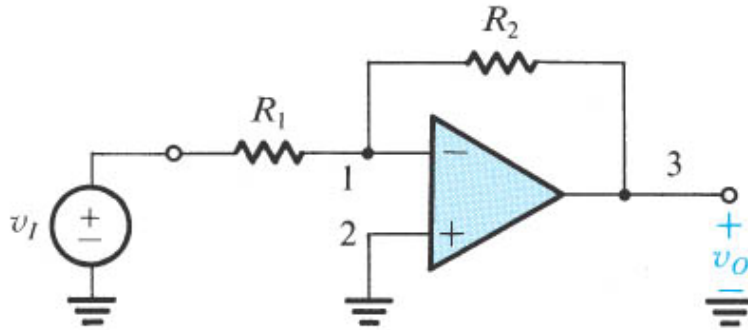

$$R_{out} = \frac{V}{I} = 0$$

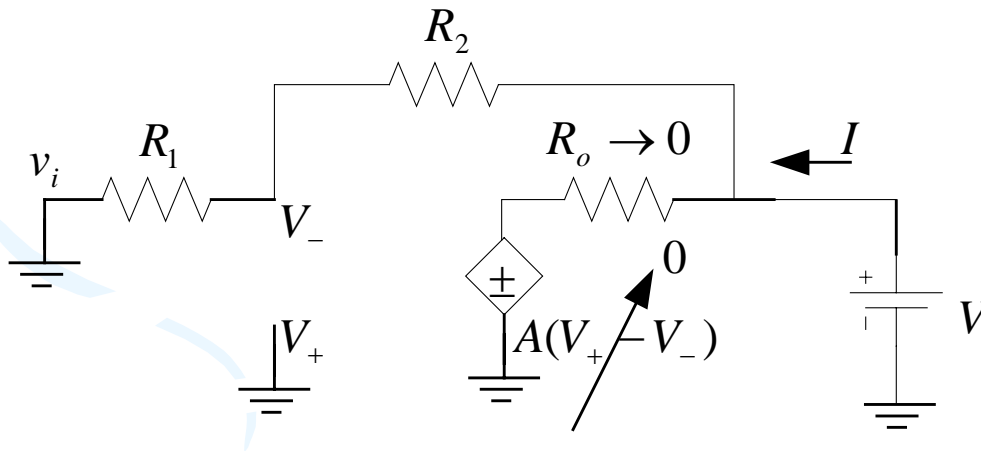

Example 2.2

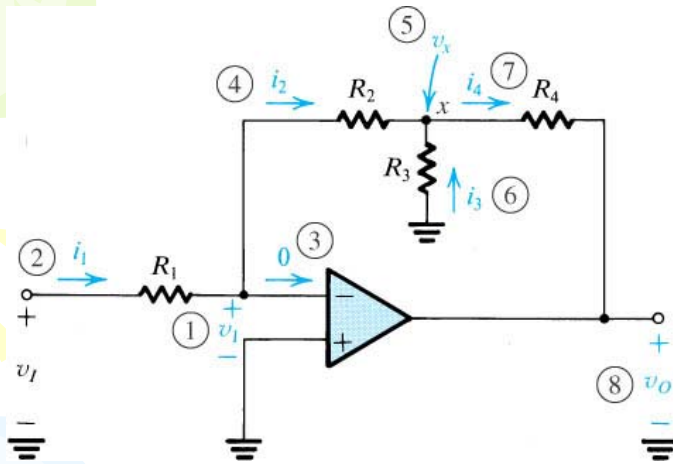

$$\frac{v_X - 0}{R_2} + \frac{v_X}{R_3} + \frac{v_X - v_o}{R_4} = 0 \dots (1)$$

$$\frac{0 - v_I}{R_1} + \frac{0 - v_X}{R_2} = 0 \dots (2)$$

$$\frac{v_o}{v_i} = -\frac{R_2}{R_1} \left(1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right)$$

Comparing with Example 2.1

Design an amplifier with a gain -100 and an input resistance of $1M$.

Example 2.1:

$$R_1 = 1M$$

$$R_2 = 100M$$


Example 2.2:

$$\frac{v_o}{v_i} = -\frac{R_2}{R_1} \left(1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right)$$

$$R_1 = 1M, R_2 = 1M$$

$$R_3 = 10.2k, R_4 = 1M$$

Exercise 2.6

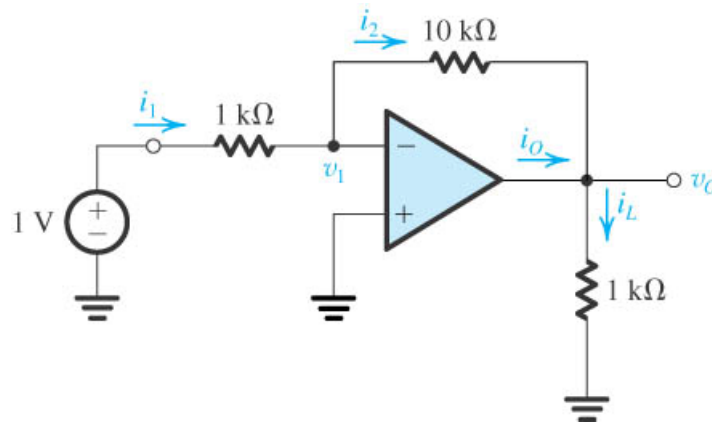

$$\frac{v_- - 1}{1k} + \frac{v_- - v_o}{10k} = 0 \dots (1)$$

$$v_- = 0 \dots (2)$$

$$\frac{-1}{1k} + \frac{-v_o}{10k} = 0 \Rightarrow v_o = \frac{-10k}{1k} = -10V$$

Find


$$i_L = \frac{-10}{1k} = -10mA$$

$$i_2 = \frac{0 - (-10)}{10k} = 1mA$$

$$i_O = -11mA$$

$$i_1 = i_2 = 1mA$$

Weighted summer

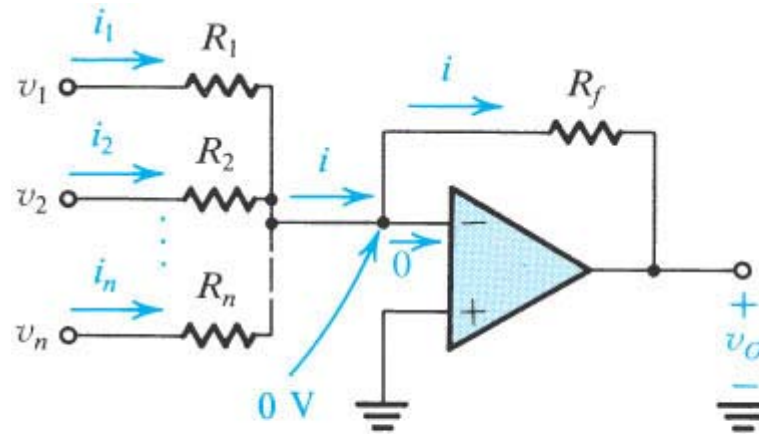


$$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n \right)$$

$$\frac{0 - v_1}{R_1} + \frac{0 - v_2}{R_2} + \dots + \frac{0 - v_n}{R_n} + \frac{0 - v_o}{R_f} = 0 \dots (1)$$

$$\Rightarrow \frac{-v_1}{R_1} + \frac{-v_2}{R_2} + \dots + \frac{-v_n}{R_n} = \frac{v_o}{R_f}$$

$$\Rightarrow v_o = \frac{-R_f}{R_1} v_1 + \frac{-R_f}{R_2} v_2 + \dots + \frac{-R_f}{R_n} v_n$$

Exercise D2.8

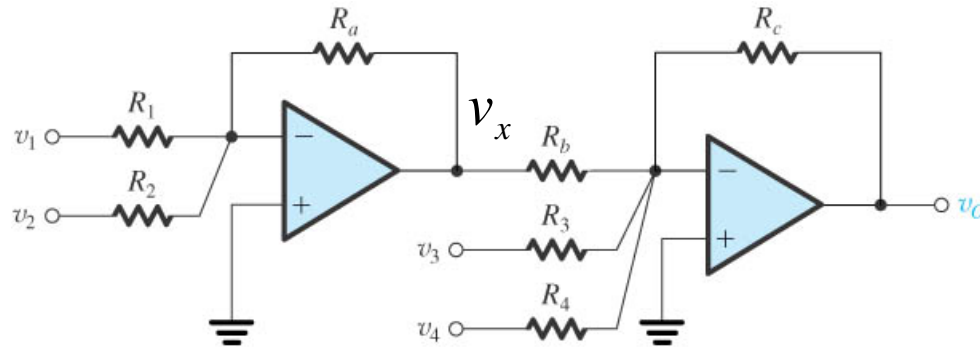


$$v_x = -\left(\frac{R_a}{R_1} v_1 + \frac{R_a}{R_2} v_2\right)$$

$$v_o = -\left(\frac{R_c}{R_3} v_3 + \frac{R_c}{R_4} v_4 + \frac{R_c}{R_b} v_x\right)$$

$$v_o = -\left(\frac{R_c}{R_3} v_3 + \frac{R_c}{R_4} v_4\right) + \frac{R_c}{R_b} \left(\frac{R_a}{R_1} v_1 + \frac{R_a}{R_2} v_2\right)$$

Non-inverting amplifier

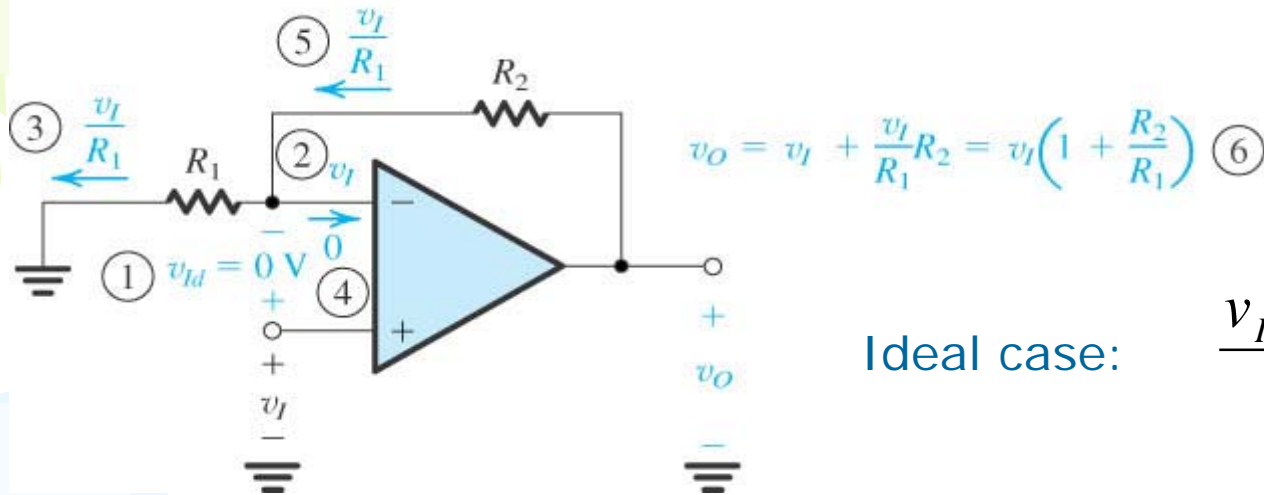

Ideal case:

$$\frac{v_I - 0}{R_1} + \frac{v_I - v_o}{R_2} = 0$$

$$\Rightarrow v_o = \left(1 + \frac{R_2}{R_1}\right)v_I$$

Non-ideal case: $A \neq \infty$



$$\frac{v_i - 0}{R_1} + \frac{v_i - v_o}{R_2} = 0 \dots (1)$$

$$v_o = A(v_i - v_-) \dots \dots \dots (2)$$


$$(1) \rightarrow v_- = \frac{v_o}{R_2} \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$\frac{v_o}{v_i} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{R_2}{R_1} \frac{1}{A}}$$

Voltage follower

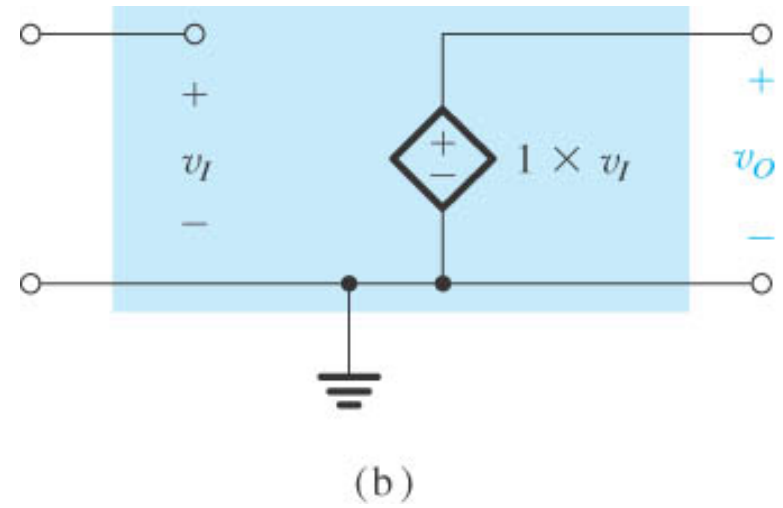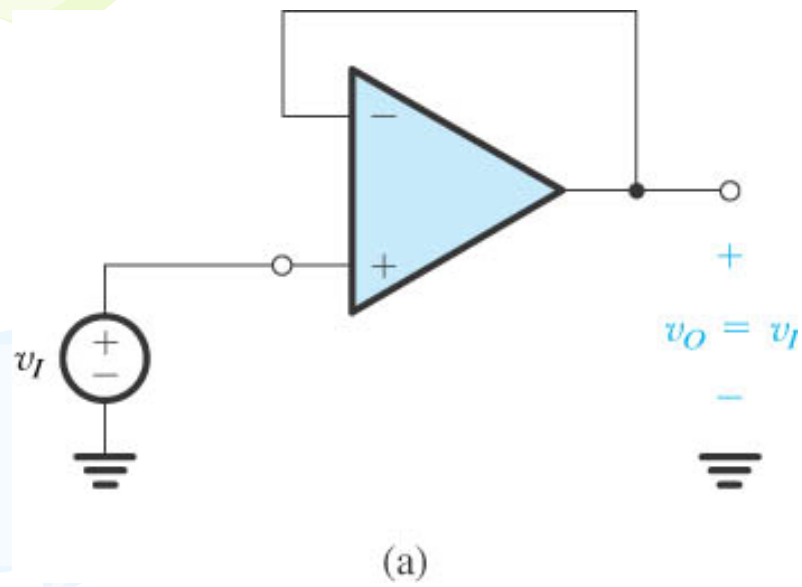

Exercise D2.9

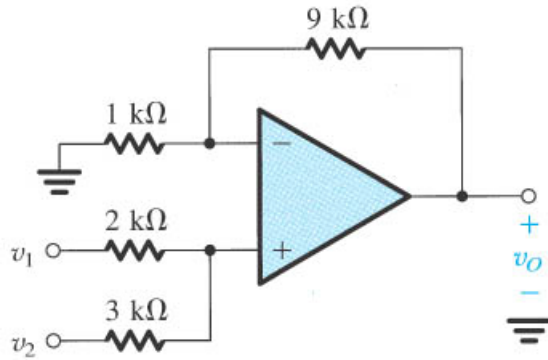

$$v_- = v_+$$

$$\frac{v_- - 0}{1k} + \frac{v_- - v_o}{9k} = 0 \dots (1)$$


$$\frac{v_- - v_1}{2k} + \frac{v_- - v_2}{3k} = 0 \dots (2)$$

$$(2) \Rightarrow v_- \left(\frac{1}{2k} + \frac{1}{3k} \right) = \left(\frac{v_1}{2k} + \frac{v_2}{3k} \right)$$

$$(1) \Rightarrow v_o = 9k \left(\frac{1}{1k} + \frac{1}{9k} \right) v_-$$

$$= 9k \left(\frac{1}{1k} + \frac{1}{9k} \right) \left(\frac{2k + 3k}{2k \times 3k} \right) \left(\frac{v_1}{2k} + \frac{v_2}{3k} \right)$$

Exercise D2.13

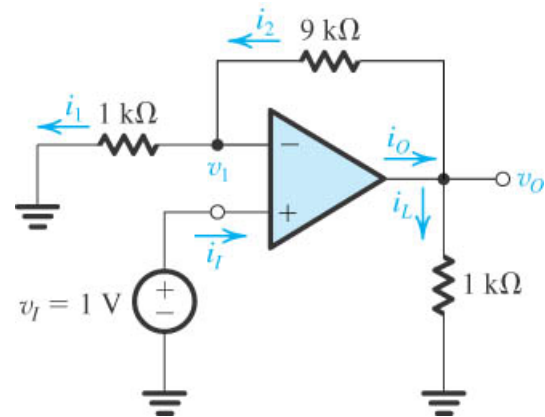

$$v_- = v_+ = 1V$$

$$\frac{1-0}{1k} + \frac{1-v_o}{9k} = 0 \dots (1)$$

$$\Rightarrow v_o = \left(\frac{1}{1k} + \frac{1}{9k} \right) 9k = 10V$$

Why use difference amplifier ?


CMRR (Common-Mode Rejection ratio)

$$CMRR \equiv 20 \log \frac{|A_d|}{|A_{cm}|}$$

$$v_o = A_d v_{id} + A_{cm} v_{icm}$$

Different-mode input

Common-mode input

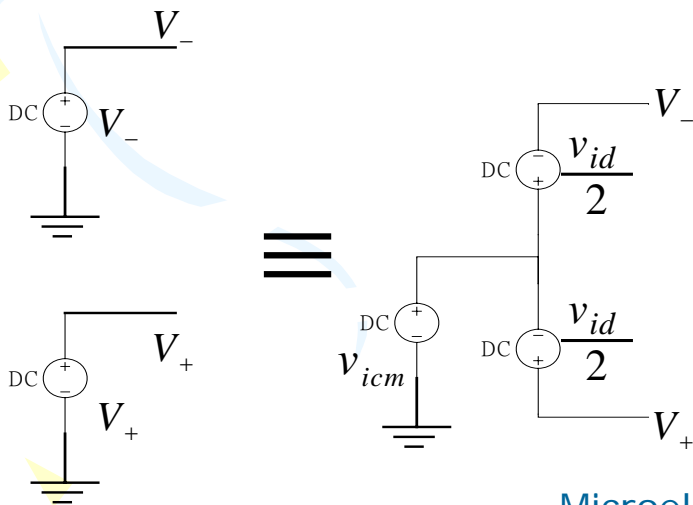


$$v_{id} \equiv v_+ - v_-$$

$$v_{icm} \equiv \frac{1}{2} (v_+ + v_-)$$

Difference Amplifier

Method I:

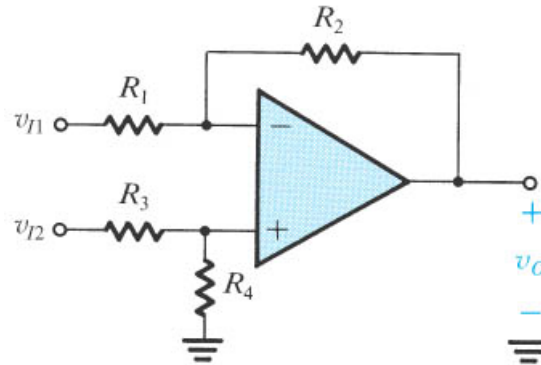

$$v_- = v_+$$

$$\frac{v_- - v_{i1}}{R_1} + \frac{v_- - v_o}{R_2} = 0 \dots (1)$$


$$\frac{v_+ - v_{i2}}{R_3} + \frac{v_+}{R_4} = 0 \dots (2)$$

$$(1) \Rightarrow v_o = R_2 \left(\frac{v_+ - v_{i1}}{R_1} + \frac{v_+}{R_2} \right) = R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) v_+ - \frac{R_2}{R_1} v_{i1}$$

$$(2) \Rightarrow v_+ \left(\frac{1}{R_3} + \frac{1}{R_4} \right) = \frac{1}{R_3} v_{i2}$$


Different-mode input

Method I: superposition

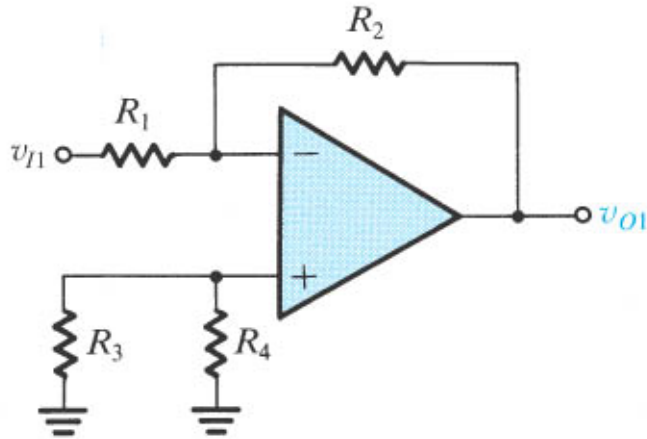

(a)

$$v_{o1} = -\frac{R_2}{R_1} v_{i1}$$

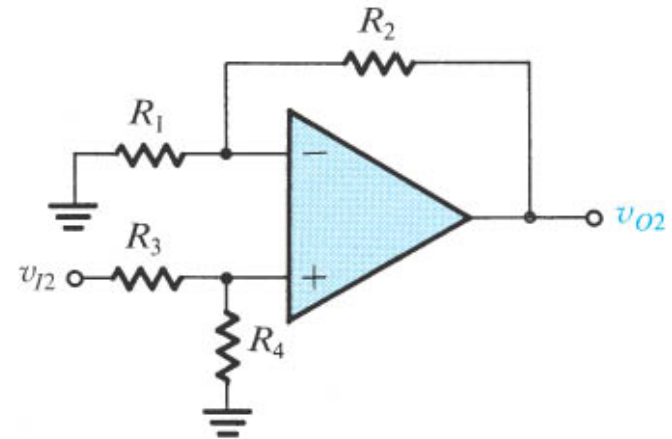


(b)

$$v_{o2} = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) v_{i2} = \frac{R_2}{R_1} v_{i2} \quad (\text{let } R_3 = R_1, R_4 = R_2)$$

$$v_o = v_{o1} + v_{o2} = \frac{R_2}{R_1} (v_{i2} - v_{i1}) = A_d (v_{i2} - v_{i1})$$

Common-mode input

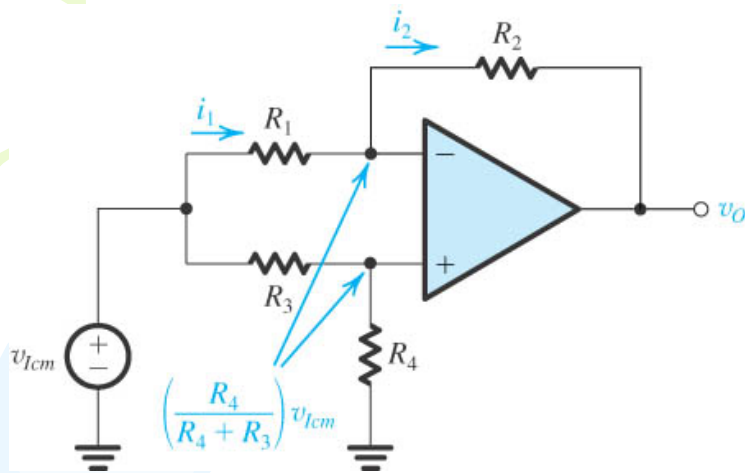

$$i_1 = \frac{1}{R_1} \left[v_{icm} - \frac{R_4}{R_3 + R_4} v_{icm} \right] = \frac{R_3}{R_3 + R_4} \frac{1}{R_1} v_{icm}$$

$$v_o = \frac{R_4}{R_3 + R_4} v_{icm} - i_2 R_2$$

$$\because i_1 = i_2 \Rightarrow v_o = \left[\frac{R_4}{R_3 + R_4} - \frac{R_3}{R_3 + R_4} \frac{R_2}{R_1} \right] v_{icm}$$

$$A_{cm} = \frac{R_4}{R_3 + R_4} \left[1 - \frac{R_3}{R_4} \frac{R_2}{R_1} \right]$$


$$\because R_3 = R_1, R_4 = R_2 \Rightarrow \therefore A_{cm} = 0$$

CMRR=infinite

$$\text{if } R_3 \neq R_1, R_4 \neq R_2 \Rightarrow A_{cm} \neq 0$$

CMRR \neq infinite

Consider the problem of input resistance

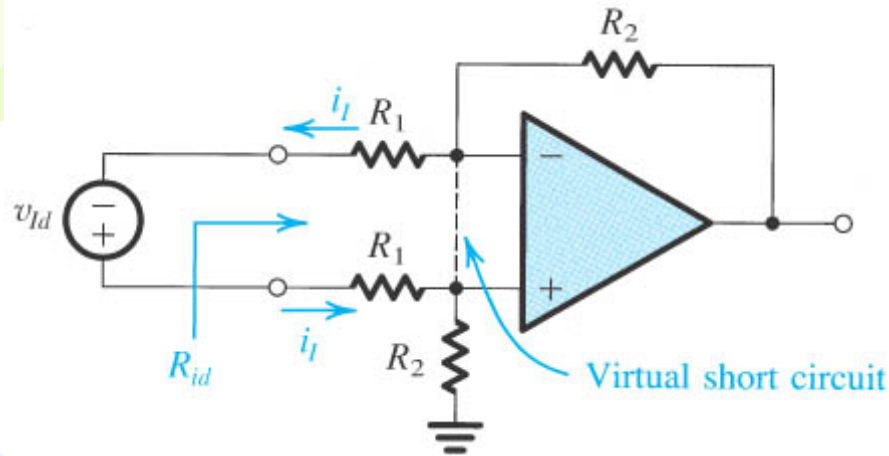

$$v_{id} = i_1 R_1 + i_1 R_1 = 2R_1 i_1$$


$$\Rightarrow R_{in(diff)} = 2R_1$$

Differential mode input resistance

$$v_o = \frac{R_2}{R_1} v_{id}$$

$$if \quad R_{in} \uparrow \rightarrow R_1 \uparrow \rightarrow v_o \downarrow$$

Instrumentation Amplifier

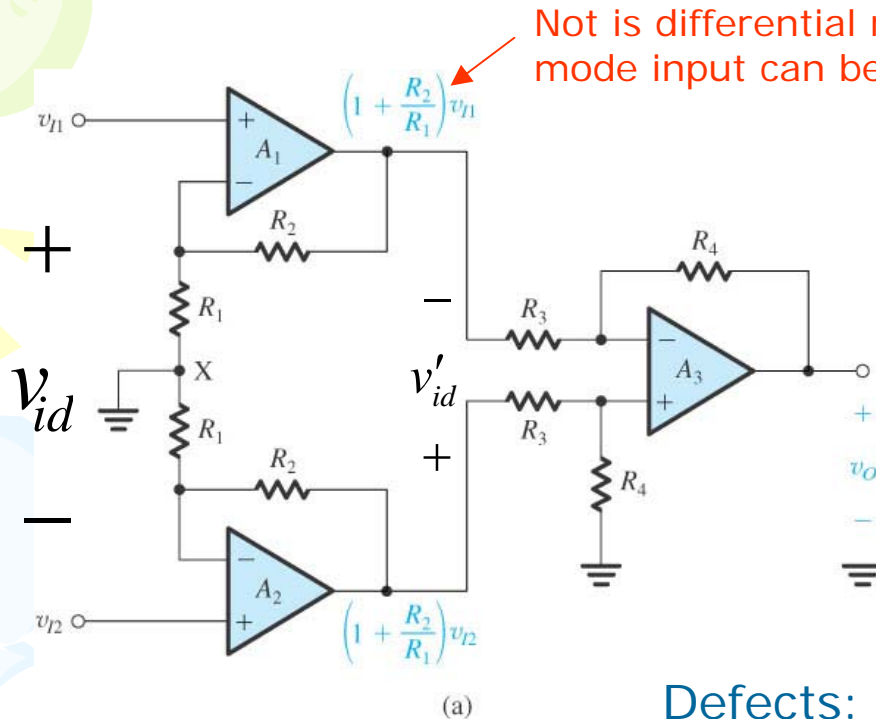

$$v_o = \frac{R_4}{R_3} v'_{id}$$

$$v'_{id} = \left(1 + \frac{R_2}{R_1}\right) (v_{i2} - v_{i1})$$

$$v_o = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) (v_{i2} - v_{i1})$$

Advantages:

1. $R_{in} \rightarrow \infty$
2. $A_d = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right)$


Big differential gain

Defects:

1. Common mode gain=differential mode gain. $v_o \rightarrow v_{sat}$
2. Resistance R_1 and R_2 have to match.

$$v'_{id} = \left(1 + \frac{R_2}{R_1}\right) (v_{i2} - v_{i1})$$

Remove the point x

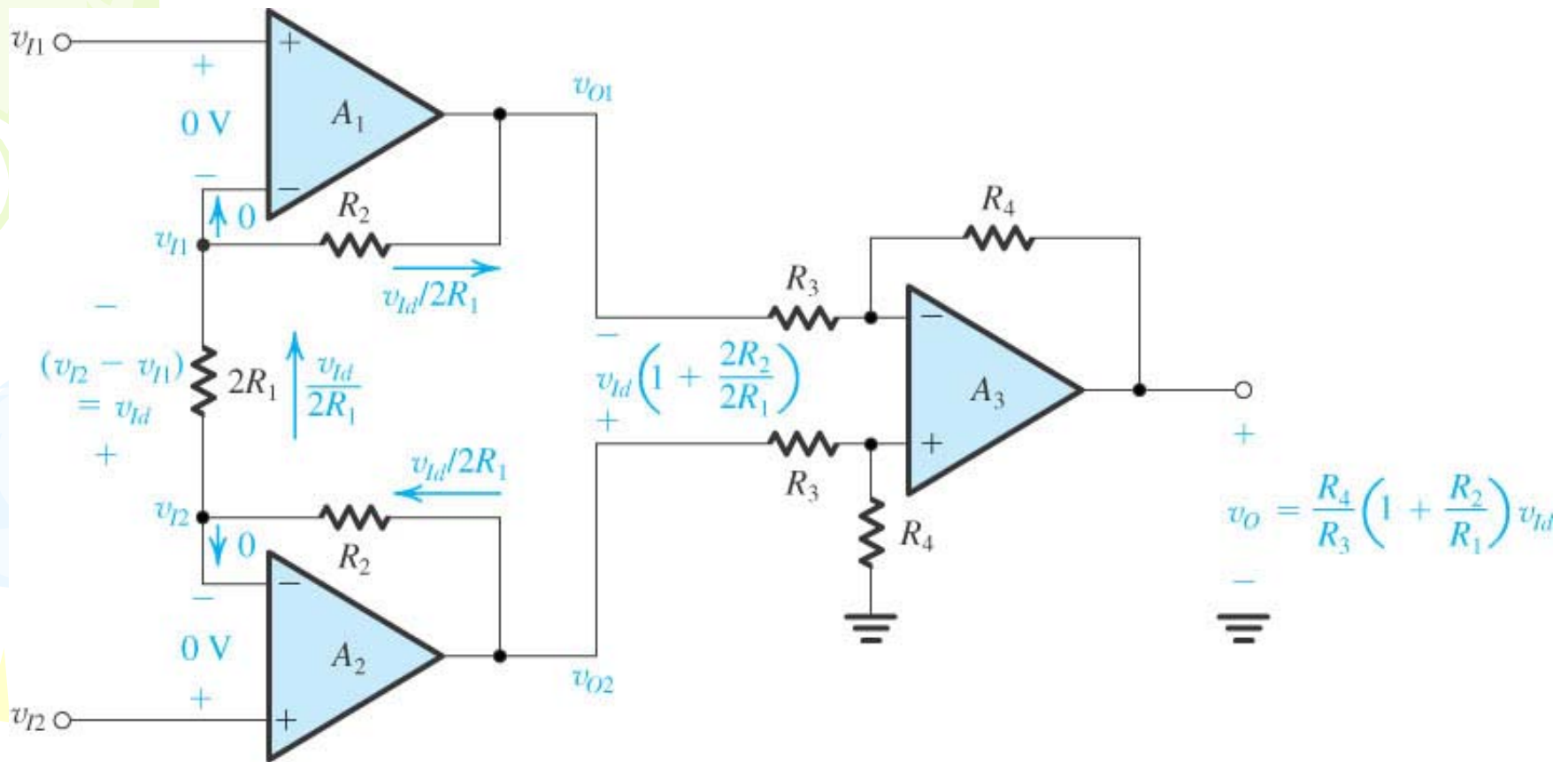


(c)



DC non-ideal characters

1. Finite open loop gain (finite CMRR)
2. Finite BW
3. Offset voltage
4. Input bias and offset current



Frequency response (open-loop)

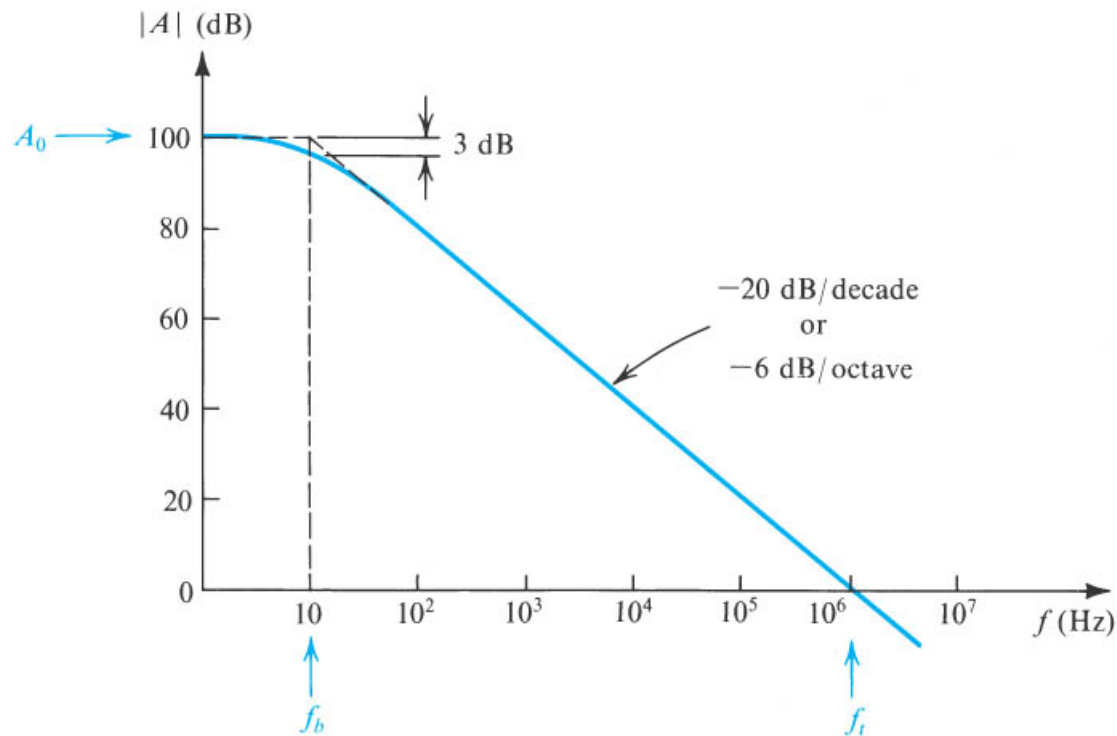

$$A(s) = \frac{A_o}{1 + s/\omega_b} \Rightarrow 0dB : \frac{\omega_t}{\omega_b} = A_o$$

$$\omega_t = A_o \omega_b$$

Frequency response (closed loop)

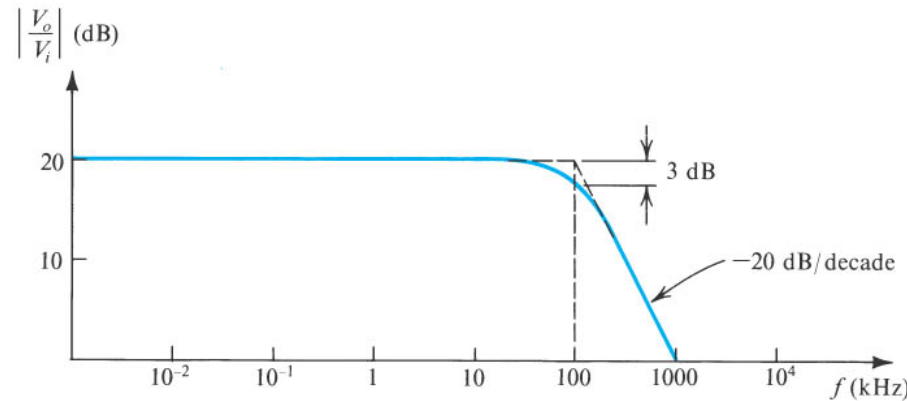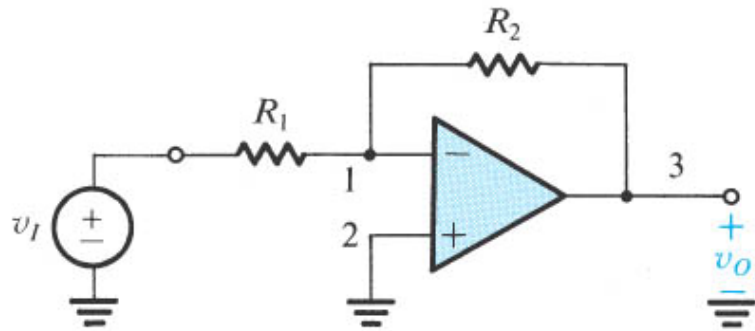


$$\frac{v_o}{v_i} = \frac{-R_2/R_1}{1 + (1 + R_2/R_1)/A}$$

$$A(s) = \frac{A_o}{1 + s/\omega_b}$$


$$\frac{v_o}{v_i} = \frac{-R_2/R_1}{1 + \frac{1}{A_o}(1 + R_2/R_1) + \frac{s}{\omega_t/(1 + R_2/R_1)}} \approx \frac{-R_2/R_1}{1 + \frac{s}{\omega_t/(1 + R_2/R_1)}}$$

$$\omega_{3dB} = \frac{\omega_t}{1 + R_2/R_1}$$

Output voltage saturation

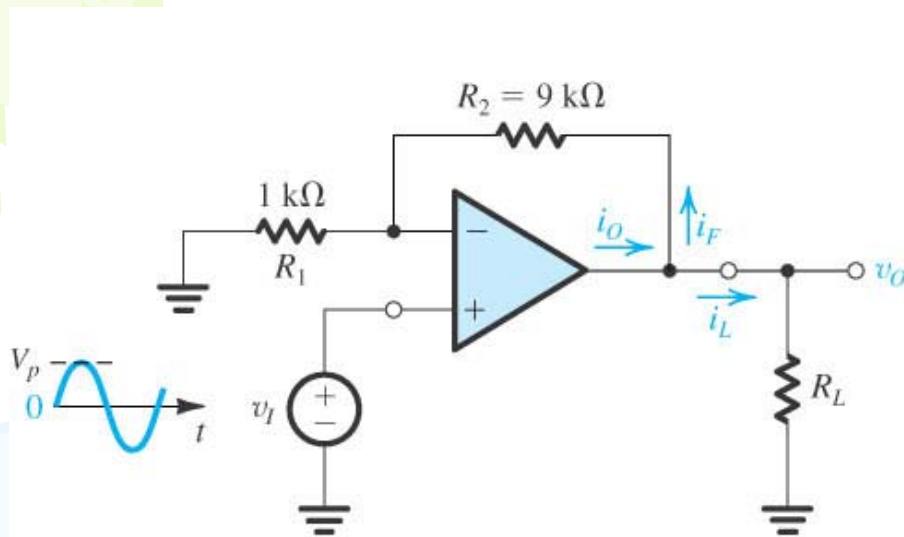

(a)

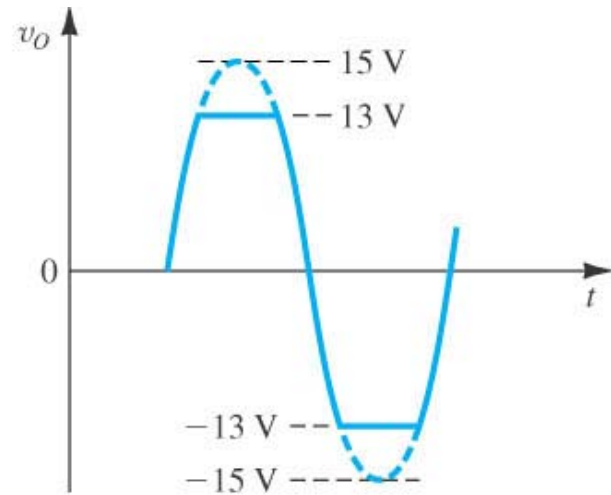


(b)


$$v_{o\max} = \pm 13\text{ V}$$
$$i_{o\max} = \pm 20\text{ mA}$$

Slew rate

$$SR \equiv \left. \frac{dv_o}{dt} \right|_{\max} (V / \mu s)$$

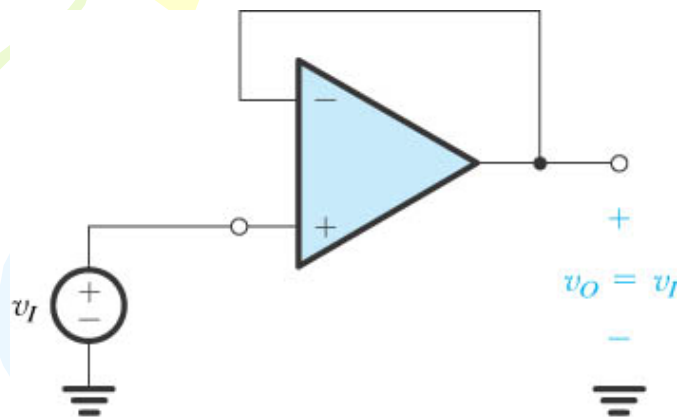

(a)

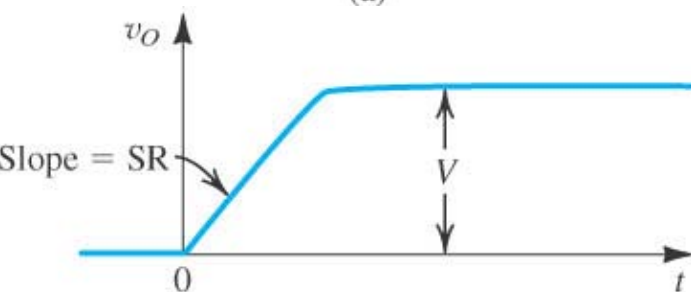

(c)



(b)


$$\frac{v_o}{v_i} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{R_2}{A R_1}}$$

$$A = \frac{A_o}{1 + s / \omega_b}$$

$$\frac{v_o}{v_i} \approx \frac{1}{1 + \frac{s}{\omega_t}} (\because R_2 = 0, R_1 = \infty)$$

let $v_i = V(\text{unit step})$
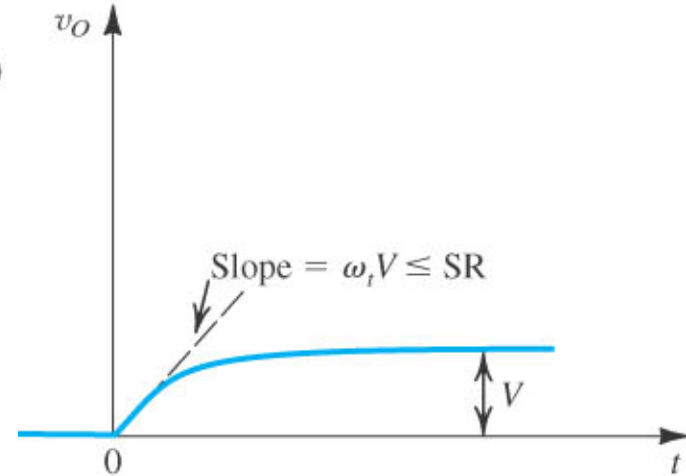
$$V_o(s) = \frac{\omega_t}{\omega_t + s} \frac{V}{s} = \frac{-V}{s + \omega_t} + \frac{V}{s} \Rightarrow v_o(t) = V(1 - e^{-\omega_t t})$$




(d)


$$\omega_t = A_o \omega_b$$

Offset voltage

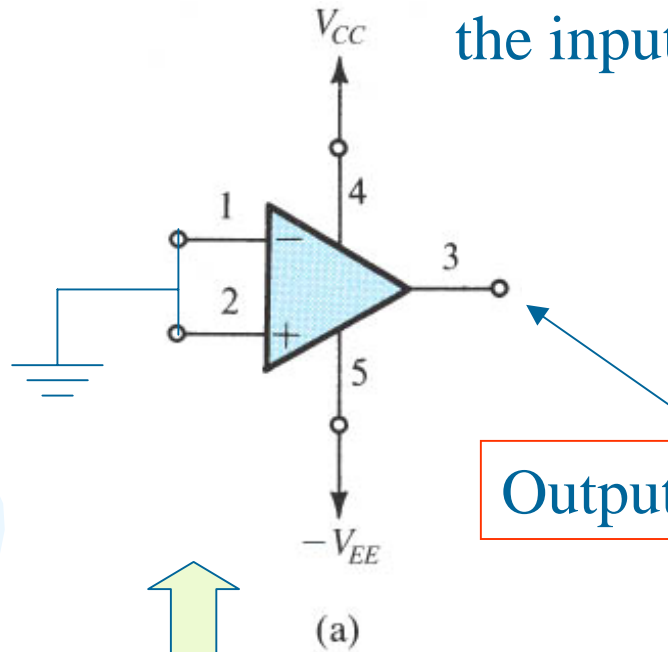From the component mismatches in the input differential stage





Output = + saturation or - saturation

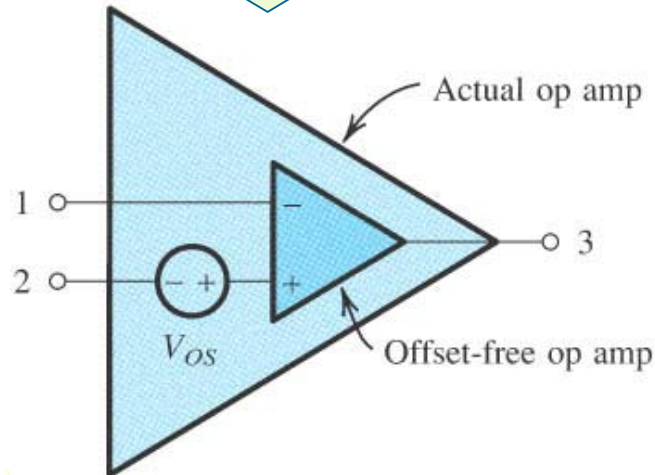


$$v_{os} \approx 1 \sim 5mV$$


May be positive or negative

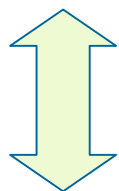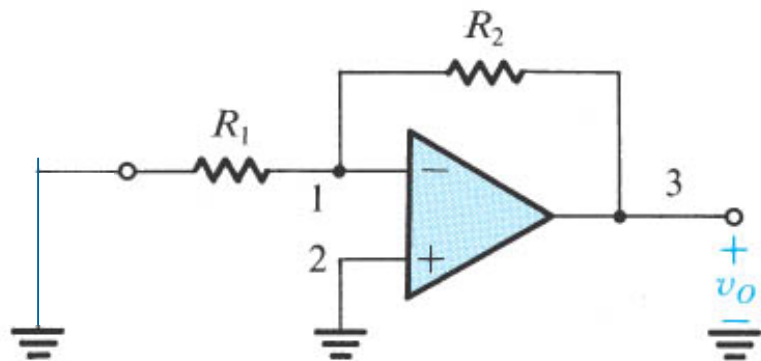



1. Reduce the allowable signal swing
2. When input is dc we would not know the output is due to v_{os} or signals

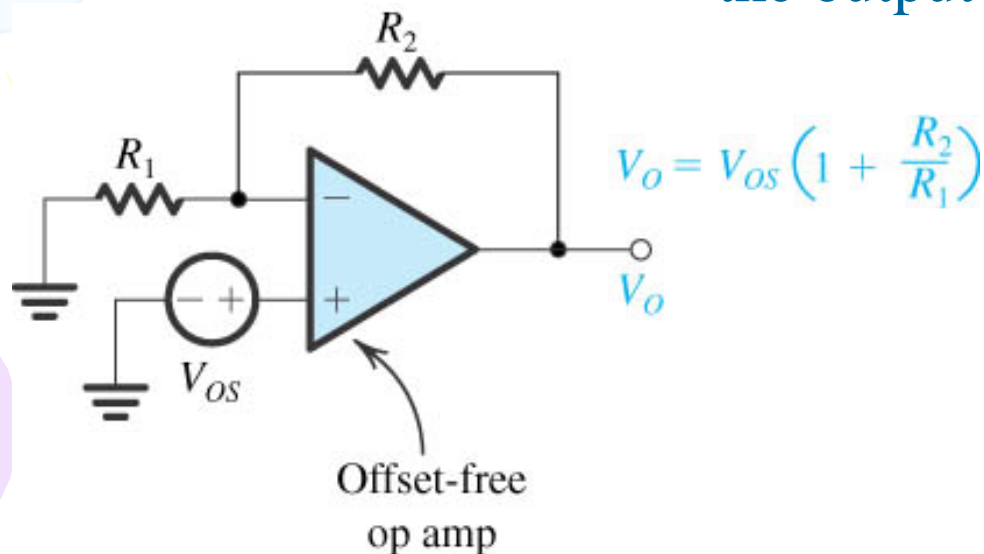

Solution 1: Offset-nulling terminals

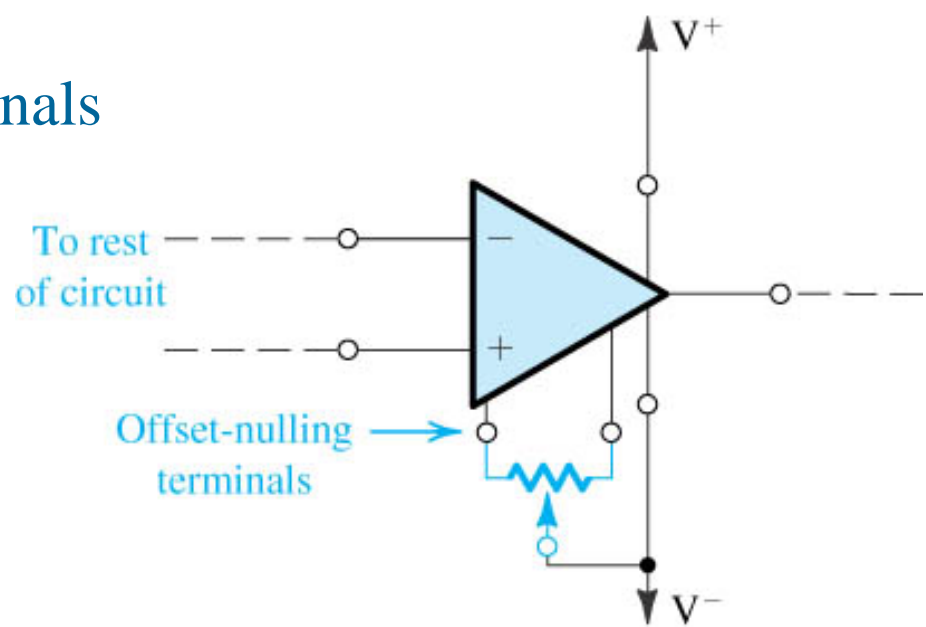

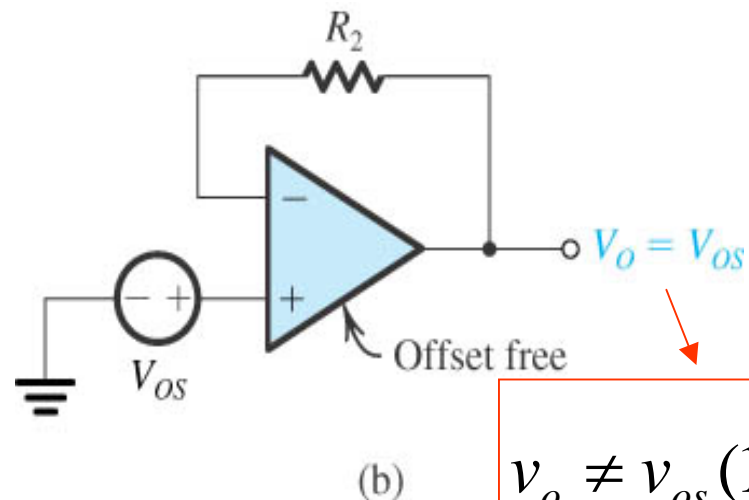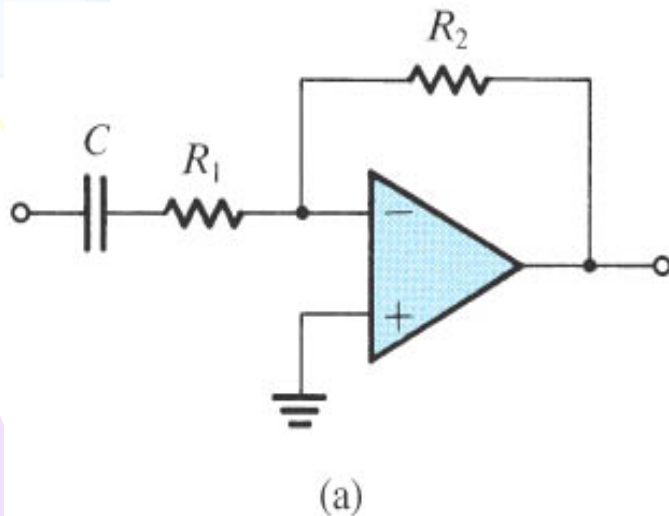Solution 2: Capacitive coupling (only ac signal be amplified)




$$v_o \neq v_{os} \left(1 + \frac{R_2}{R_1}\right)$$

Offset current


$$I_B = \frac{I_{B1} + I_{B2}}{2}$$

$$I_{os} \equiv |I_{B1} - I_{B2}|$$

Input offset current

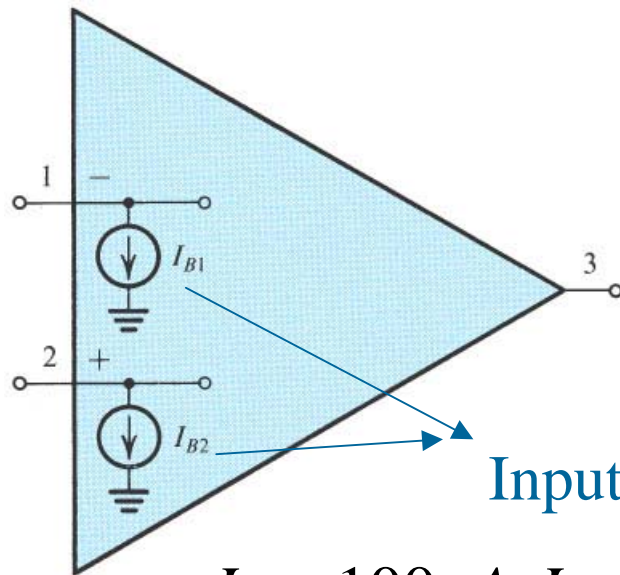

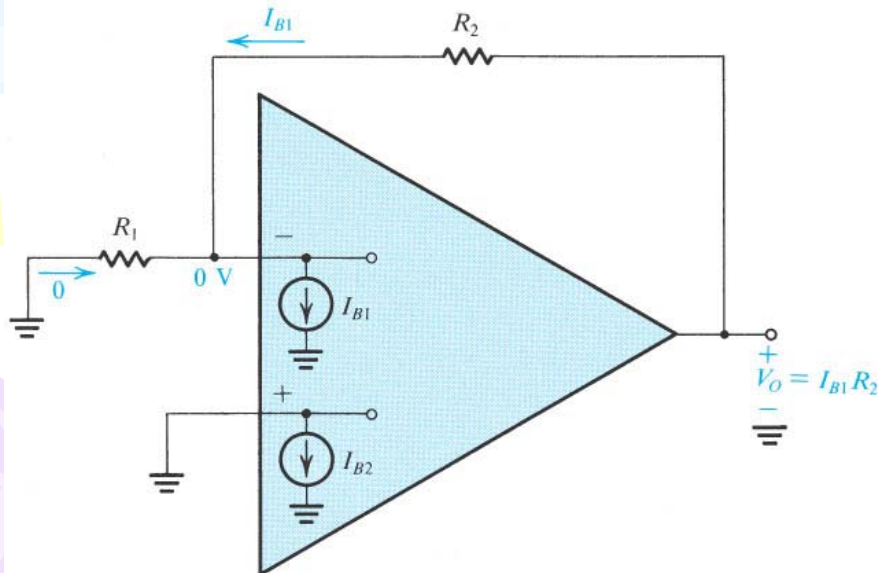
$$I_B \approx 100nA, I_{os} \approx 10nA$$



$$V_o = I_{B1} R_2 \Rightarrow R_2 \downarrow$$

Upper limit R_2

Solution : introducing R_3

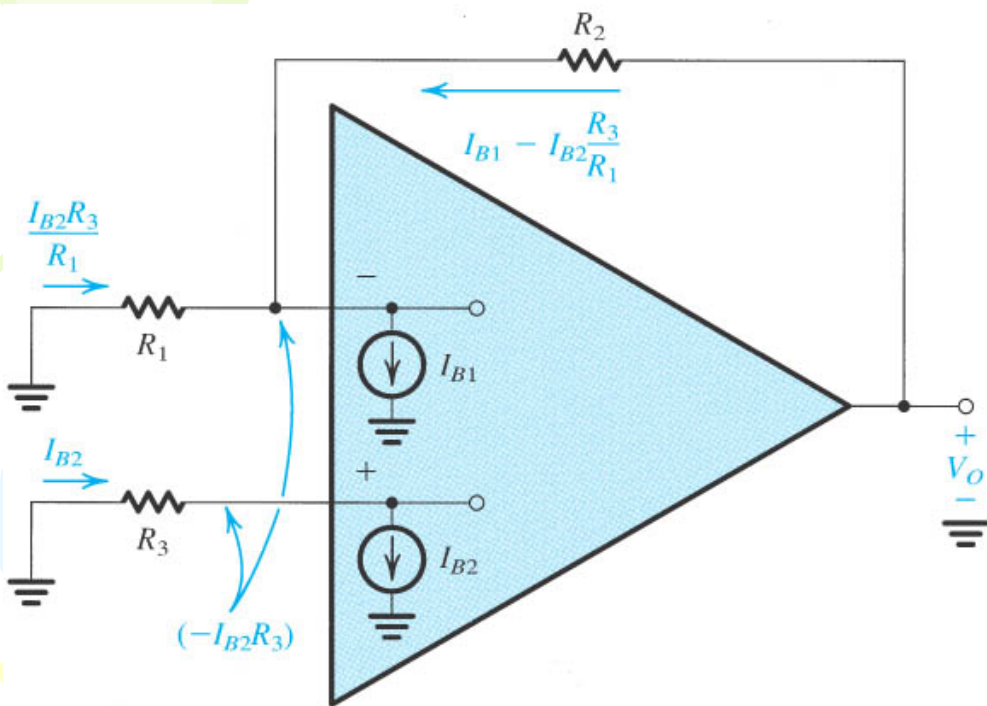

$$V_o = -I_{B2}R_3 + R_2(I_{B1} - I_{B2}\frac{R_3}{R_1})$$


$$\text{if } I_{B1} = I_{B2} = I_B$$

$$V_o = I_B[R_2 - R_3(1 + \frac{R_2}{R_1})]$$

$$\text{choose } R_3 = \frac{R_2}{(1 + \frac{R_2}{R_1})} = R_1 // R_2$$

$$\Rightarrow V_o = 0$$


Inverse amplifier

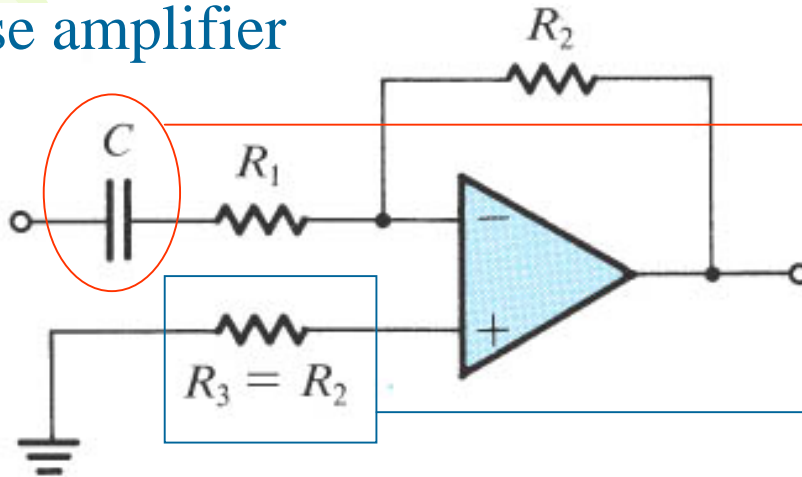

Reduce the effect of V_{os}

Reduce the effect of I_{os}



Non-inverse amplifier

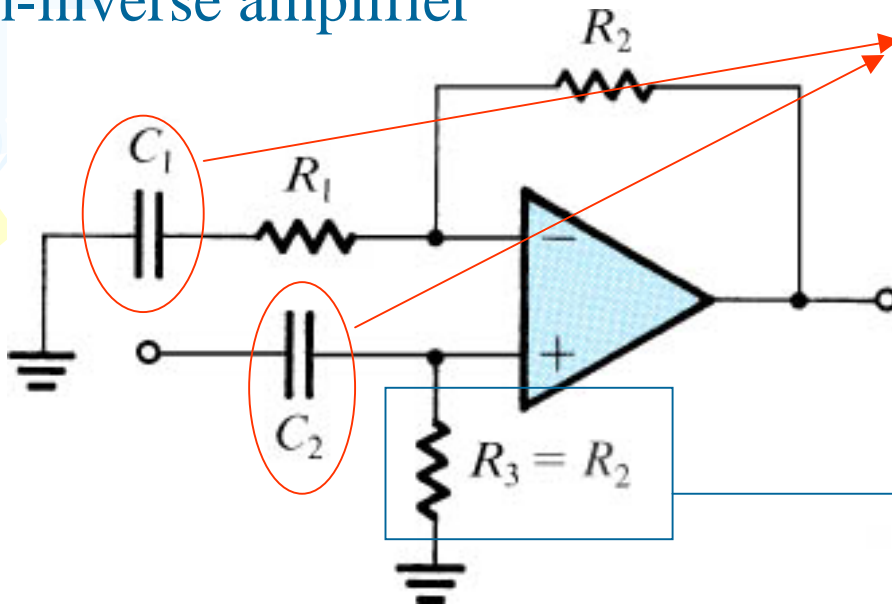

Reduce the effect of V_{os}


Reduce the effect of I_{os}

Integrator & Differentiator

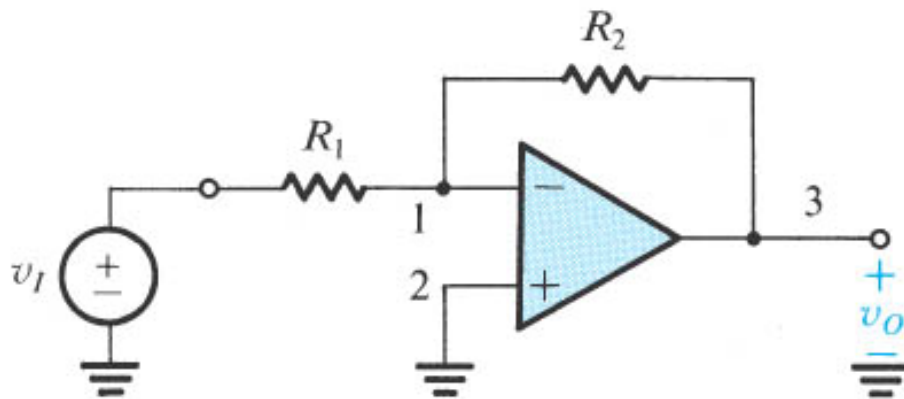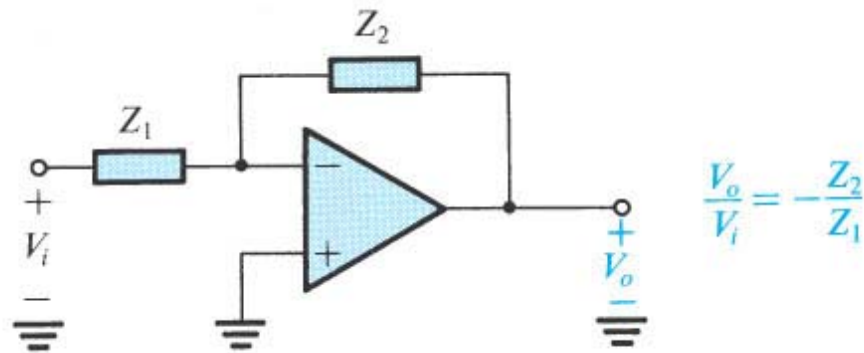

$$\frac{0 - v_I}{Z_1} + \frac{0 - v_O}{Z_2} = 0$$
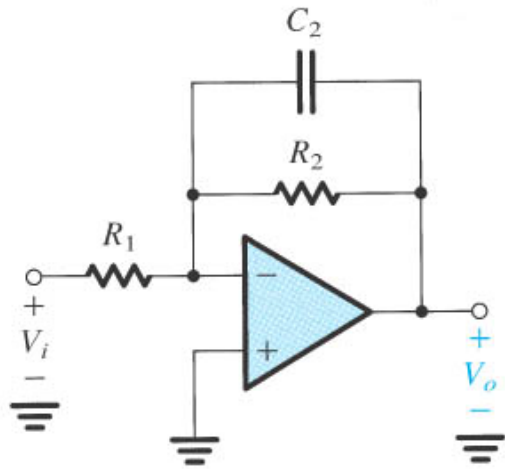
$$\Rightarrow G = \frac{v_O}{v_I} = -\frac{Z_2}{Z_1}$$



$$\frac{0 - v_i(t)}{R_1} + \frac{0 - v_o(t)}{R_2} + C_2 \frac{d[0 - v_o(t)]}{dt} = 0$$

$$\Rightarrow C_2 \frac{dv_o(t)}{dt} + \frac{v_o(t)}{R_2} = \frac{-v_i(t)}{R_1}$$



$$\Rightarrow sC_2 v_o + \frac{v_o}{R_2} = \frac{-v_i}{R_1}$$

$$\frac{v_o}{v_i} = -\frac{Z_2}{Z_1} = -\frac{1}{R_1 / R_2 + sC_2 R_1}$$

$$\Rightarrow \frac{v_o}{v_i} = -\frac{R_2 / R_1}{1 + sC_2 R_2}$$


$$\omega_0 = \frac{1}{C_2 R_2}$$

Miller Integrator

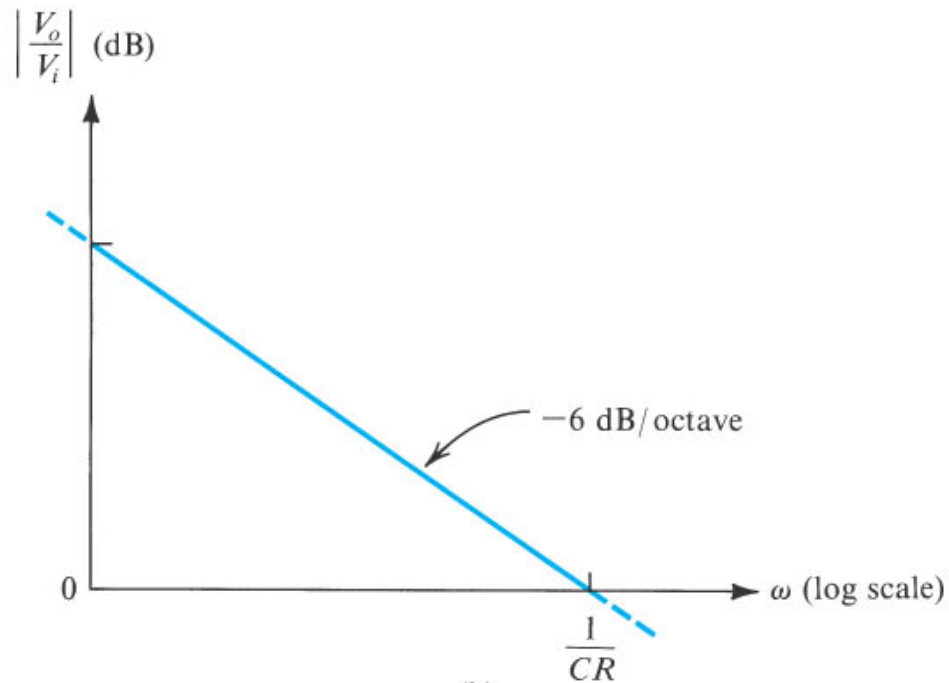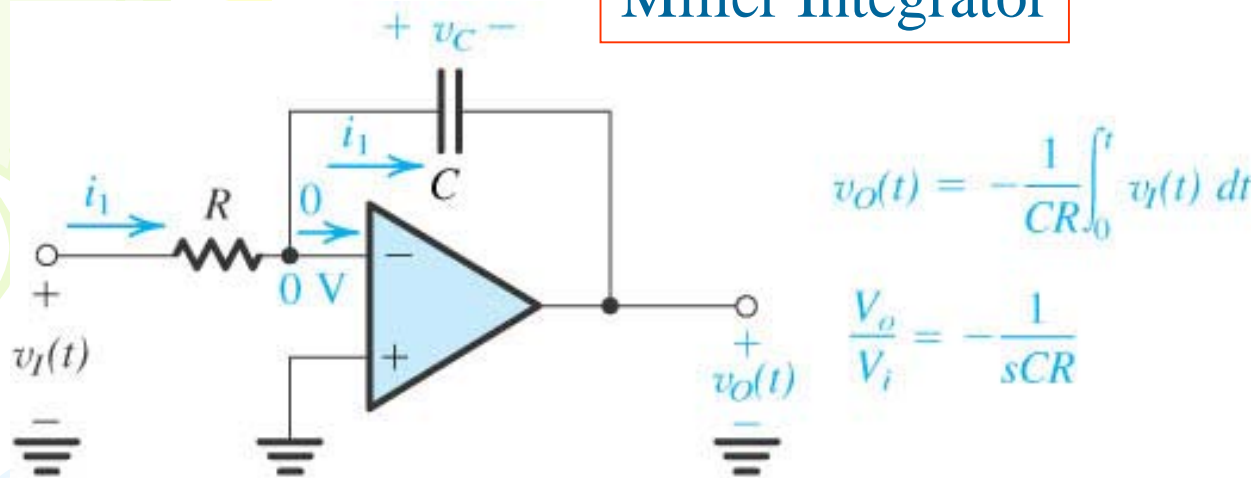

(b)

Consider V_{os} offset voltage

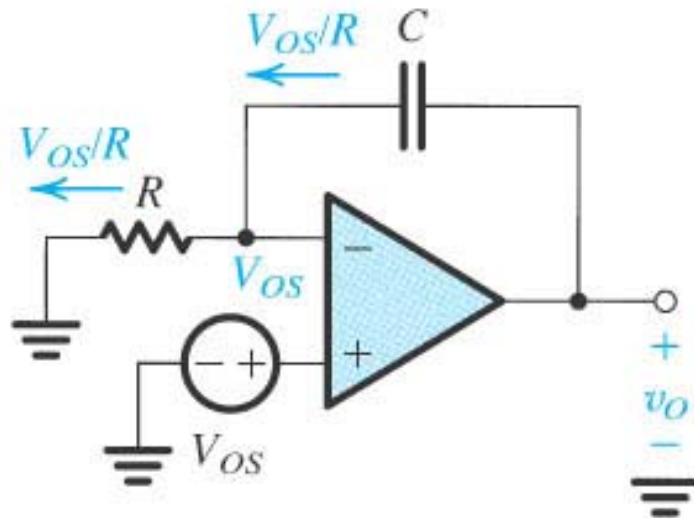


$$v_o = V_{os} + \frac{1}{C} \int_0^t \frac{V_{os}}{R} dt$$



$$= V_{os} + \frac{V_{os}}{CR} t$$

V_{sat}

Consider I_{os} offset current

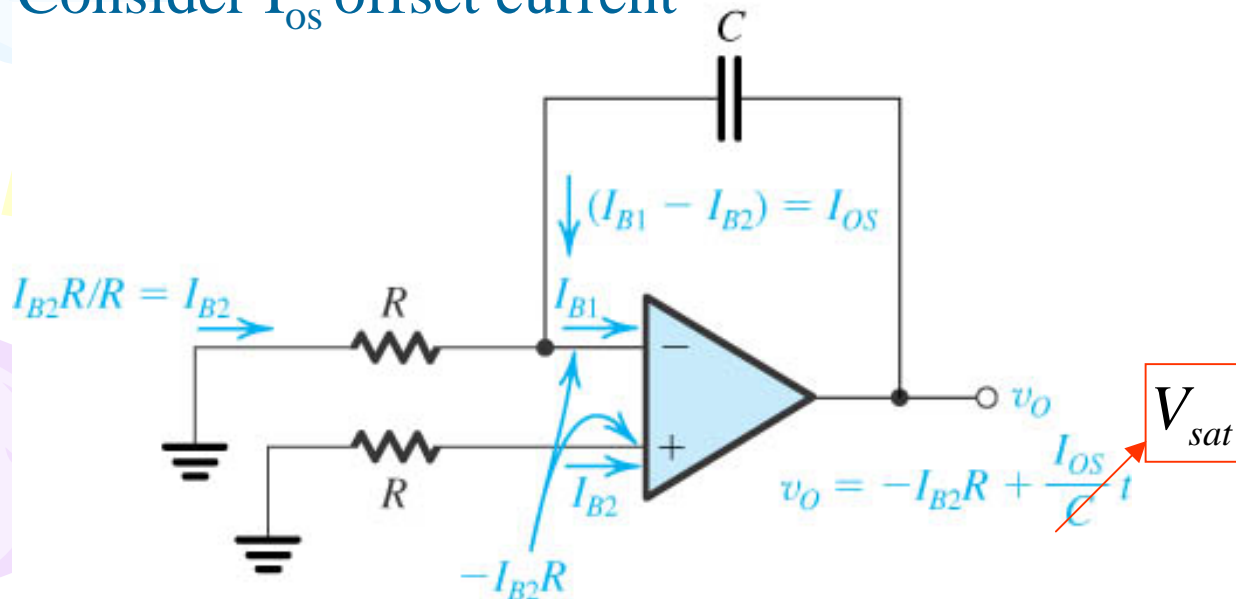

Solution :

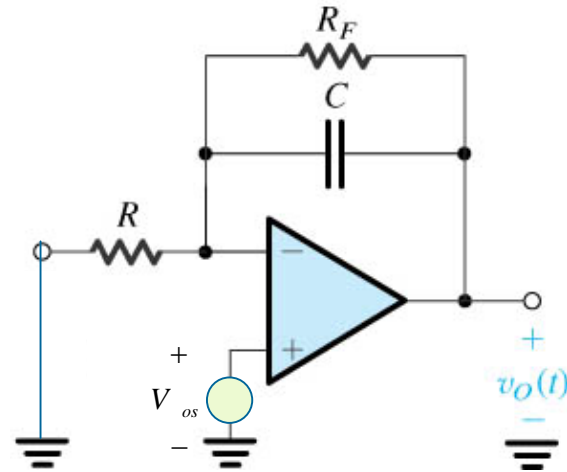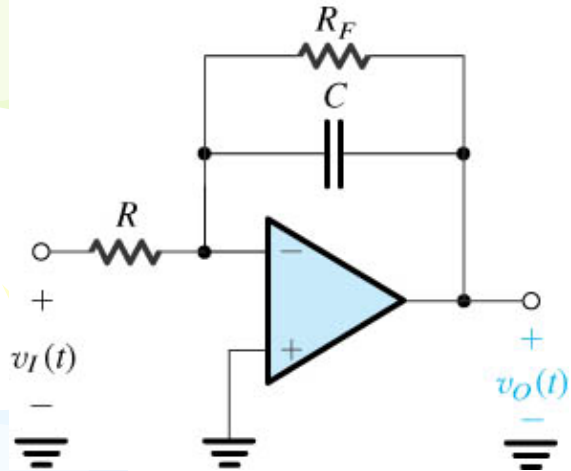

$$\frac{V_{os}}{R} + \frac{V_{os} - v_o}{\frac{1}{sC}} + \frac{V_{os} - v_o}{R_f} = 0$$

$$\frac{v_o}{V_{os}} = \frac{\frac{1}{R} + \frac{1}{R_f} + sC}{\frac{1}{R_f} + sC} = \left[1 + \frac{\frac{1}{R}}{\frac{1}{R_f} + sC} \right]$$

$$v_o = \left[1 + \frac{\frac{1}{R}}{\frac{1}{R_f} + sC} \right] V_{os} = V_{os} + \frac{\frac{1}{RC}}{\frac{1}{R_f C} + s} V_{os}$$

$$v_o(t) = V_{os} + \frac{V_{os}}{RC} e^{-\frac{1}{R_f C} t}$$

$$v_o(t) = V_{os} + \frac{V_{os}}{RC} t$$


$$\frac{-I_{B2}R}{R} + \frac{-I_{B2}R - v_o}{1/sC} + \frac{-I_{B2}R - v_o}{R_f} = 0$$

$$(sC + \frac{1}{R_f})v_o = -I_{B2}R[\frac{1}{R} + sC + \frac{1}{R_f}]$$


$$v_o = \frac{-I_{B2}R[\frac{1}{R} + sC + \frac{1}{R_f}]}{(sC + \frac{1}{R_f})} = -I_{B2}R + \frac{-I_{B2}}{(sC + \frac{1}{R_f})} = -I_{B2}R + \frac{-I_{B2}C}{(s + \frac{1}{R_f C})}$$

$$v_o(t) = -I_{B2}R + (-I_{B2}C)e^{-\frac{1}{R_f C}t}$$

$$v_o = -I_{B2}R + \frac{I_{os}}{C}t$$

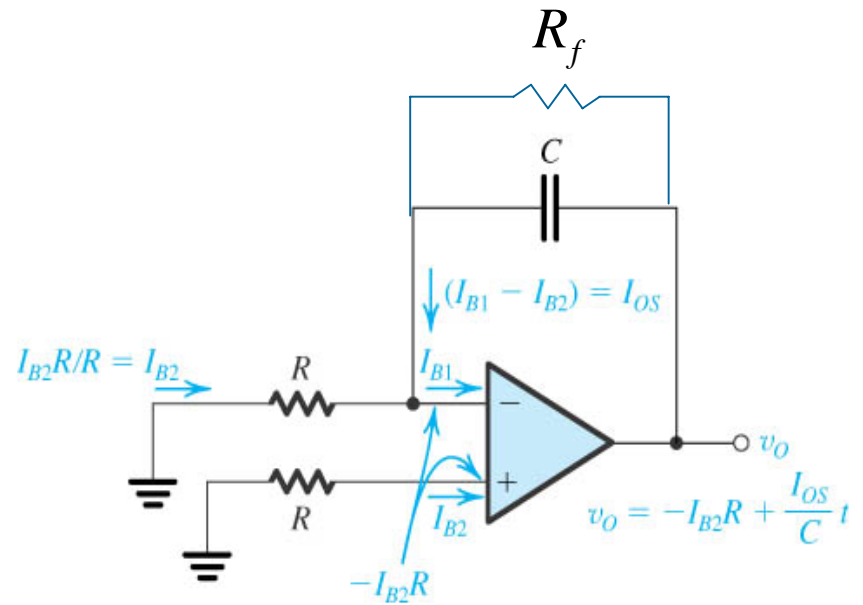

Example 2.7 sketch output response

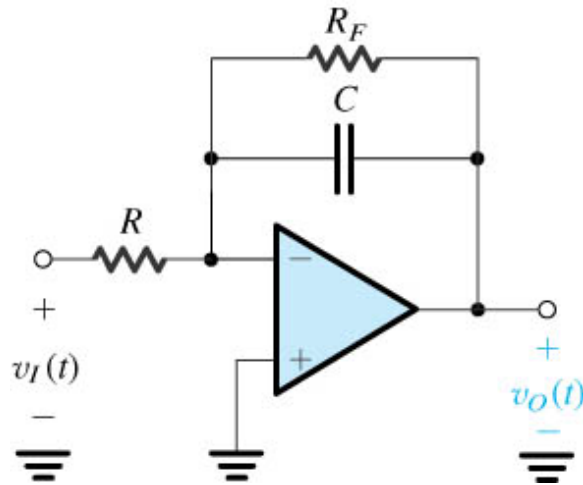

$$R = 10k$$

$$C = 10nF$$

$$R_F = \infty, \quad R_F = 1M$$

$$V_{sat} = \pm 13V$$


Case I: $R_F = \infty$

$$v_o(t) = -\frac{1}{RC} \int_0^t v_i(t) dt$$

Case II: $R_F = 1M$

$$\frac{v_O}{v_I} = -\frac{R_F / R_1}{1 + sC_2R_F}$$


Differentiator

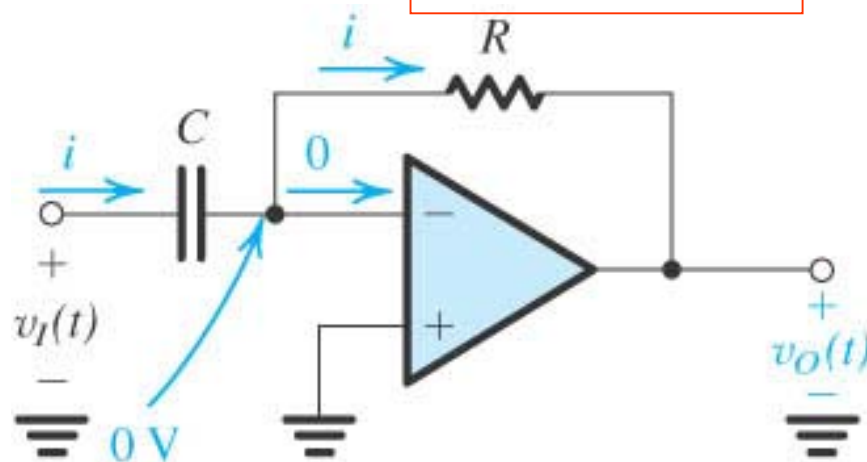

$$i(t) = C \frac{dv_I(t)}{dt}$$


$$v_O(t) = -CR \frac{dv_I(t)}{dt}$$

$$\frac{V_o}{V_i} = -sCR$$

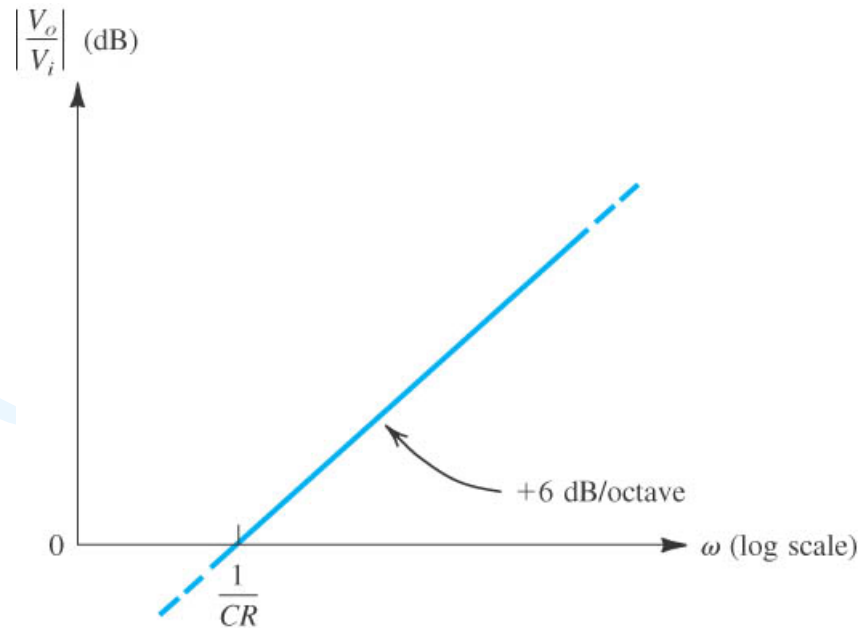


(b)

Problem *2.31

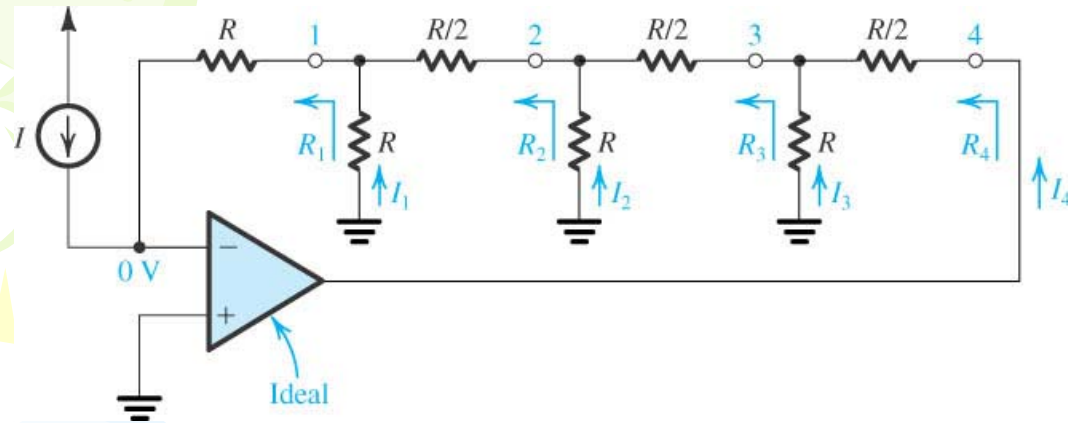

Problem *2.43

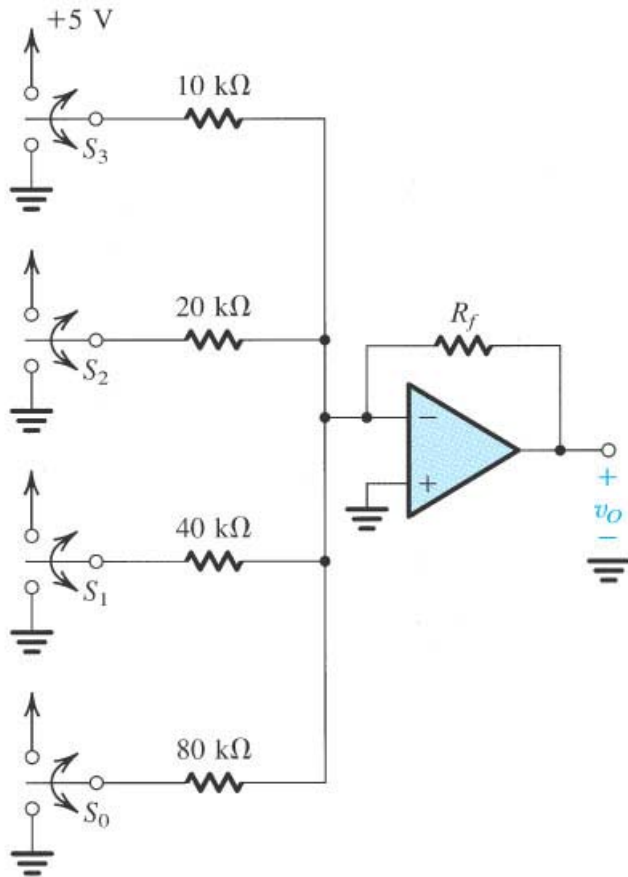

$$\frac{V_- - S_3}{10k} + \frac{V_- - S_2}{20k} + \frac{V_- - S_1}{40k} + \frac{V_- - S_0}{80k} + \frac{V_- - V_0}{R_f} = 0$$


$$\frac{0 - 5S_3}{10k} + \frac{0 - 5S_2}{20k} + \frac{0 - 5S_1}{40k} + \frac{0 - 5S_0}{80k} + \frac{0 - V_0}{R_f} = 0$$

$$V_0 = -5R_f \left[\frac{S_3}{10k} + \frac{S_2}{20k} + \frac{S_1}{40k} + \frac{S_0}{80k} \right]$$


$$V_0 = -\frac{5R_f}{80k} [8S_3 + 4S_2 + 2S_1 + 1S_0]$$

$$= -\frac{R_f}{16k} [8S_3 + 4S_2 + 2S_1 + 1S_0]$$


Problem **2.69

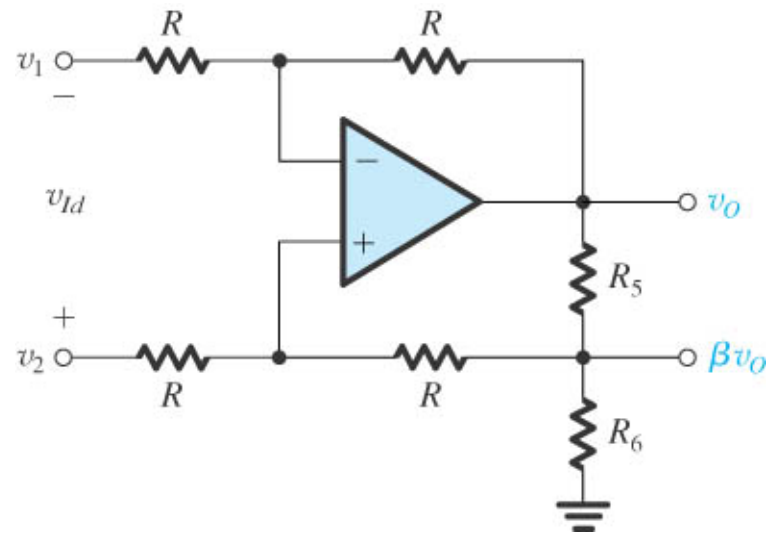


Problem *2.77

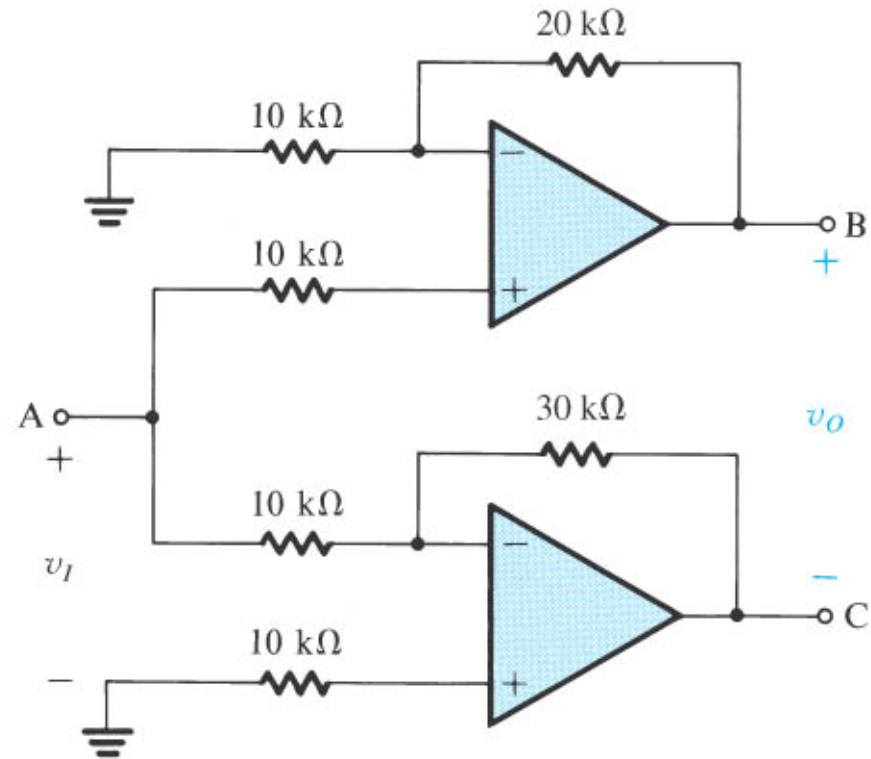

Problem *2.78

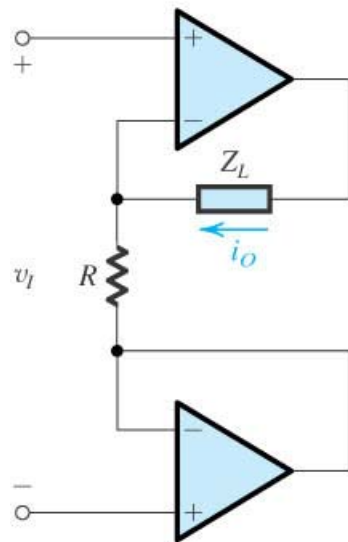


(a)

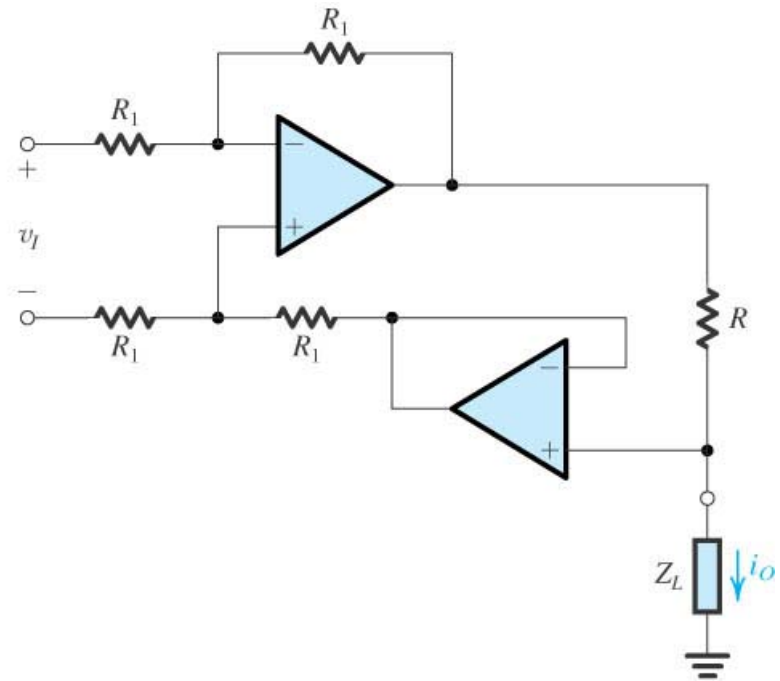

(b)

Problem C*2.126

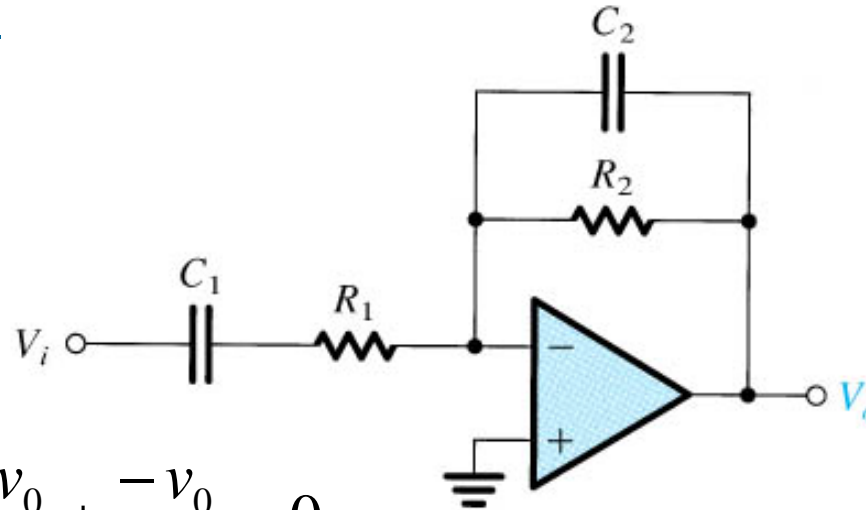

$$\frac{-v_i}{R_1 + 1/sC_1} + \frac{-v_o}{R_2} + \frac{-v_o}{1/sC_2} = 0$$

$$\frac{-v_o}{R_2} + \frac{-v_o}{1/sC_2} = \frac{v_i}{R_1 + 1/sC_1}$$

$$\frac{-R_2(R_2 + 1/sC_2)}{R_2} v_o = \frac{v_i}{R_1 + 1/sC_1}$$

$$\frac{v_o}{v_i} = -\frac{R_2}{(R_1 + 1/sC_1)(R_2 + 1/sC_2)}$$



Non-ideal OP amplifiers

1. Type A: Finite open-loop gain (unknown)
2. Type B: Finite open-loop gain = K
3. Type C: $A_{vo} \neq \infty, R_o \neq 0, R_i \neq \infty$

1. Infinite input impedance
2. Zero output impedance
3. Zero common-mode gain
4. Infinite open-loop gain
5. Infinite bandwidth

} Ideal OPA characters

Type A: Finite open-loop gain (unknown)

$$v_- \neq v_+$$



Three balloons (green, blue, and purple) are positioned on the left side of the slide. Each balloon has a string and several small yellow triangular flags attached to it.

Type B: Finite open-loop gain =K

$$v_o = K(v_- - v_+)$$

Type C:
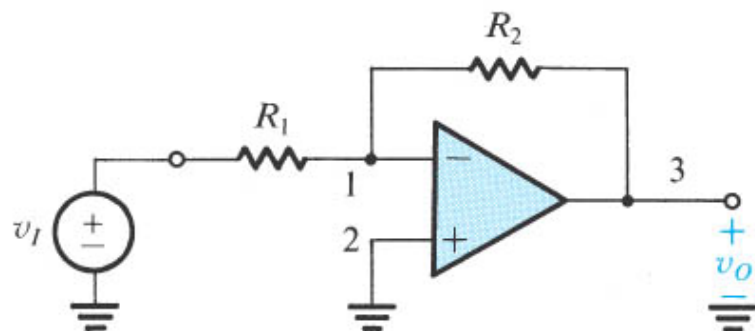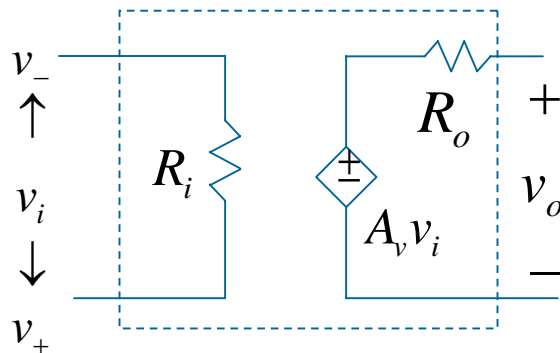
$$A_v \neq \infty, R_o \neq 0, R_i \neq \infty$$



$$\frac{v_- - v_I}{R_1} + \frac{v_- - v_+}{R_i} + \frac{v_- - v_o}{R_2} = 0$$

$$\frac{v_o - v_-}{R_2} + \frac{v_o - A_v(v_- - v_+)}{R_o} = 0$$

