
# Lecture 06


## **BJT Circuits**
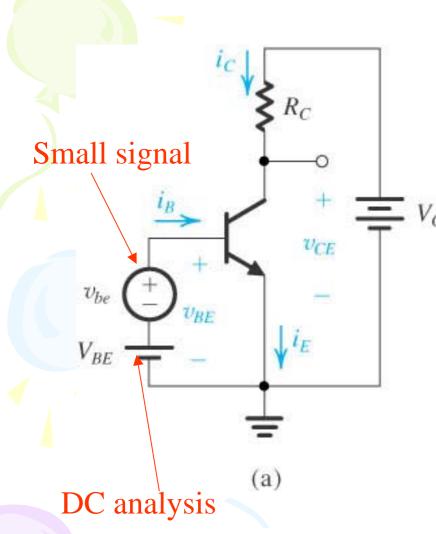
# topics

- Small-signal operation
  - Hybrid  $\pi$  model
  - T-model
  - Early Effect
- Single-stage BJT amplifiers
  - Amplifier basic structure
  - CE Amplifier
  - CB Amplifier
  - CC Amplifier



### DC analysis

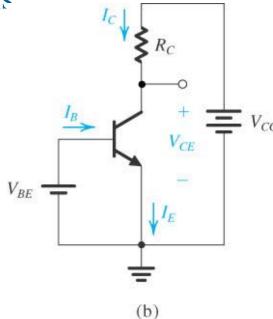


$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$I_{C} = I_{S}e^{\frac{V_{BE}}{V_{T}}}$$

$$I_{E} = \frac{I_{C}}{\alpha}$$

$$I_B = \frac{I_C}{\beta}$$

$$V_C = V_{CE} = V_{CC} - I_C R_C$$

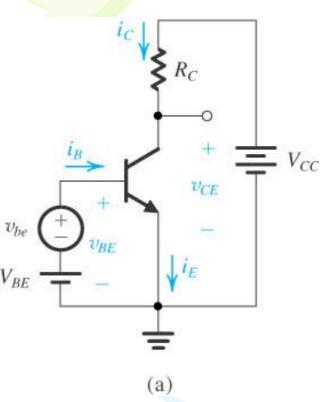


$$i_{C} = I_{S}e^{\frac{v_{BE}}{V_{T}}} = I_{S}e^{(\frac{V_{BE}+v_{be}}{V_{T}})} = I_{S}e^{\frac{V_{BE}}{V_{T}}}e^{\frac{v_{be}}{V_{T}}} = I_{C}e^{\frac{v_{be}}{V_{T}}}$$

$$i_{C} \approx I_{C}(1 + \frac{v_{be}}{V_{T}}) \leftarrow if \quad v_{be} << V_{T}$$


$$i_c = \frac{I_C}{V_T} v_{be} = g_m v_{be}$$


$$g_m = \frac{I_C}{V_T}$$


transconductance

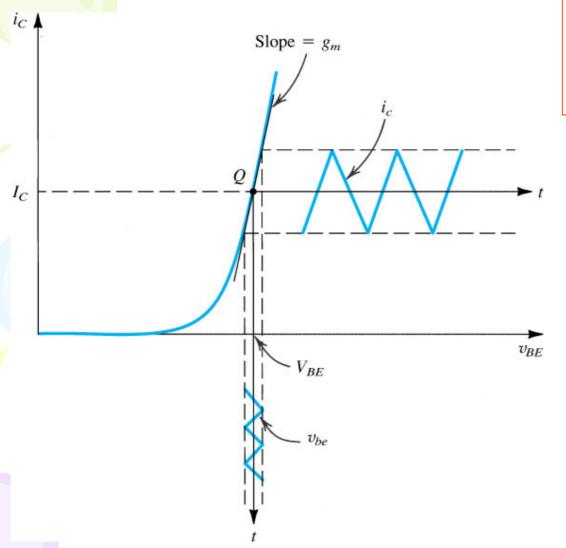


$$g_m = \frac{\partial i_C}{\partial v_{BE}}\Big|_{i_C = I_C}$$

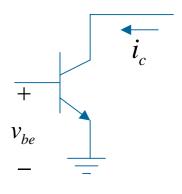

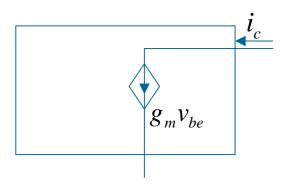

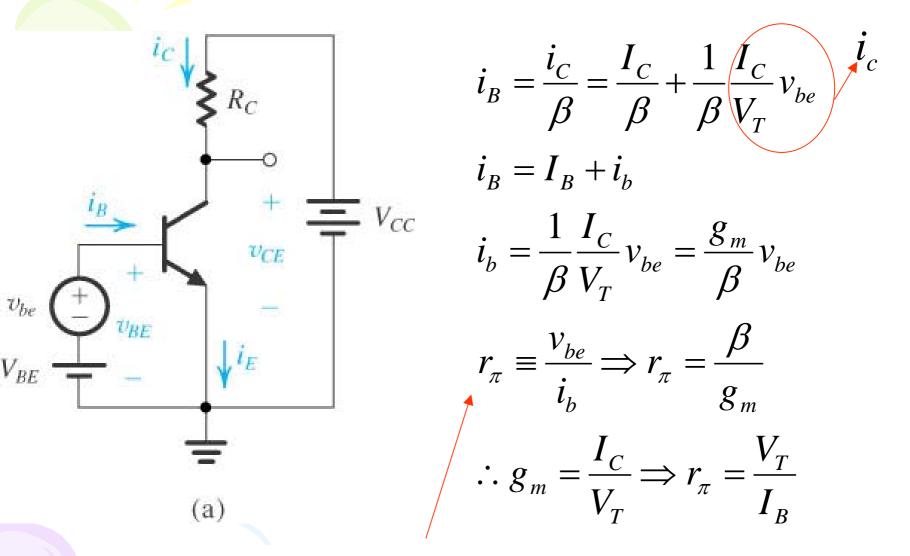

Small-signal input resistance

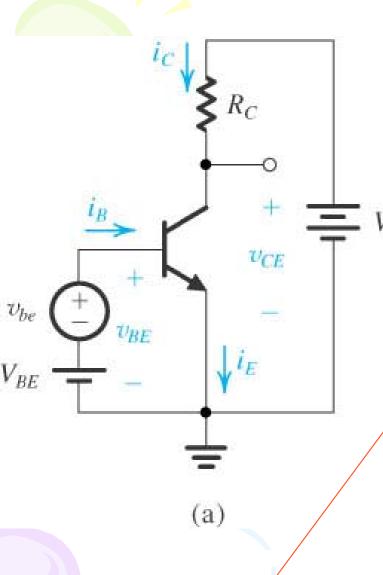

Emitter resistance

$$i_{E} = \frac{i_{C}}{\alpha} = \frac{I_{C}}{\alpha} + \frac{i_{c}}{\alpha}$$

$$i_{E} = I_{E} + i_{e} \quad i_{c}$$

$$i_{e} = \frac{I_{C}}{\alpha V_{T}} v_{be} = \frac{I_{E}}{V_{T}} v_{be}$$


$$r_{e} \equiv \frac{v_{be}}{i_{e}} \Rightarrow r_{e} = \frac{V_{T}}{I_{E}}$$

$$\therefore g_m = \frac{I_C}{V_T} \Longrightarrow r_e = \frac{\alpha}{g_m} \approx \frac{1}{g_m}$$

$$v_{be} = i_b r_\pi = i_e r_e$$

$$r_{\pi} = \frac{i_e}{i_b} r_e \Longrightarrow r_{\pi} = (\beta + 1) r_e$$

Microelectronic Circuit by meiling CHEN

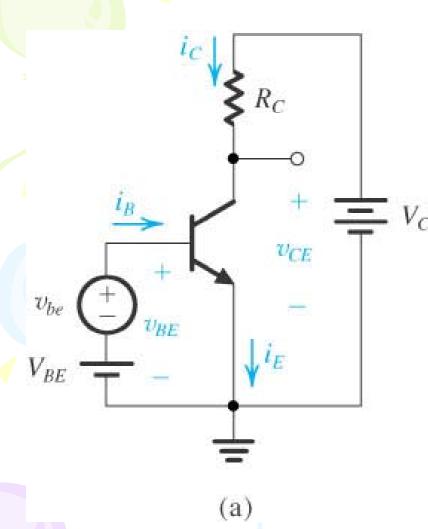

#### Voltage gain

$$A_{v} \equiv \frac{v_{c}}{v_{be}}$$

$$v_{C} = V_{CC} - i_{C}R_{C}$$

$$V_{CC} = V_{CC} - (I_{C} + i_{c})R_{C}$$

$$= (V_{CC} - I_{C}R_{C}) - i_{c}R_{C}$$

$$= V_{C} - i_{c}R_{C}$$

$$= V_{C} - i_{c}R_{C}$$

$$v_{c} = -i_{c}R_{C} = -g_{m}v_{be}R_{C}$$

$$\Rightarrow A_{v} = -g_{m}R_{C} = -\frac{I_{C}R_{C}}{V_{T}}$$


### Hybird- π Model


$$i_{e} = \frac{v_{be}}{r_{\pi}} + g_{m}v_{be} = \frac{v_{be}}{r_{\pi}}(1 + g_{m}r_{\pi})$$


$$= \frac{v_{be}}{r_{\pi}}(1 + \beta) = \frac{v_{be}}{r_{\pi}} = \frac{v_{be}}{r_{e}}$$

$$\frac{v_{be}}{r_{e}}(1 + \beta)$$
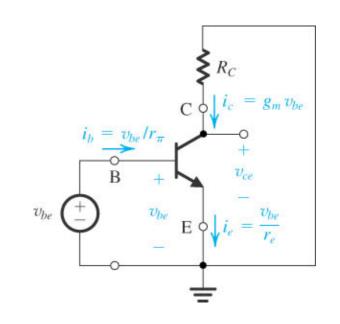
$$g_m v_{be} = g_m (i_b r_\pi) = \beta i_b$$



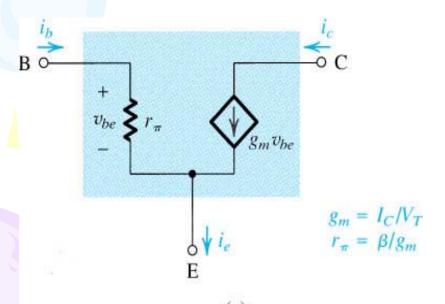

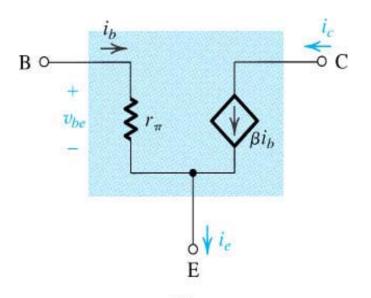


#### T- Model

$$i_b = \frac{v_{be}}{r_e} + g_m v_{be} = \frac{v_{be}}{r_e} (1 + g_m r_e)$$


$$= \frac{v_{be}}{r_e}(1+\alpha) = \frac{v_{be}}{r_e}(1-\frac{\beta}{\beta+1}) = \frac{v_{be}}{r_{\pi}}$$

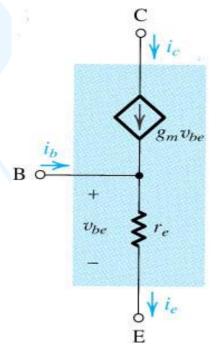
$$g_m v_{be} = g_m (i_e r_e) = \alpha i_e$$



$$g_m = I_C/V_T$$
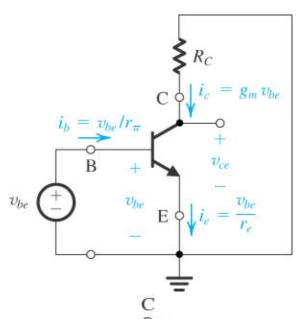
$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$$




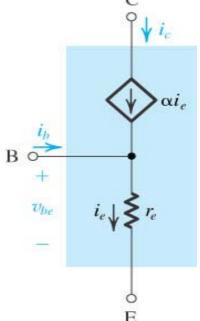


(a) ..... Circuit by meiling CHEN

#### Example 5.14

### DC analysis

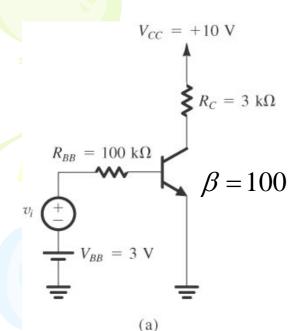

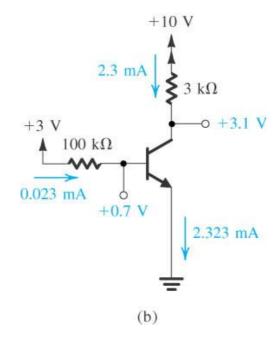

DC analysis

$$I_B = \frac{V_{BB} - V_{BE}}{R_{BB}} = \frac{3 - 0.7}{100k} = 0.023mA$$


$$I_C = \beta I_B = 100 \times 0.023 = 2.3 \text{mA}$$

$$I_E = \frac{I_C}{\alpha} = \frac{2.3}{0.99} = 2.32 mA$$

$$V_C = V_{CC} - I_C R_C = 10 - 2.3 \times 3 = 3.1V$$

Confirm transistor in active mode

#### Small-signal analysis

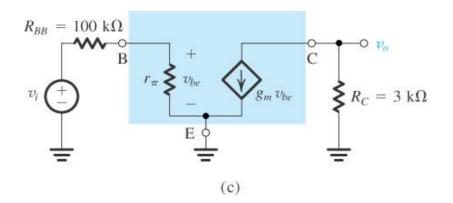

$$r_{e} = \frac{V_{T}}{I_{E}} = \frac{25mV}{2.32mA} = 10.8\Omega$$


$$g_{m} = \frac{I_{C}}{V_{T}} = \frac{2.3mA}{25mV} = 92 \frac{mA}{V}$$


$$r_{\pi} = \frac{\beta}{g_{m}} = \frac{100}{92} = 1.09k\Omega$$


$$v_{be} = v_i \frac{r_{\pi}}{r_{\pi} + R_{BB}} = v_i \frac{1.09}{101.09} = 0.011v_i$$


$$v_o = -g_m v_{be} R_C = -92 \times 0.011v_i \times 3 = -3.04v_i$$


$$A_v = \frac{v_o}{v_i} = -3.04$$

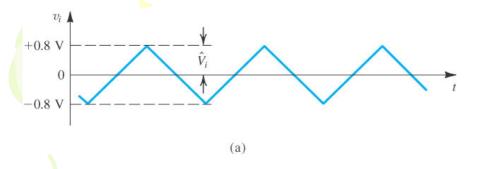

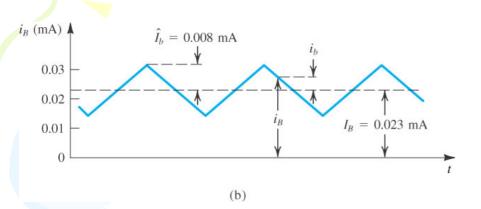


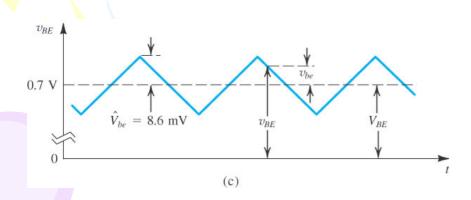

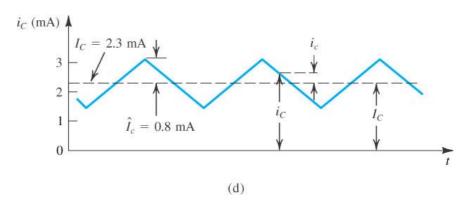

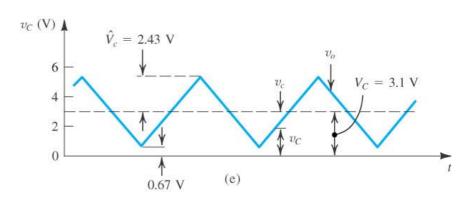

#### Example 5.16

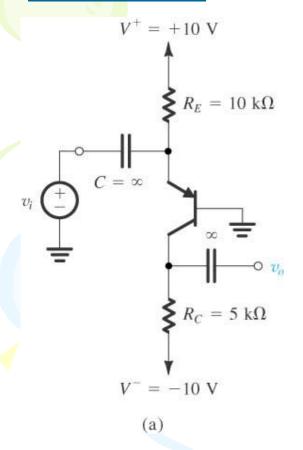


### DC analysis

$$I_E = \frac{10 - 0.7}{10k} = 0.93mA$$


$$I_C = \alpha I_E = 0.99 \times 0.93 = 0.92mA$$

$$V_C = I_C R_C - 10V = -5.4V$$

Confirm transistor in active mode

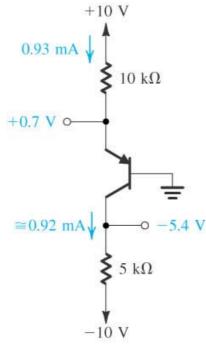

Microelectronic Circuit I meiling CHEN

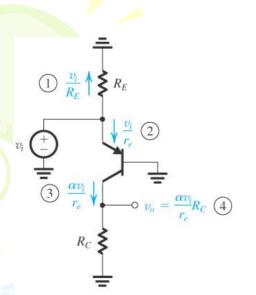

### Small-signal analysis

$$r_e = \frac{V_T}{I_E} = \frac{25mV}{0.93mA} = 27\Omega$$


$$v_o = -\alpha i_e R_C$$

$$i_e = -\frac{v_i}{r}$$


$$\Rightarrow v_o = \alpha \frac{R_C}{r_o} v_i$$


$$A_{v} = \frac{v_{o}}{v_{i}} = \alpha \frac{R_{C}}{r_{e}} = 0.99 \frac{5k}{27} = 183.3$$

(c)

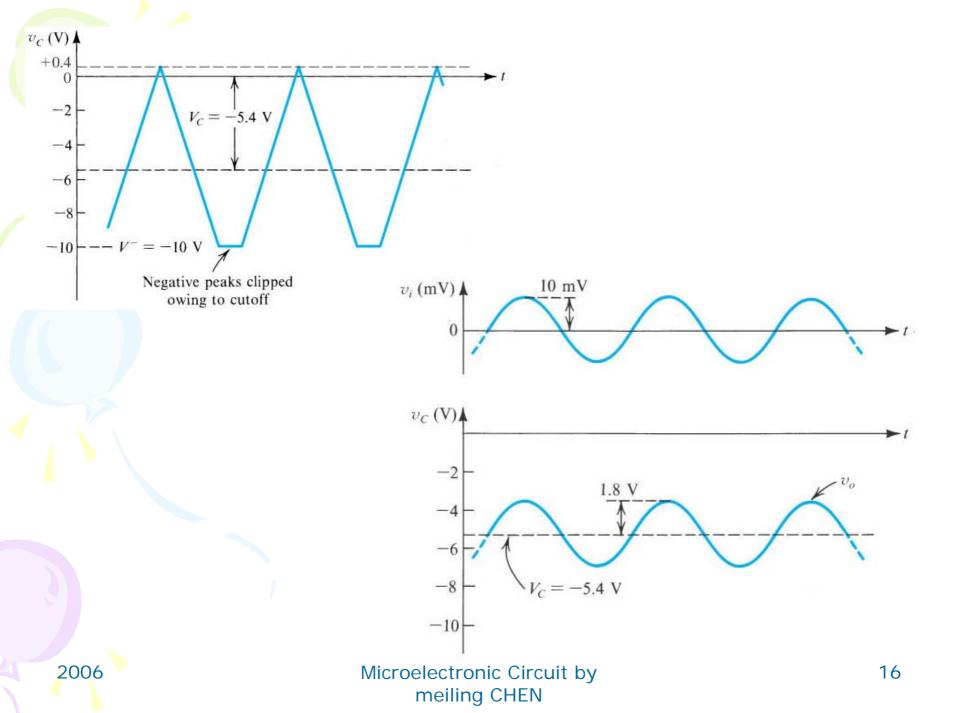
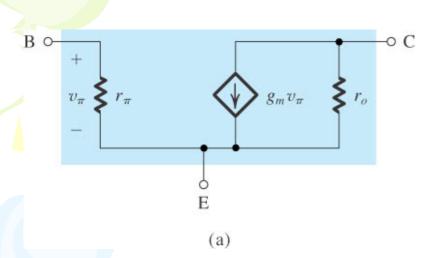
#### Small-signal model with Early Effect




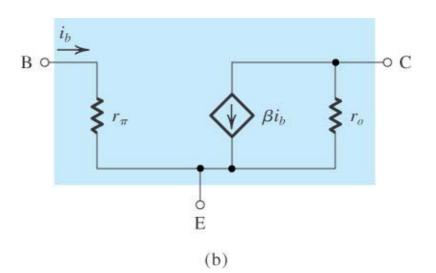

$$r_{o} = \frac{V_{A} + V_{CE}}{I_{E}} \approx \frac{V_{A}}{I_{E}}$$

$$V_{A} \rightarrow Early \quad voltage$$

#### Exercise 5.40

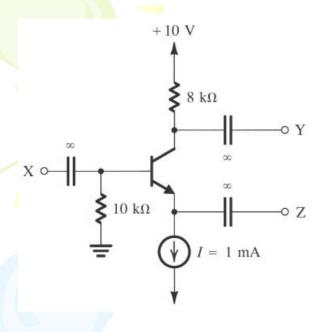

$$I_C = \alpha I_E = 0.99 \times 1 \text{mA} = 0.99 \text{mA}$$

$$V_B = -I_B \times 10k = -\frac{0.99m}{100} \times 10k = -0.099V$$

$$V_E = V_B - 0.7V = -0.799V$$
 Active mode

$$V_C = I_C R_C - 10V = -0.99m \times 8k + 10V = 2.08V$$

$$\stackrel{\circ}{\parallel} \qquad r_o = \frac{V_A}{I_E} = \frac{100mV}{1mA} = 100\Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{0.99mA}{25mV} = 0.0396 \frac{mA}{V}$$


$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{0.0396} = 2.525k\Omega$$

## given

$$I_F = 1mA$$

$$\beta = 100$$

$$V_{\scriptscriptstyle A} = 100V$$

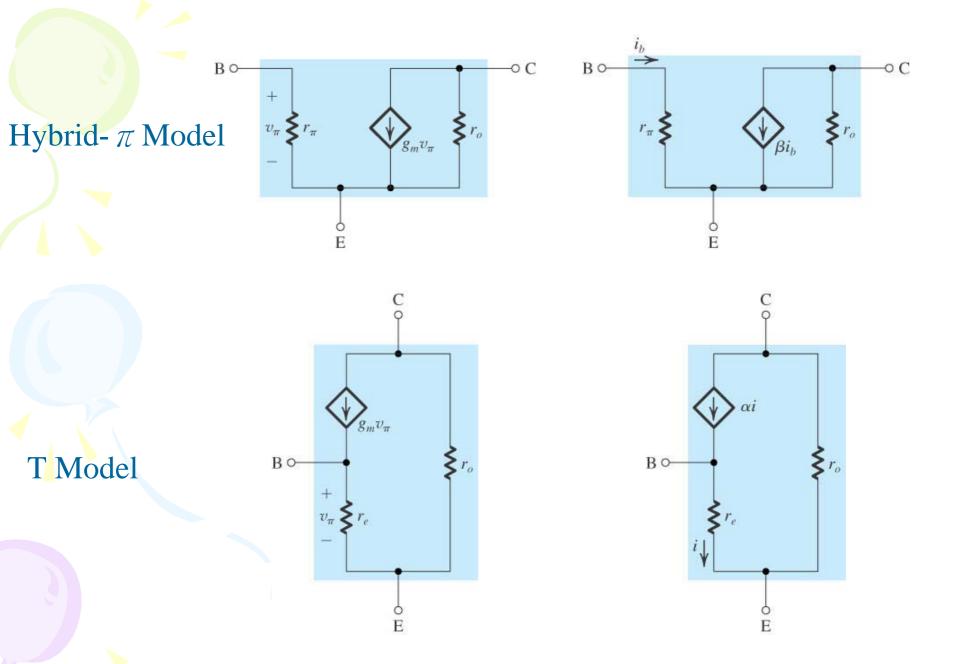


# Signal-stage BJT amplifiers

- Common-Emitter (CE) Amplifier
- Common-Base (CB) Amplifier
- Common-Collector (CC) Amplifier
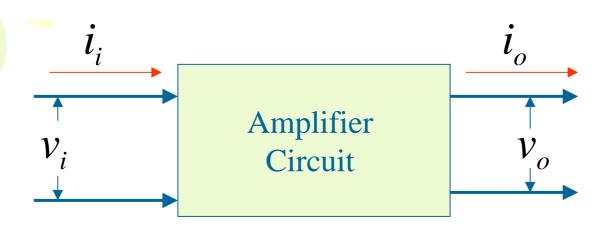
# **Amplifier Categories**

- Voltage Amplifier
- Current Amplifier
- Transconductance Amplifier
- Transresistance Amplifier



$$gain \equiv \frac{output}{input}$$

$$powergain \quad A_P \equiv \frac{v_o i_o}{v_i i_i}$$


$$voltagegain \quad A_{v} \equiv \frac{v_{o}}{v_{i}}$$


currentgain 
$$A_i \equiv \frac{i_o}{i_i}$$

transconduc tan ce 
$$G_m \equiv \frac{i_o}{v_i}$$

transresis tan ce 
$$R_m \equiv \frac{V_o}{i_i}$$

## Voltage Amplifier

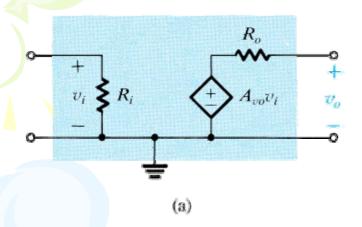

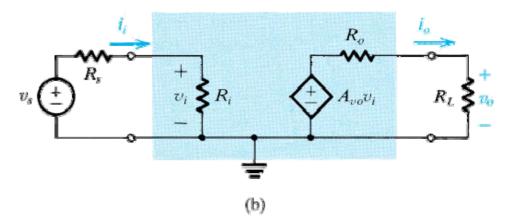

#### Open-Circuit voltage Gain:


$$A_{vo} \equiv \frac{v_o}{v_i}\Big|_{i_o=0}$$

#### Ideal voltage amplifier:

$$R_i = \infty$$

$$R_o = 0$$

## Current Amplifier

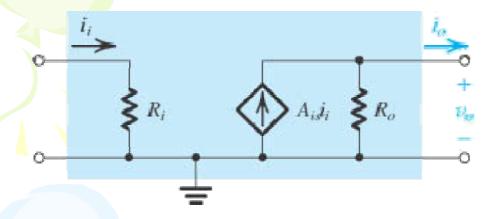


#### Short-Circuit current Gain:

$$A_{is} \equiv \frac{\dot{i}_o}{\dot{i}_i}\Big|_{v_o=0}$$

#### Ideal voltage amplifier:

$$R_i = 0$$
$$R_o = \infty$$

## Transconductance Amplifier

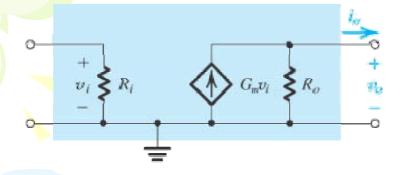

#### **Short-Circuit Transconductance:**


$$G_m \equiv \frac{i_o}{v_i}\Big|_{v_o=0}$$

## **Ideal transconductance amplifier:**

$$R_i = \infty$$

$$R_o = \infty$$

## Transresistance Amplifier

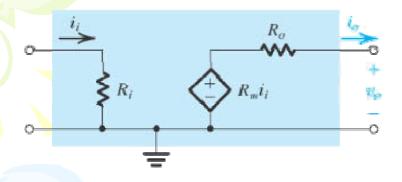


## Open-Circuit Transresistance: Ideal Transresistance amplifier:

$$R_m \equiv \frac{v_o}{i_i}\Big|_{i_o=0}$$


$$R_i = 0$$
$$R_o = 0$$


#### Example 1.3


## Cascade Amplifier

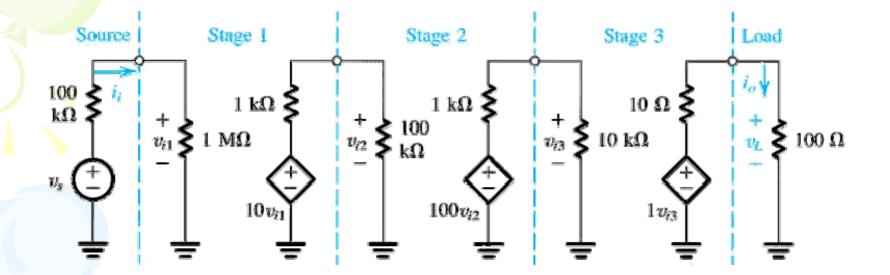



## Amplifier basic structure

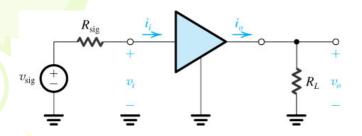


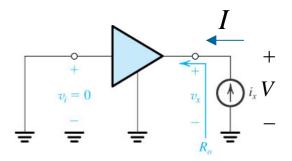

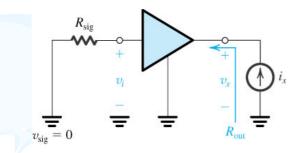


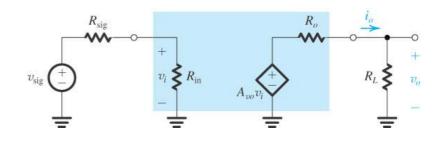


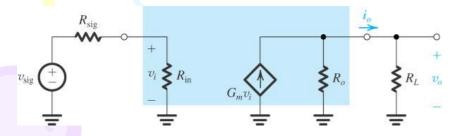

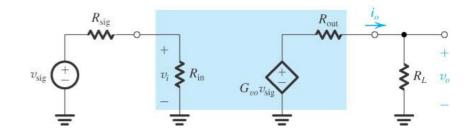

#### Definitions:

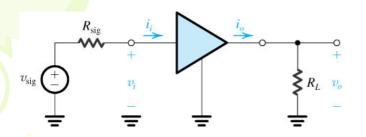

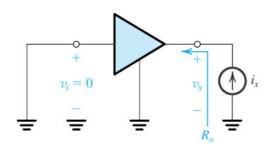

No load input resistance  $R_i \equiv \frac{v_i}{i}\Big|_{R_L = \infty}$ 

$$R_i \equiv \frac{v_i}{i_i}\Big|_{R_L = \infty}$$

Short-circuit transconductance

Input resistance

$$R_{in} \equiv \frac{v_i}{i_i}$$

 $G_m \equiv \frac{l_o}{l_{R_L=0}}$ Amplifier propre output resistante

Open-circuit voltage gain 
$$A_v \equiv \frac{v_o}{v_i}\Big|_{R_L = \infty}$$

$$A_{v} \equiv \frac{v_{o}}{v_{i}} \Big|_{R_{L} = \infty}$$

$$R_o \equiv \frac{v_x}{i_x} \Big|_{v_i = 0}$$

Voltage gain

$$A_{v} \equiv \frac{v_{o}}{v_{c}}$$

Output resistance

$$R_o \equiv \frac{v_x}{i_x} \Big|_{v_{signal} = 0}$$

$$A_{v} \equiv \frac{v_{o}}{v_{i}}$$

Overall voltage gain

Open-circuit overall voltage gain 
$$G_{vo} \cong \frac{v_o}{v_{signal}}\Big|_{R_L = \infty}$$
 Overall voltage gain


Short-circuit current gain  $A_{is} \equiv \frac{i_o}{i_c}\Big|_{R_L=0}$ 

$$A_i \equiv \frac{i_o}{i}$$


$$G_{v} \equiv \frac{v_{o}}{v_{signal}}$$


Current gain
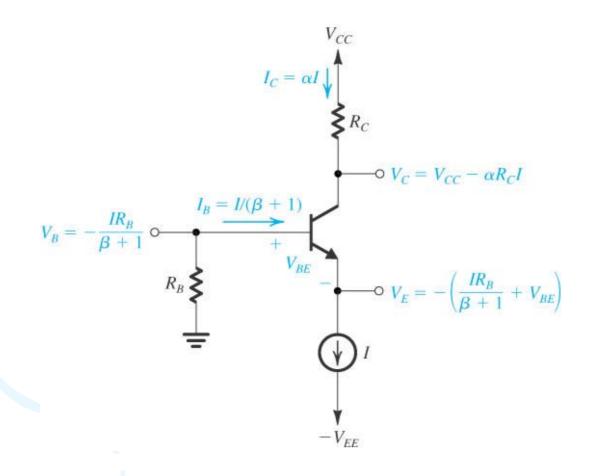
#### Constant current bias ( we can also use the others biasing structures)




#### Exercise 5.41

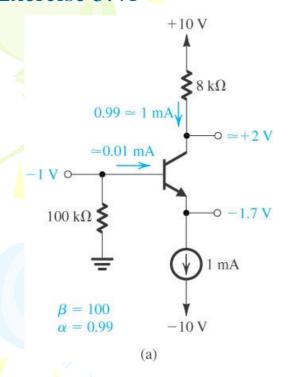


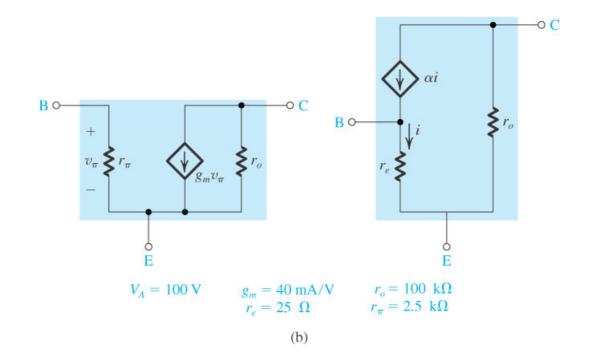


#### Common-Emitter amplifier

#### Small signal CKT

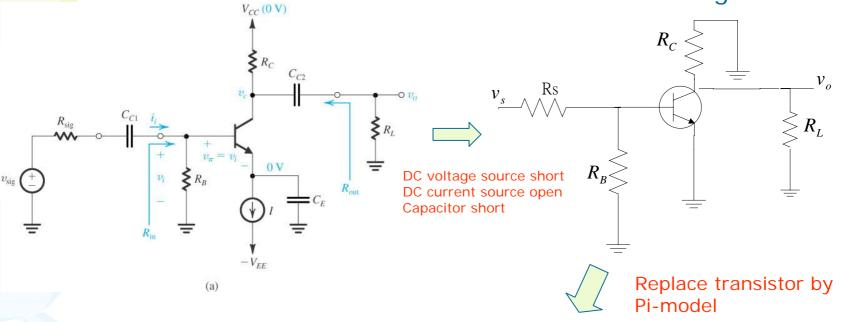

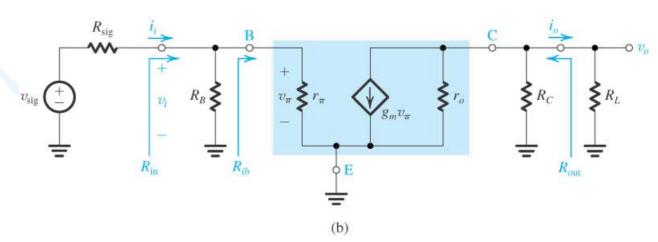

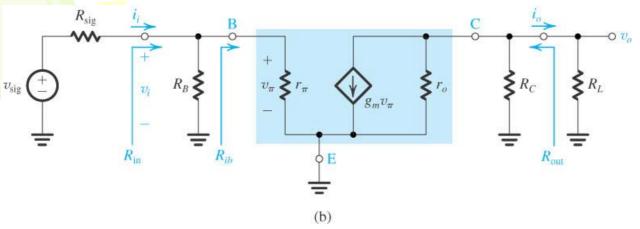

$$R_{in} = \frac{v_i}{i_i} = R_B // r_{\pi}$$

$$R_{ib} = r_{\pi}$$

$$if \quad R_B >> r_{\pi} \rightarrow R_{in} \approx R_{ib} = r_{\pi}$$

$$v_i = v_{signal} \frac{R_{in}}{R_{signal} + R_{in}} \approx v_{signal} \frac{r_{\pi}}{R_{signal} + r_{\pi}}$$

$$v_i = v_{\pi}$$

$$v_o = -g_m v_{\pi} (r_o // R_C // R_L)$$

$$A_v = -g_m (r_o // R_C // R_L)$$

$$R_{out} = R_C // r_o$$

$$G_{v} \equiv \frac{v_{o}}{v_{signal}}$$


$$= \frac{-g_{m}(r_{o} // R_{C} // R_{L})}{R_{signal} + R_{in}} R_{in}$$

$$= \frac{-\beta (R_{C} // R_{L} // r_{o})}{r_{\pi} + R_{signal}}$$


$$i_{os} = -g_{m}v_{\pi}$$


$$A_{is} \equiv \frac{i_{os}}{i} = -g_{m}R_{in}$$

### Common-Emitter amplifier

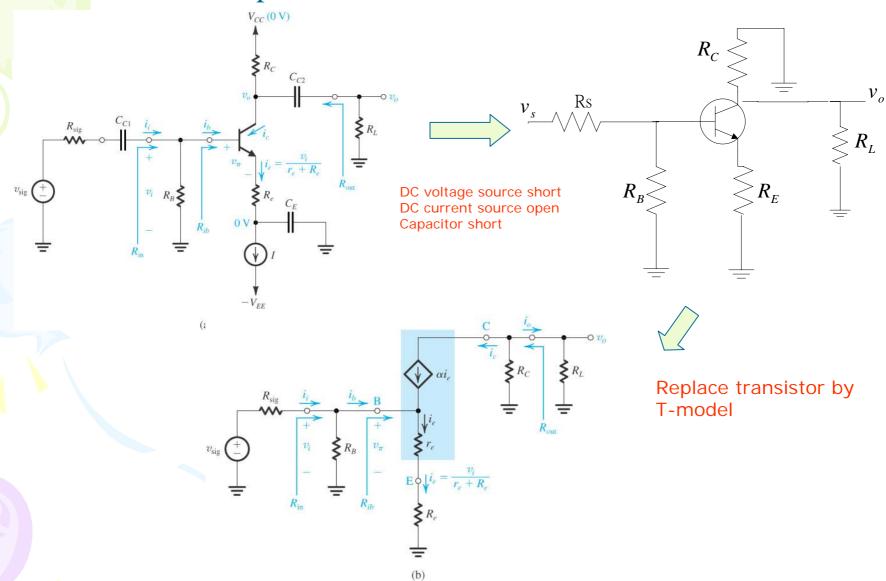


### Common-Base amplifier

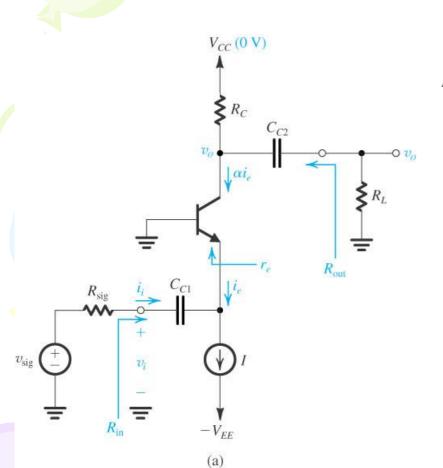

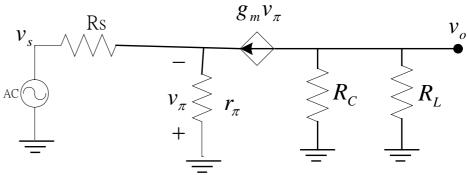



#### $\pi$ Model equivalent Circuit

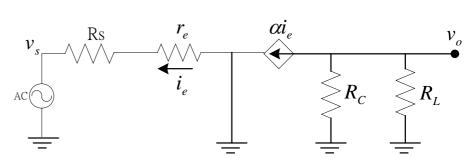



T-Model equivalent Circuit


## Common-collector amplifier

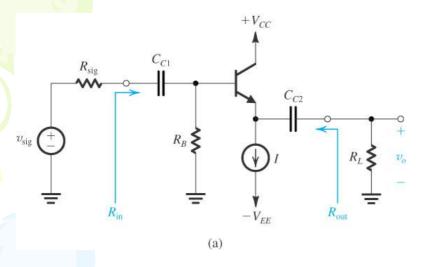


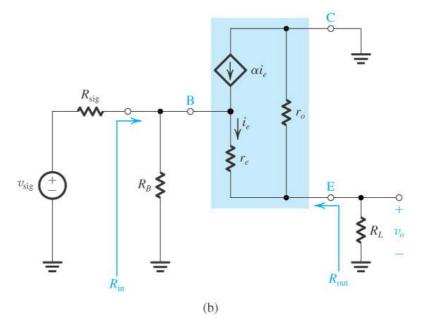

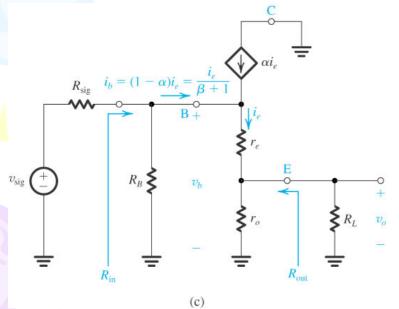

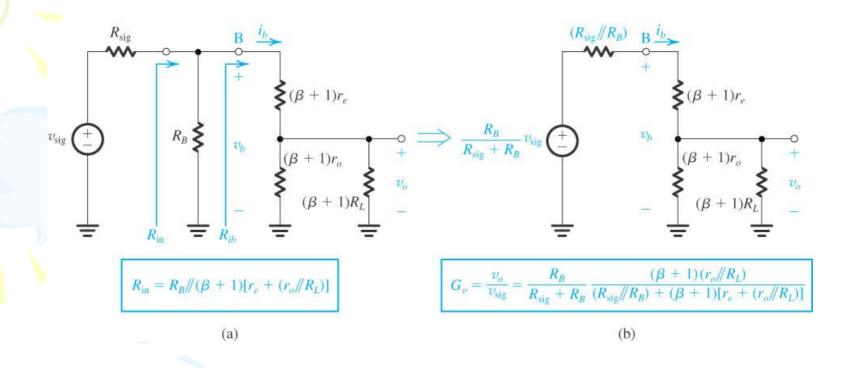

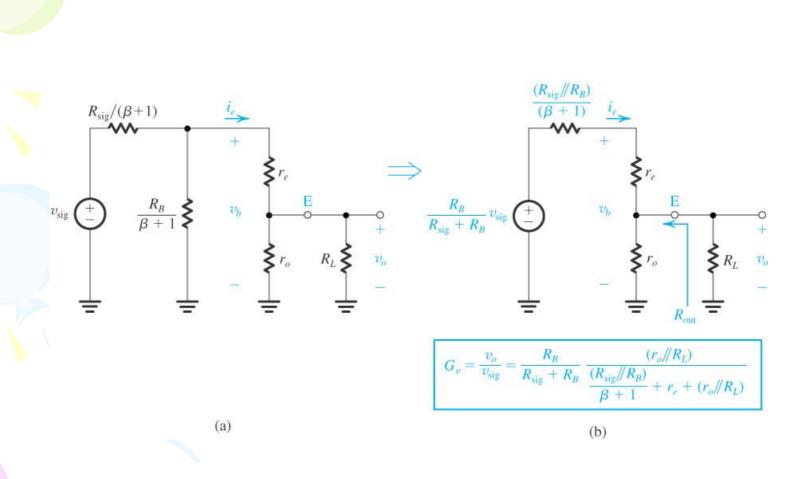

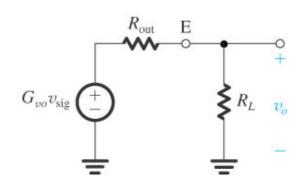


$$G_{vo} = \frac{R_B}{R_{\text{sig}} + R_B} \frac{r_o}{\frac{(R_{\text{sig}} /\!/ R_B)}{(\beta + 1)} + r_e + r_o}$$

$$R_{\text{out}} = r_o /\!\!/ \left(r_e + \frac{R_{\text{sig}} /\!/ R_B}{\beta + 1}\right)$$

## Summary I

#### **Common Emitter**

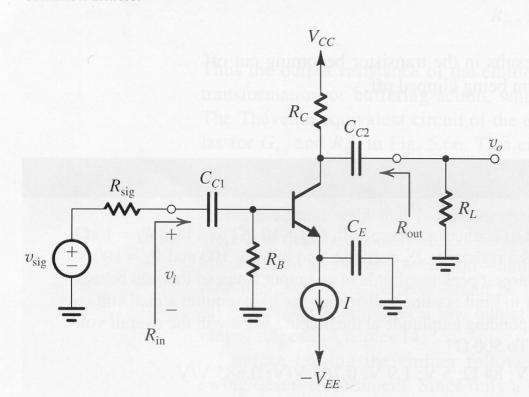

$$R_{\text{in}} = R_B \| r_{\pi} = R_B \| (\beta + 1) r_e$$

$$A_v = -g_m(r_o \| R_C \| R_L)$$
Inverse phase
$$R_{\text{out}} = r_o \| R_C$$


$$G_v = -\frac{(R_B \| r_{\pi})}{(R_B \| r_{\pi}) + R_{\text{sig}}} g_m(r_o \| R_C \| R_L)$$

$$\cong -\frac{\beta(r_o \| R_C \| R_L)}{r_{\pi} + R_{\text{sig}}}$$

$$A_{is} = -g_m R_{\text{in}} \cong -\beta$$

$R_i$	middle	$A_{_{\scriptscriptstyle \mathcal{V}}}$	High(>1)
$R_o$	high	$A_{i}$	High(>1)
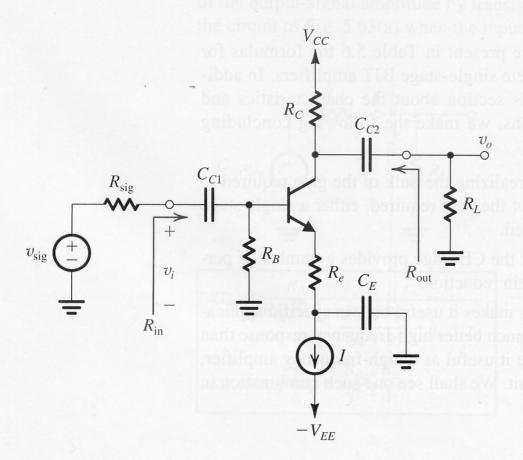
#### **Common Emitter with Emitter Resistance**



Neglecting  $r_o$ :

$$R_{\text{in}} = R_B \parallel (\beta + 1)(r_e + R_e)$$


$$A_v = -\frac{\alpha(R_C \parallel R_L)}{r_e + R_e} \cong \frac{-g_m(R_C \parallel R_L)}{1 + g_m R_e}$$

$$R_{\text{out}} = R_C$$

$$G_v \cong -\frac{\beta(R_C \parallel R_L)}{R_{\text{sig}} + (\beta + 1)(r_e + R_e)}$$

$$\frac{v_\pi}{v_i} \cong \frac{1}{1 + g_m R_e}$$

#### **Common Base**

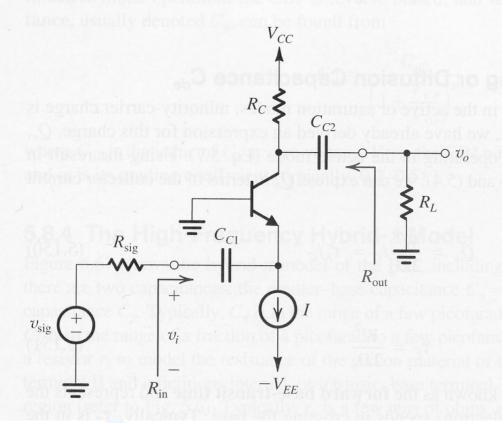

Neglecting  $r_o$ :

$$R_{\text{in}} = r_e$$

$$A_v = g_m(R_C \parallel R_L)$$


$$R_{\text{out}} = R_C$$

$$G_v = \frac{\alpha(R_C \parallel R_L)}{R_{\text{sig}} + r_e}$$

$$A_{is} \cong \alpha$$

$R_{i}$	low	$A_{_{\scriptscriptstyle \mathcal{V}}}$	Low (<1)
$R_o$	highest	$A_{i}$	Low (<=1)
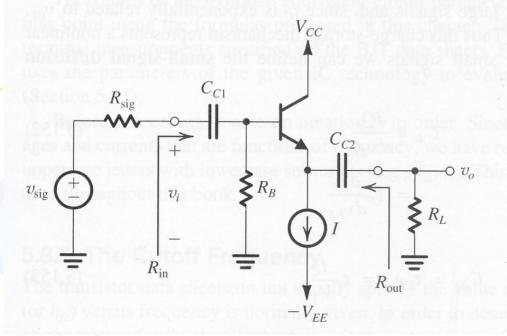
#### Common Collector or Emitter Follower



$$R_{\text{in}} = R_B \| (\beta + 1)[r_e + (r_o \| R_L)]$$

$$A_v = \frac{(r_o \| R_L)}{(r_o \| R_L) + r_e}$$


$$R_{\text{out}} = r_o \| \left[ r_e + \frac{R_{\text{sig}} \| R_B}{\beta + 1} \right]$$

$$G_v = \frac{R_B}{R_B + R_{\text{sig}}} \frac{(r_o \| R_L)}{\frac{R_{\text{sig}} \| R_B}{\beta + 1} + r_e + (r_o \| R_L)}$$


$$A_{is} \cong \beta + 1$$

$R_{i}$	high	$A_{_{\scriptscriptstyle \mathcal{V}}}$	Low (<=1)
$R_o$	low	$A_{i}$	Highest (>1)

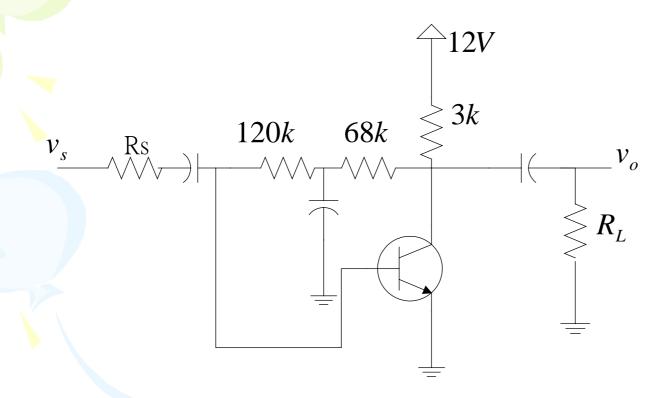
#### Common-Emitter amplifier (with collector feedback bias)


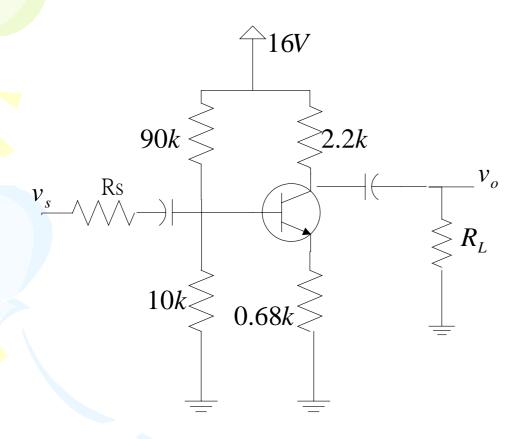
### Common-Emitter amplifier with emitter resistance (by using self-bias)


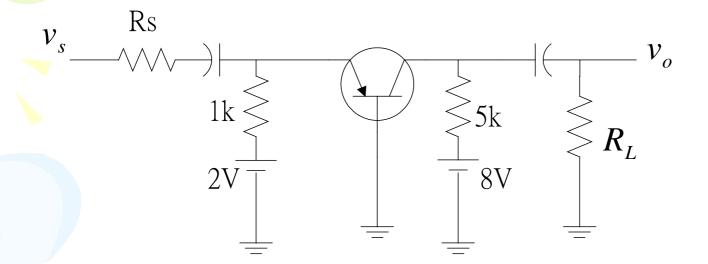
## Common-Base amplifier (by using self-bias)



## Common-Collector amplifier (by using self-bias)

