




Lecture 14

Feedback

topics


- The series-shunt feedback
- The series-series feedback
- The shunt-shunt feedback
- The shunt-series feedback

Two port networks

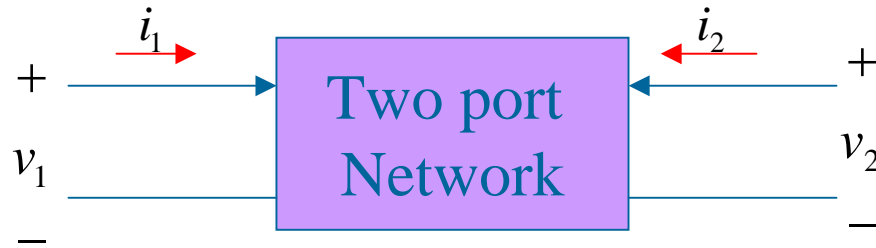

Type I: Impedance z-parameters

$$\begin{aligned} v_1 &= f(i_1, i_2) = z_{11}i_1 + z_{12}i_2 \\ v_2 &= f(i_1, i_2) = z_{21}i_1 + z_{22}i_2 \end{aligned} \quad \Rightarrow \quad \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

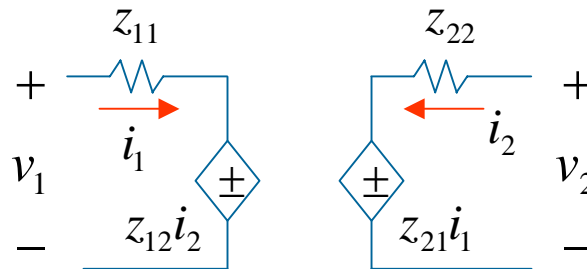


Type II: Admittance y-parameters

$$i_1 = f(v_1, v_2) = y_{11}v_1 + y_{12}v_2$$

$$i_2 = f(v_1, v_2) = y_{21}v_1 + y_{22}v_2$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

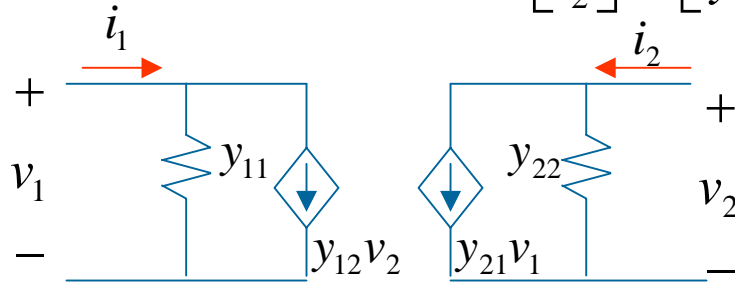


Type III: hybrid h-parameters

$$v_1 = f(i_1, v_2) = h_{11}i_1 + h_{12}v_2$$

$$i_2 = f(i_1, v_2) = h_{21}i_1 + h_{22}v_2$$

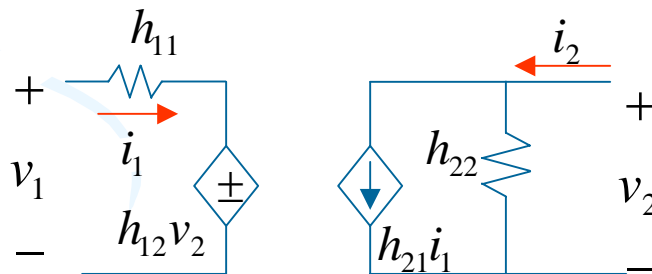
$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$



$$\begin{bmatrix} v_{be} \\ i_c \end{bmatrix} = \begin{bmatrix} h_{ie} & h_{re} \\ h_{fe} & h_{oe} \end{bmatrix} \begin{bmatrix} i_b \\ v_{ce} \end{bmatrix}$$

Type IV: Inverse-hybrid g-parameters

$$\begin{aligned} i_1 &= f(v_1, i_2) = g_{11}v_1 + g_{12}i_2 \\ v_2 &= f(v_1, i_2) = g_{21}v_1 + g_{22}i_2 \end{aligned} \quad \Rightarrow \quad \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$

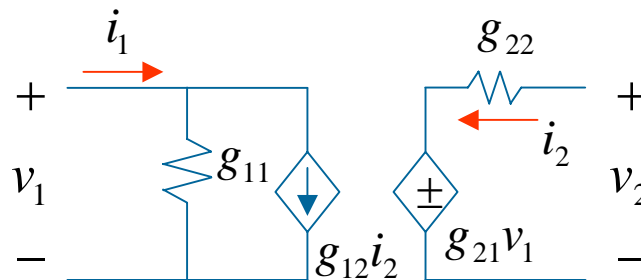

Type V: transmission ABCD parameters


$$\begin{aligned} v_1 &= f(v_2, -i_2) = Av_2 + B(-i_2) \\ i_1 &= f(v_2, -i_2) = Cv_2 + D(-i_2) \end{aligned} \quad \Rightarrow \quad \begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

Type VI: Inverse transmission parameters


$$\begin{aligned} v_2 &= f(v_1, -i_1) = A'v_1 + B'(-i_1) \\ i_2 &= g(v_1, -i_1) = C'v_1 + D'(-i_1) \end{aligned} \Rightarrow \begin{bmatrix} v_2 \\ i_2 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} v_1 \\ -i_1 \end{bmatrix}$$

Two port Network combination:

I. Cascade : ABCD parameters

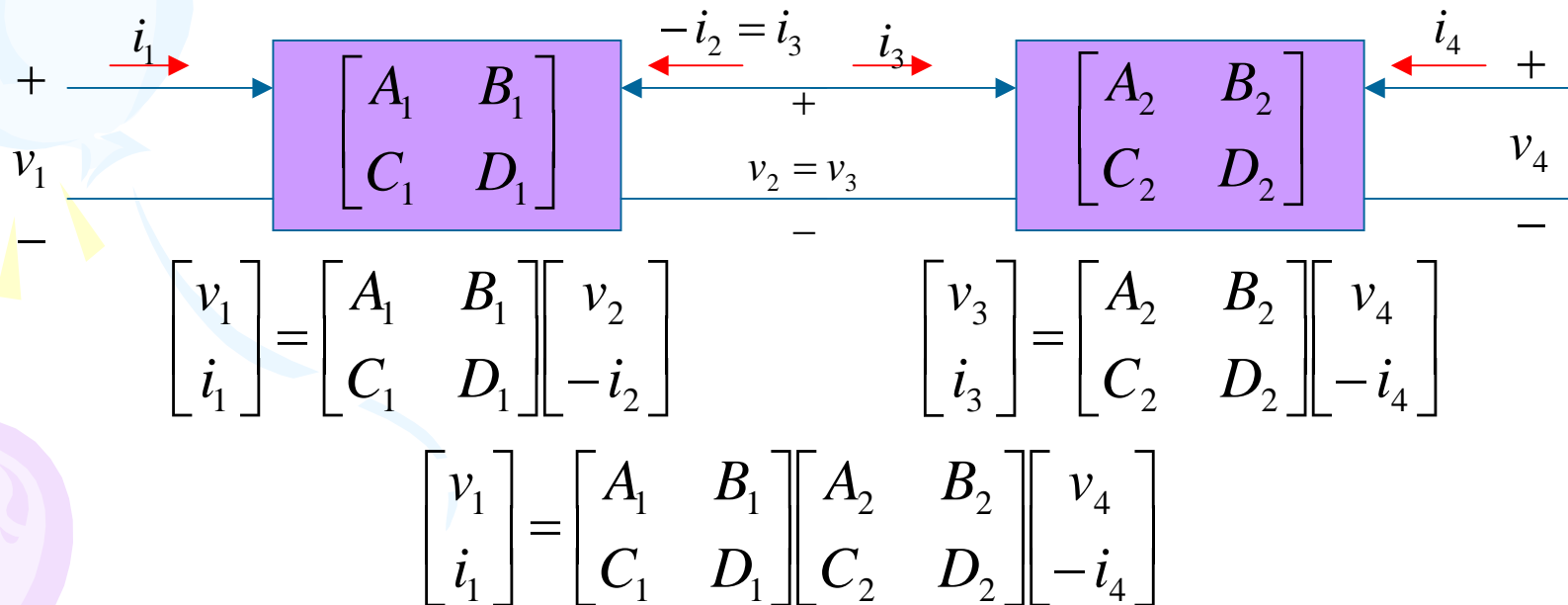

II: series-shunt

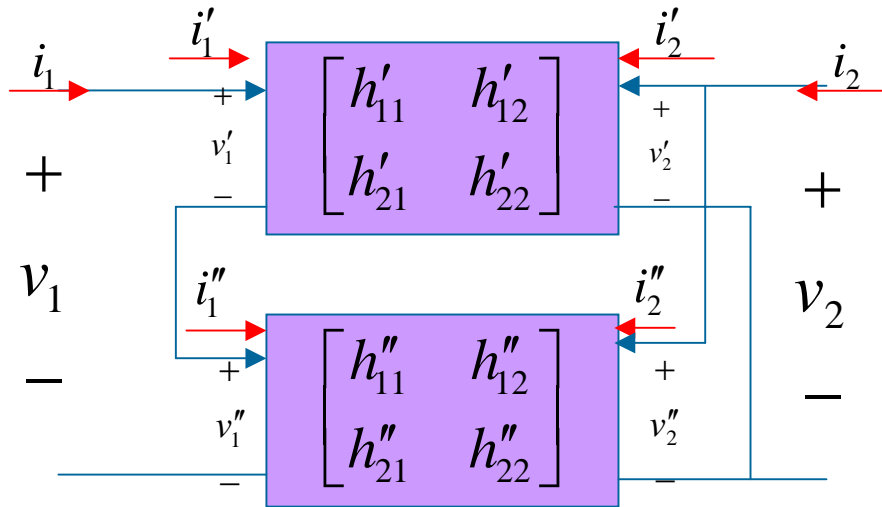

$$i_1 = i_1' = i_1''$$

$$v_1 = v_1' + v_1''$$


$$i_2 = i_2' + i_2''$$

$$v_2 = v_2' = v_2''$$

$$\begin{bmatrix} v_1' \\ i_2' \end{bmatrix} = \begin{bmatrix} h'_{11} & h'_{12} \\ h'_{21} & h'_{22} \end{bmatrix} \begin{bmatrix} i_1' \\ v_2' \end{bmatrix} \quad \begin{bmatrix} v_1'' \\ i_2'' \end{bmatrix} = \begin{bmatrix} h''_{11} & h''_{12} \\ h''_{21} & h''_{22} \end{bmatrix} \begin{bmatrix} i_1'' \\ v_2'' \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_1' \\ i_2' \end{bmatrix} + \begin{bmatrix} v_1'' \\ i_2'' \end{bmatrix} = \left\{ \begin{bmatrix} h'_{11} & h'_{12} \\ h'_{21} & h'_{22} \end{bmatrix} + \begin{bmatrix} h''_{11} & h''_{12} \\ h''_{21} & h''_{22} \end{bmatrix} \right\} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

Ex:

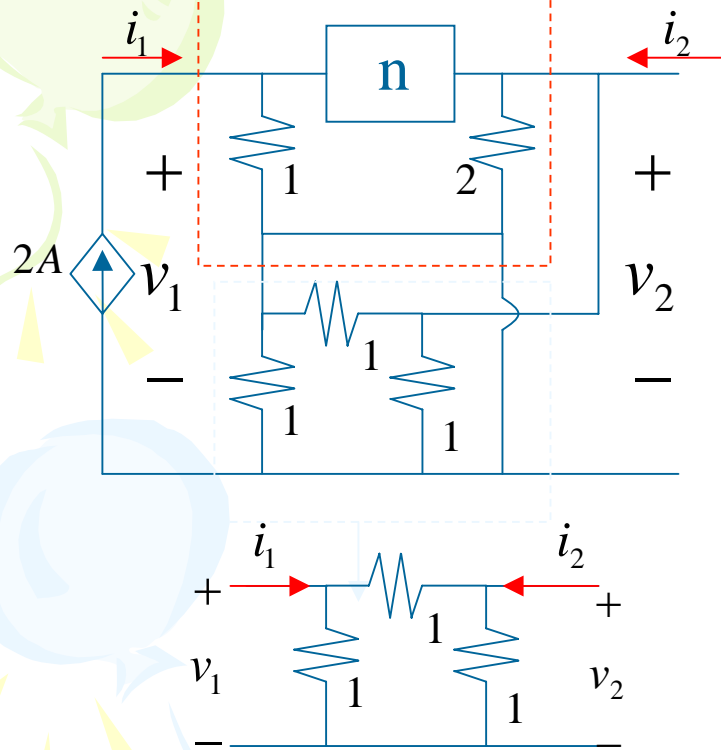

Find $v_2 = ?$

$$h = \begin{bmatrix} 2 & 1 \\ 1 & 3 \end{bmatrix}$$

$$h_{total} = \begin{bmatrix} \frac{5}{2} & \frac{3}{2} \\ \frac{1}{2} & \frac{9}{2} \end{bmatrix}$$

$$\begin{aligned} v_1 &= \frac{5}{2}i_1 + \frac{3}{2}v_2 \\ i_2 &= \frac{1}{2}i_1 + \frac{9}{2}v_2 \end{aligned} \rightarrow \begin{aligned} i_1 &= 2, i_2 = 0 \\ v_2 &= -\frac{2}{9} \end{aligned}$$


$$i_1 = \frac{v_1}{1} + \frac{v_1 - v_2}{1} \Rightarrow v_1 = \frac{1}{2}i_1 + \frac{1}{2}v_2$$

$$i_2 = \frac{v_2}{1} + \frac{v_2 - v_1}{1} \Rightarrow i_2 = -v_1 + 2v_2$$

$$i_2 = -v_1 + 2v_2 = -\frac{1}{2}i_1 + \frac{3}{2}v_2$$

$$\Rightarrow h = \begin{bmatrix} \frac{1}{2} & \frac{1}{2} \\ -\frac{1}{2} & \frac{3}{2} \end{bmatrix}$$

III: series-series

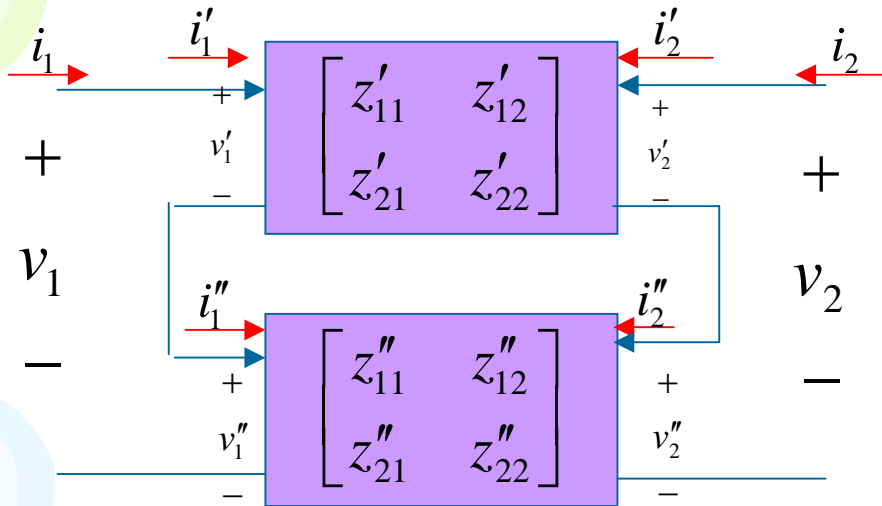

$$i_1 = i'_1 = i''_1$$

$$v_1 = v'_1 + v''_1$$

$$i_2 = i'_2 = i''_2$$


$$v_2 = v'_2 + v''_2$$

$$\begin{bmatrix} v'_1 \\ v'_2 \end{bmatrix} = \begin{bmatrix} z'_{11} & z'_{12} \\ z'_{21} & z'_{22} \end{bmatrix} \begin{bmatrix} i'_1 \\ i'_2 \end{bmatrix}$$

$$\begin{bmatrix} v''_1 \\ v''_2 \end{bmatrix} = \begin{bmatrix} z''_{11} & z''_{12} \\ z''_{21} & z''_{22} \end{bmatrix} \begin{bmatrix} i''_1 \\ i''_2 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} v'_1 \\ v'_2 \end{bmatrix} + \begin{bmatrix} v''_1 \\ v''_2 \end{bmatrix} = \left\{ \begin{bmatrix} z'_{11} & z'_{12} \\ z'_{21} & z'_{22} \end{bmatrix} + \begin{bmatrix} z''_{11} & z''_{12} \\ z''_{21} & z''_{22} \end{bmatrix} \right\} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

IV: Shunt-shunt

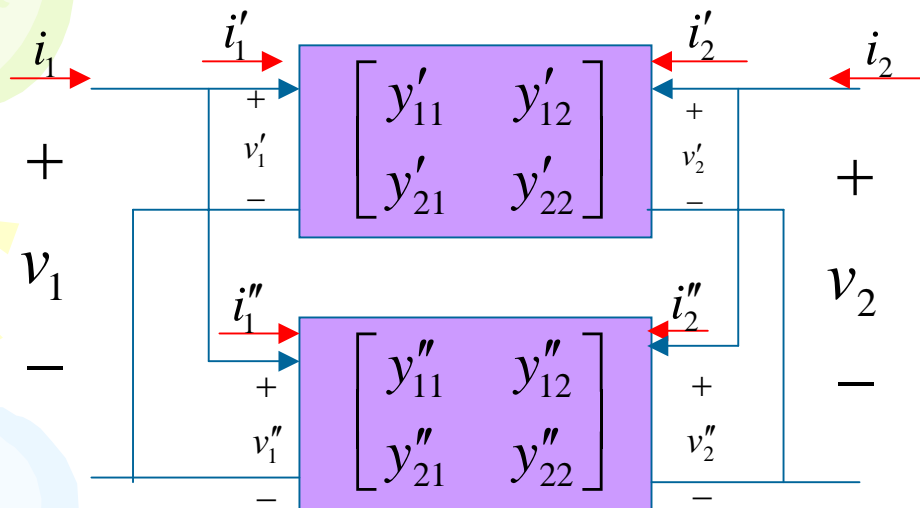

$$i_1 = i_1' + i_1''$$

$$v_1 = v_1' = v_1''$$

$$i_2 = i_2' + i_2''$$


$$v_2 = v_2' = v_2''$$

$$\begin{bmatrix} i_1' \\ i_2' \end{bmatrix} = \begin{bmatrix} y'_{11} & y'_{12} \\ y'_{21} & y'_{22} \end{bmatrix} \begin{bmatrix} v_1' \\ v_2' \end{bmatrix}$$

$$\begin{bmatrix} i_1'' \\ i_2'' \end{bmatrix} = \begin{bmatrix} y''_{11} & y''_{12} \\ y''_{21} & y''_{22} \end{bmatrix} \begin{bmatrix} v_1'' \\ v_2'' \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} i_1' \\ i_2' \end{bmatrix} + \begin{bmatrix} i_1'' \\ i_2'' \end{bmatrix} = \left\{ \begin{bmatrix} y'_{11} & y'_{12} \\ y'_{21} & y'_{22} \end{bmatrix} + \begin{bmatrix} y''_{11} & y''_{12} \\ y''_{21} & y''_{22} \end{bmatrix} \right\} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

V: shunt-series

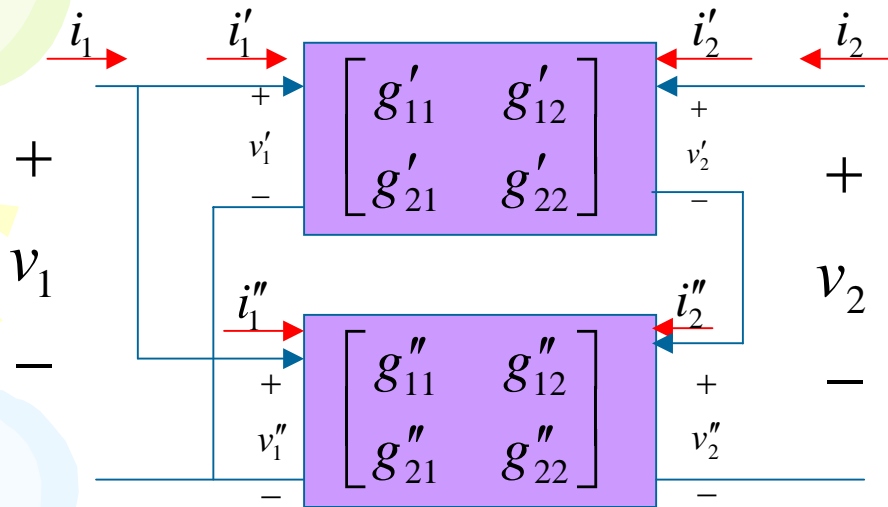

$$i_1 = i_1' + i_1''$$

$$v_1 = v_1' = v_1''$$

$$i_2 = i_2' = i_2''$$


$$v_2 = v_2' + v_2''$$

$$\begin{bmatrix} i_1' \\ v_2' \end{bmatrix} = \begin{bmatrix} g'_{11} & g'_{12} \\ g'_{21} & g'_{22} \end{bmatrix} \begin{bmatrix} v_1' \\ i_2' \end{bmatrix}$$

$$\begin{bmatrix} i_1'' \\ v_2'' \end{bmatrix} = \begin{bmatrix} g''_{11} & g''_{12} \\ g''_{21} & g''_{22} \end{bmatrix} \begin{bmatrix} v_1'' \\ i_2'' \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i_1' \\ v_2' \end{bmatrix} + \begin{bmatrix} i_1'' \\ v_2'' \end{bmatrix} = \left\{ \begin{bmatrix} g'_{11} & g'_{12} \\ g'_{21} & g'_{22} \end{bmatrix} + \begin{bmatrix} g''_{11} & g''_{12} \\ g''_{21} & g''_{22} \end{bmatrix} \right\} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$

General feedback structure

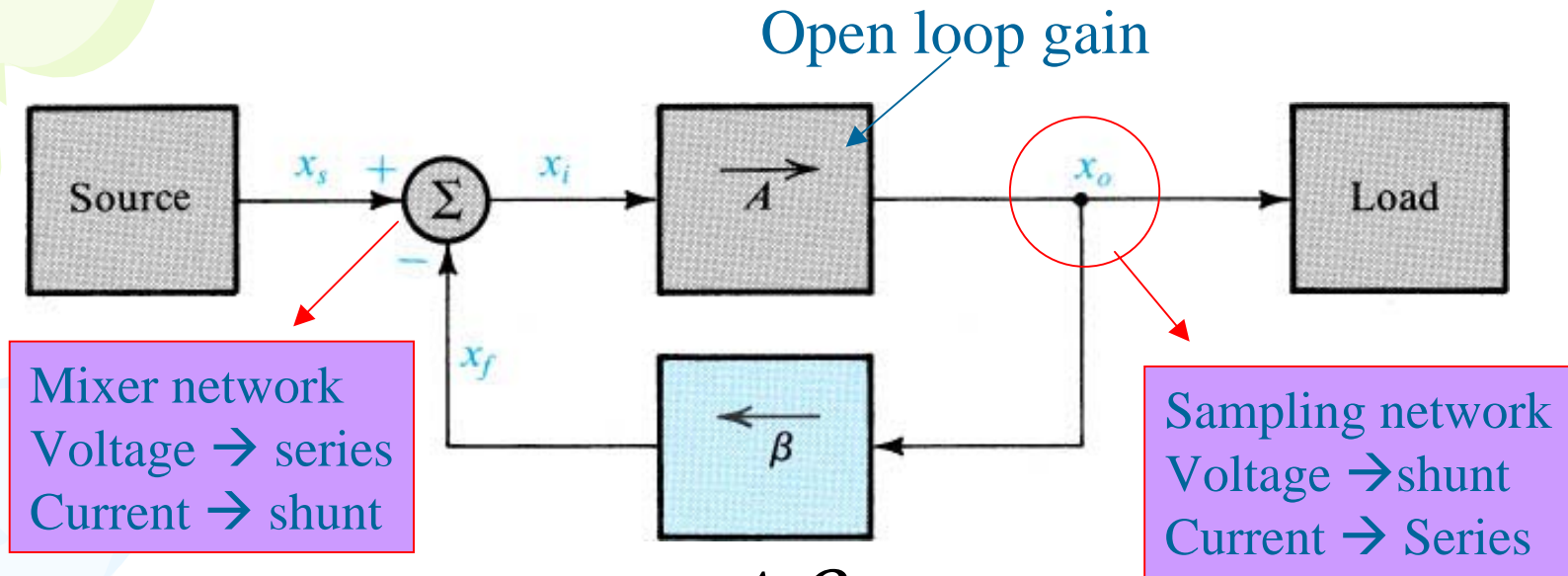

$$x_o = Ax_i$$

$$x_f = \beta x_o$$

$$x_i = x_s - x_f$$

$$A_f \equiv \frac{x_o}{x_s} = \frac{A}{1 + A\beta}$$

Closed-loop gain

$A\beta \rightarrow$ Loop gain



Negative feedback properties

- Gain desensitivity
- Bandwidth extension
- Noise reduction
- Nonlinear distortion reduction

1. Gain desensitivity

$$\frac{dA_f}{A_f} < \frac{dA}{A}$$

$$A_f \equiv \frac{x_o}{x_s} = \frac{A}{1 + A\beta}$$

$$dA_f = \frac{dA}{(1 + A\beta)^2}$$

$$\frac{dA_f}{A_f} = \frac{1}{1 + A\beta} \frac{dA}{A}$$

2. Bandwidth extension

$$BW = \omega_{Hf} - \omega_{Lf}$$

$$A(s) = \frac{A_M \omega_H}{\omega_H + s} = \frac{A_M}{1 + s / \omega_H}$$

$$A_f(s) = \frac{A(s)}{1 + \beta A(s)} = \frac{A_M / (1 + \beta A_M)}{1 + s / \omega_H (1 + \beta A_M)}$$

$$\omega_{Hf} = \omega_H (1 + \beta A_M)$$

$$A(s) = \frac{A_M s}{\omega_L + s} = \frac{A_M}{1 + \omega_L / s}$$


$$A_f(s) = \frac{A(s)}{1 + \beta A(s)}$$

$$\omega_{Lf} = \omega_L / (1 + \beta A_M)$$

3.Noise reduction


$$SNR = \frac{S}{N}$$

(*Signal* to Noise Ratio)

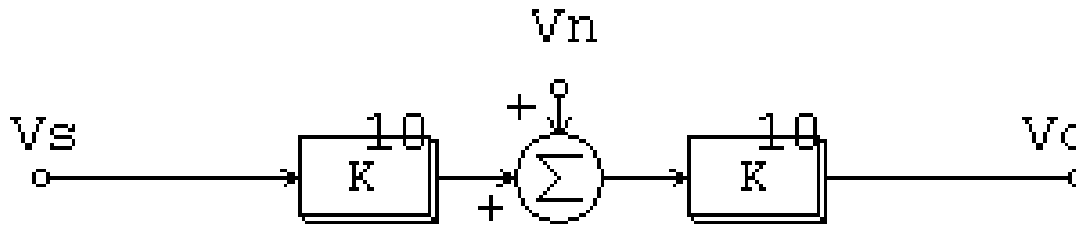

$$V_o = (10V_s + V_n)10$$

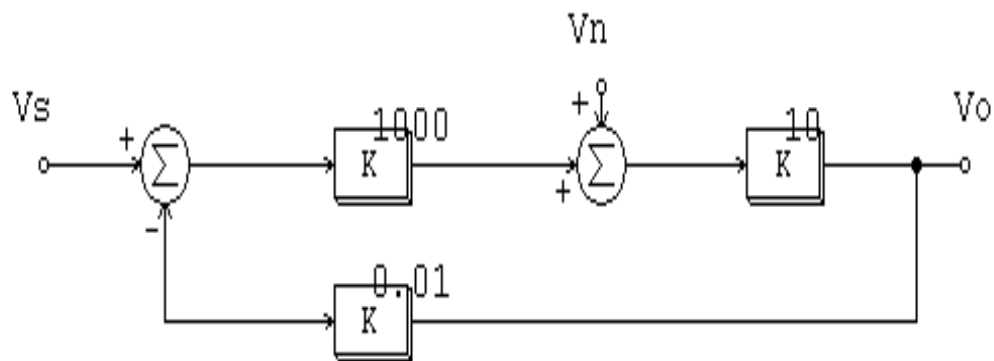
$$\frac{S}{N} = \frac{100V_s}{10V_n} = 10 \frac{S}{N}$$



$$V_o = \frac{10}{1+100} V_n + \frac{10000}{1+100} V_s$$

$$= 0.1 V_n + 100 V_s$$

$$\frac{S}{N} = 1000 \frac{S}{N}$$

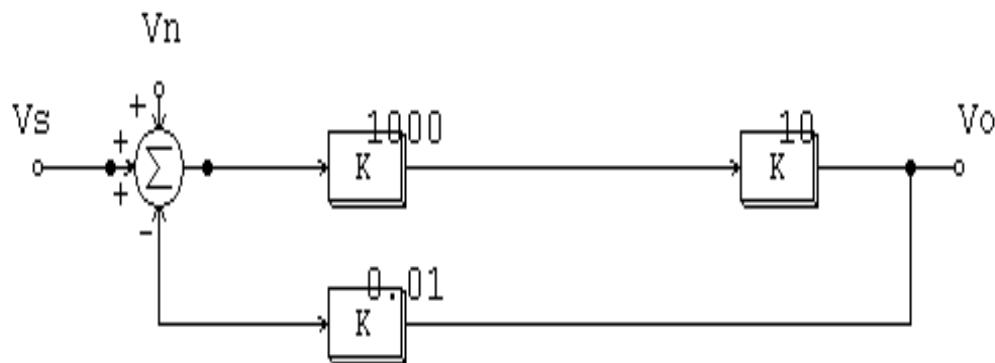

$$V_o = 10000 (V_s - 0.01 V_o + V_n)$$

$$\Rightarrow V_o = 100 V_s + 100 V_n$$

$$\frac{S}{N} = 1 \times \frac{S}{N}$$

4. Nonlinear distortion reduction


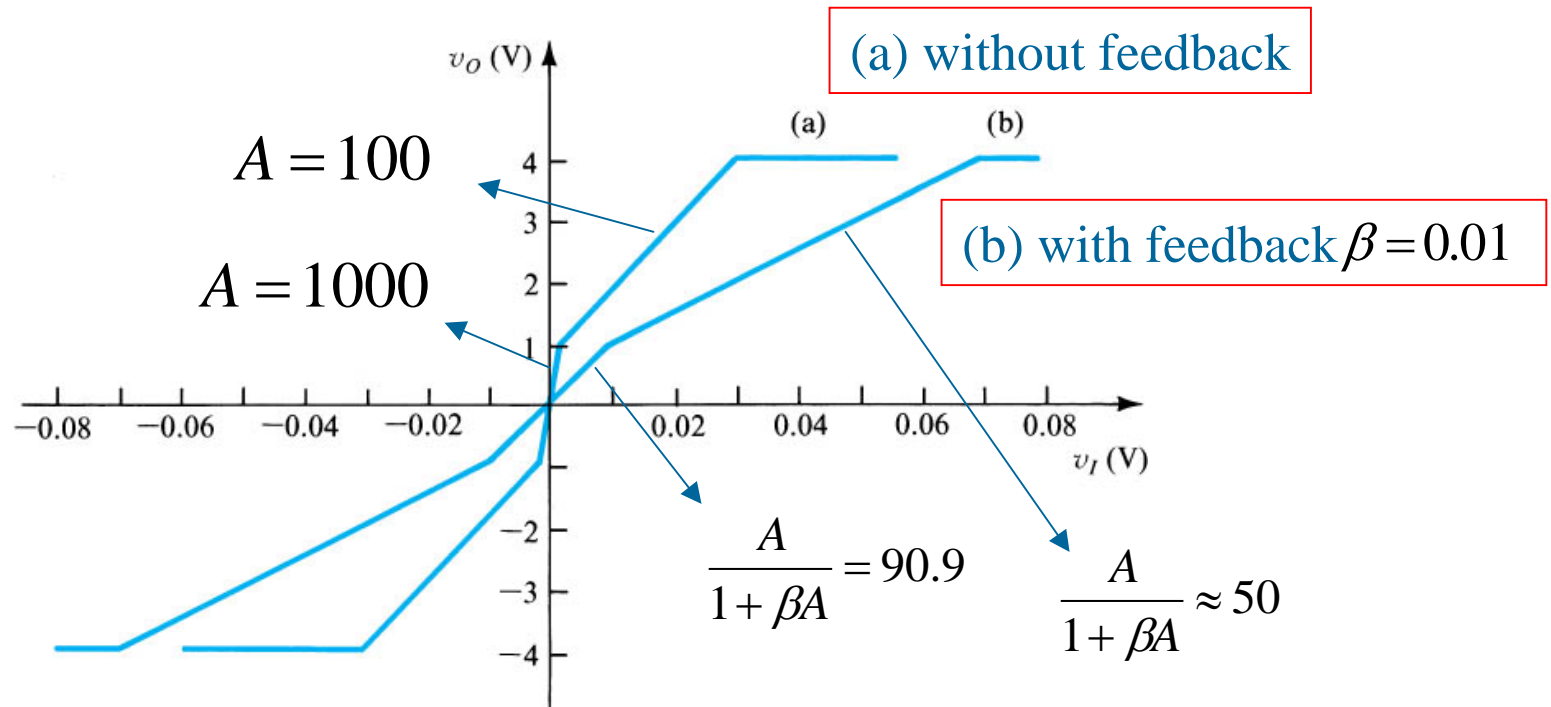





Figure 8.3 Illustrating the application of negative feedback to reduce the nonlinear distortion in amplifiers. Curve (a) shows the amplifier transfer characteristic without feedback. Curve (b) shows the characteristic with negative feedback ($\beta = 0.01$) applied.

Feedback Topology



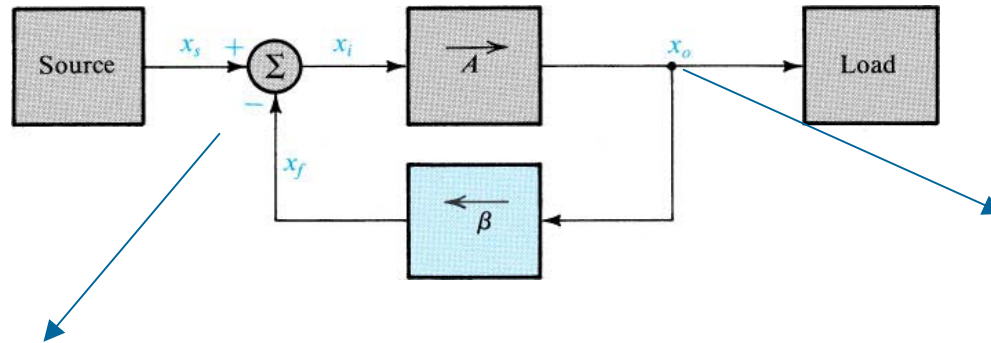






Sampling

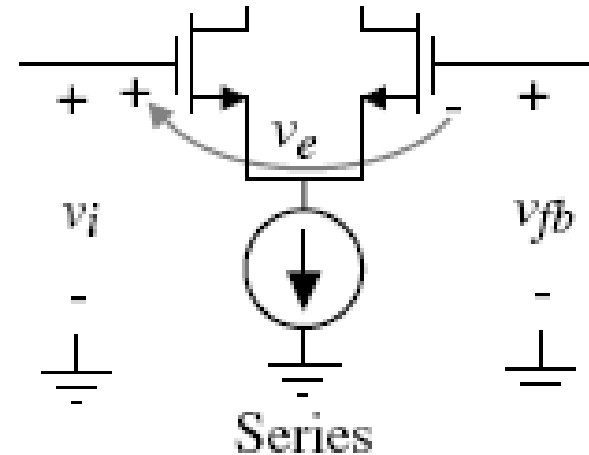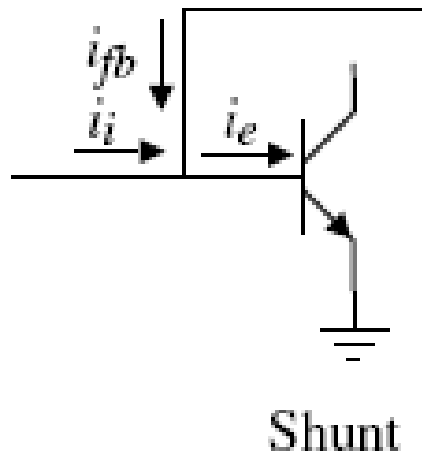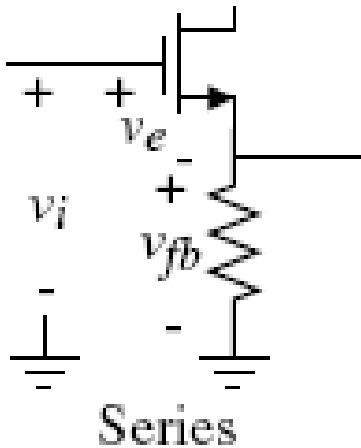
Mixer network: Voltage \rightarrow series Current \rightarrow shunt



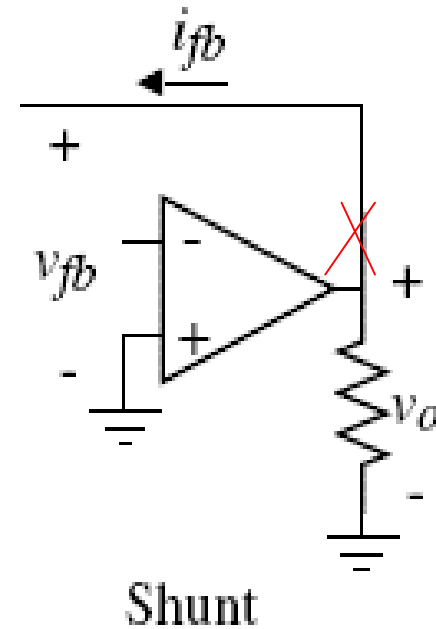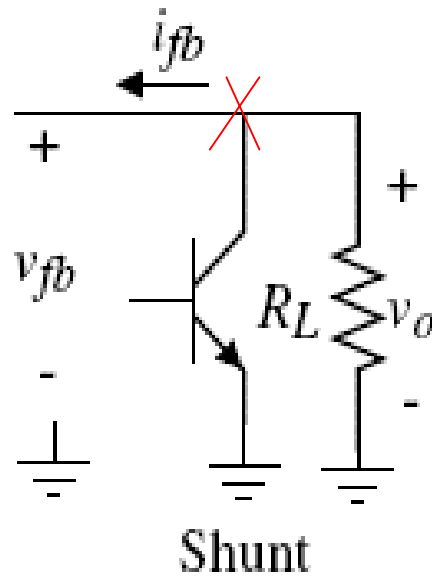
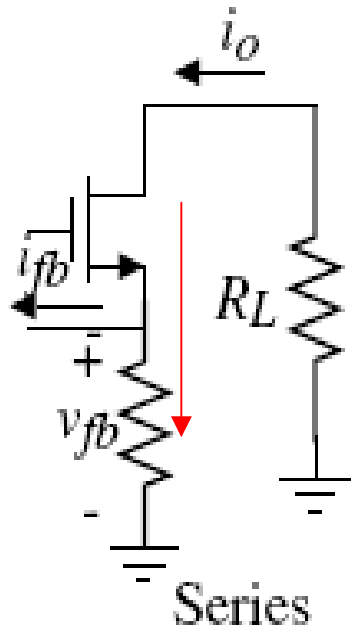
Sampling network : Voltage \rightarrow shunt Current \rightarrow Series




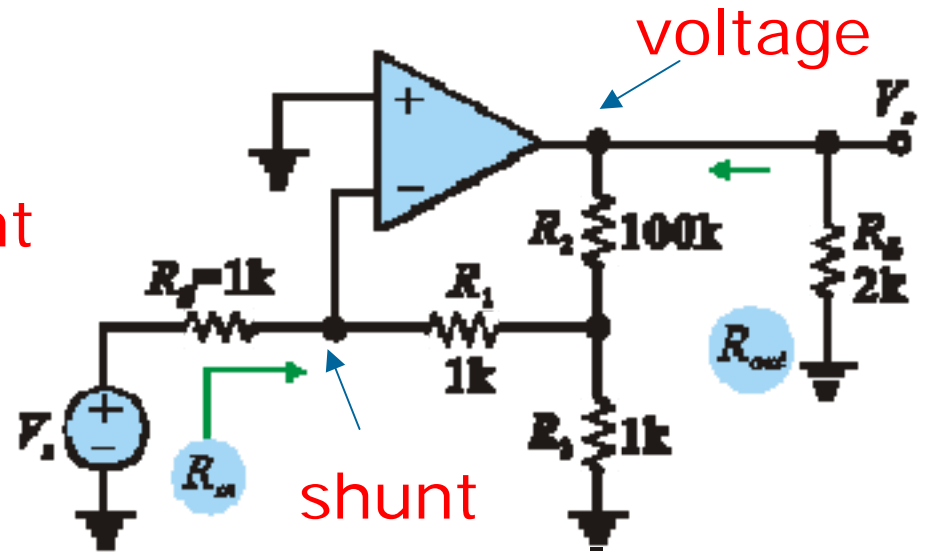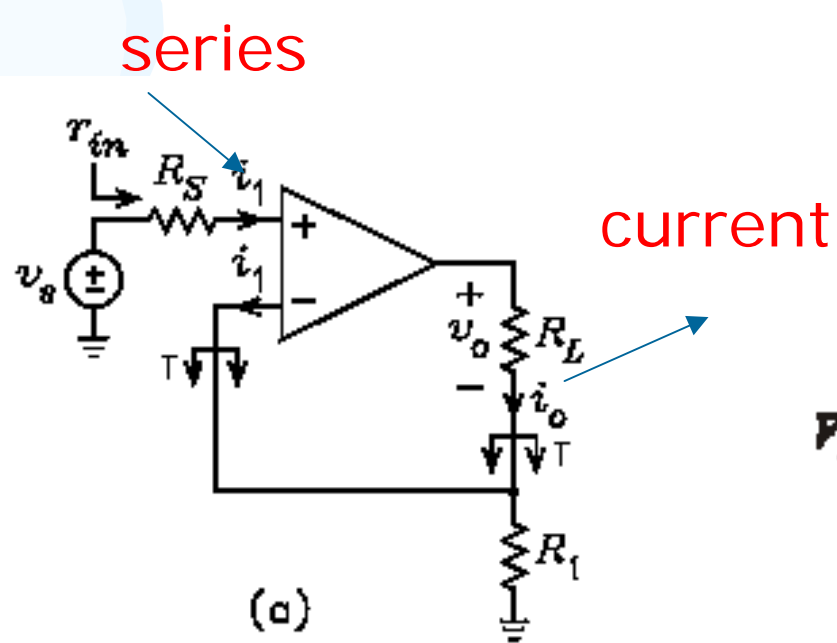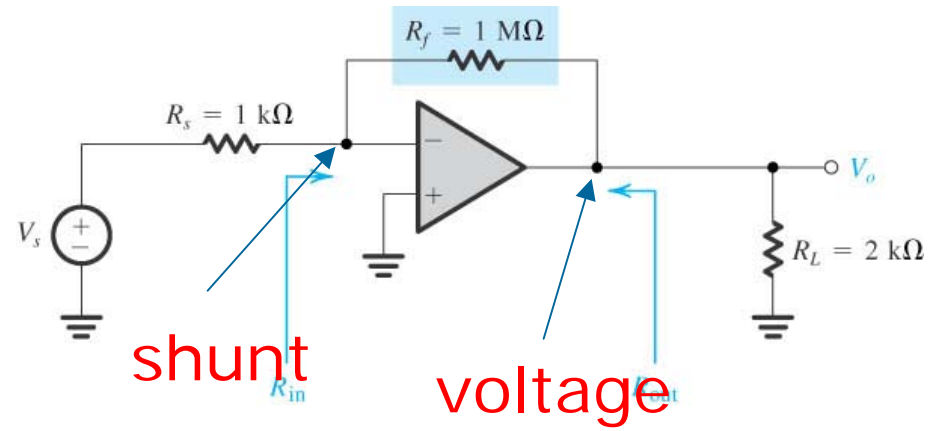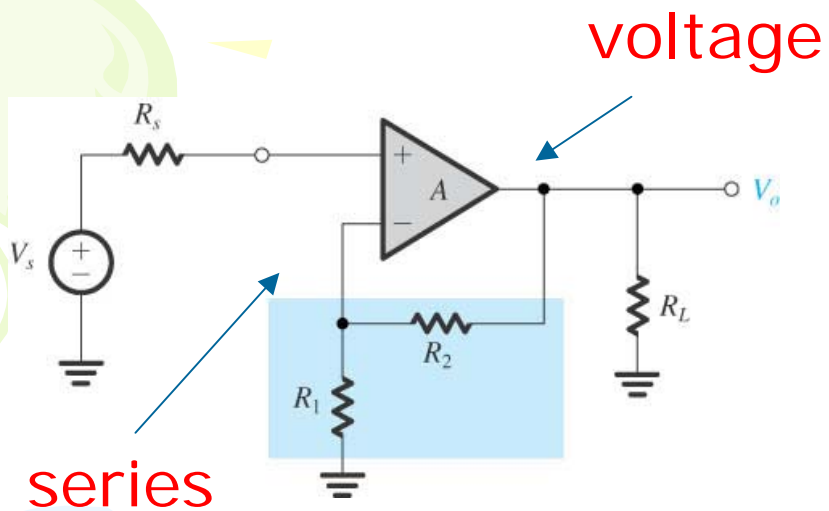

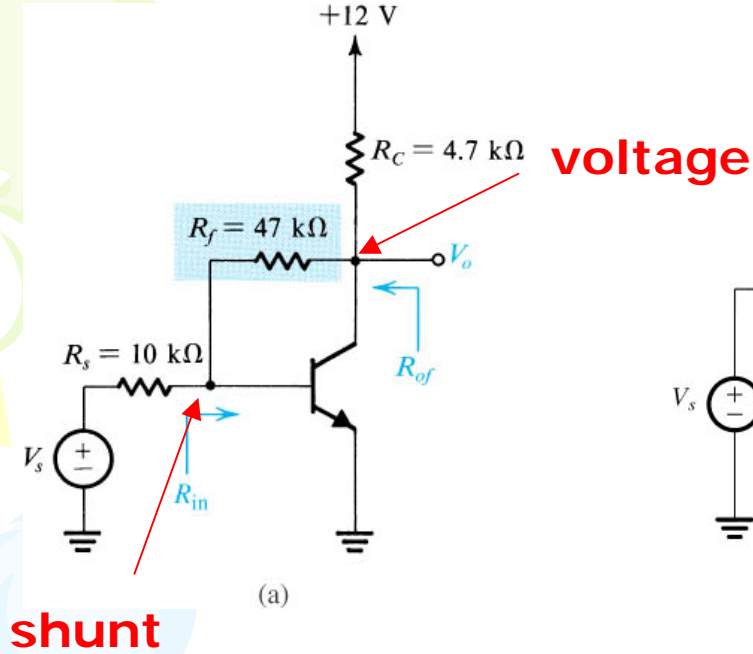



(a)

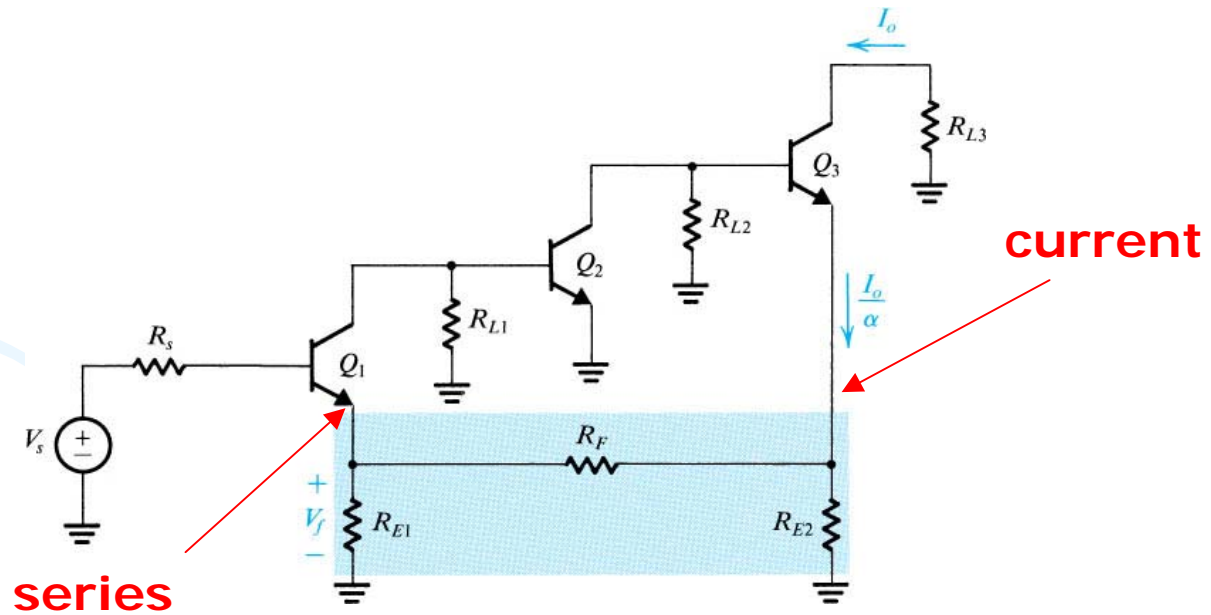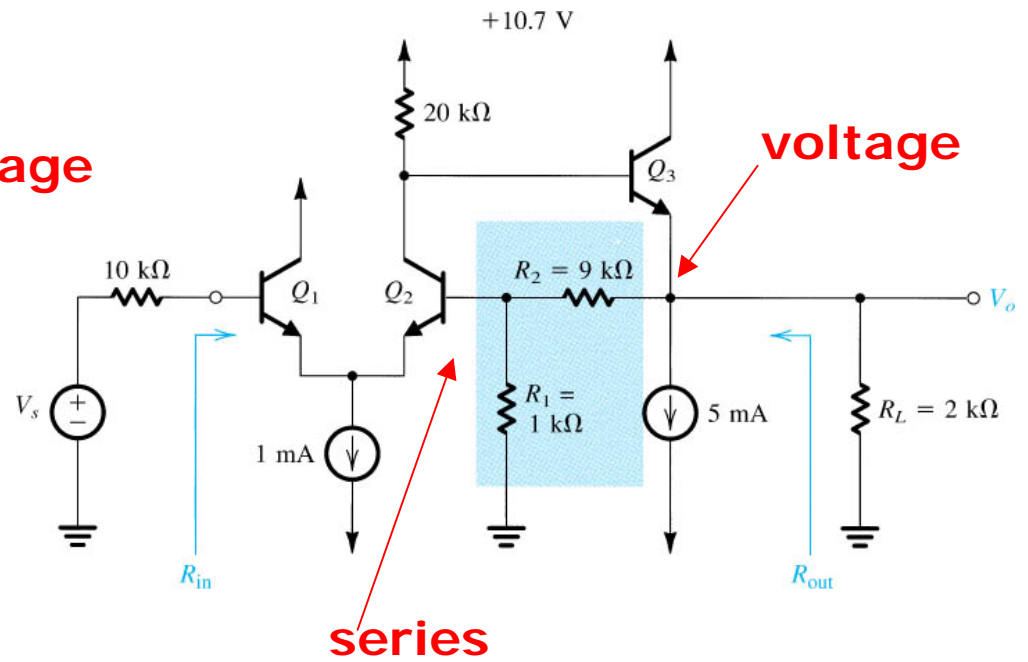

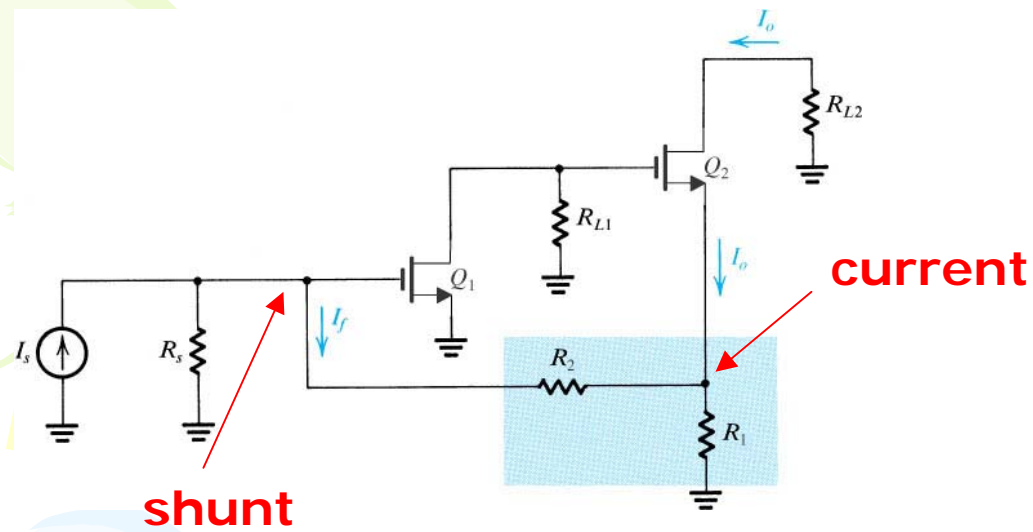



Shunt series

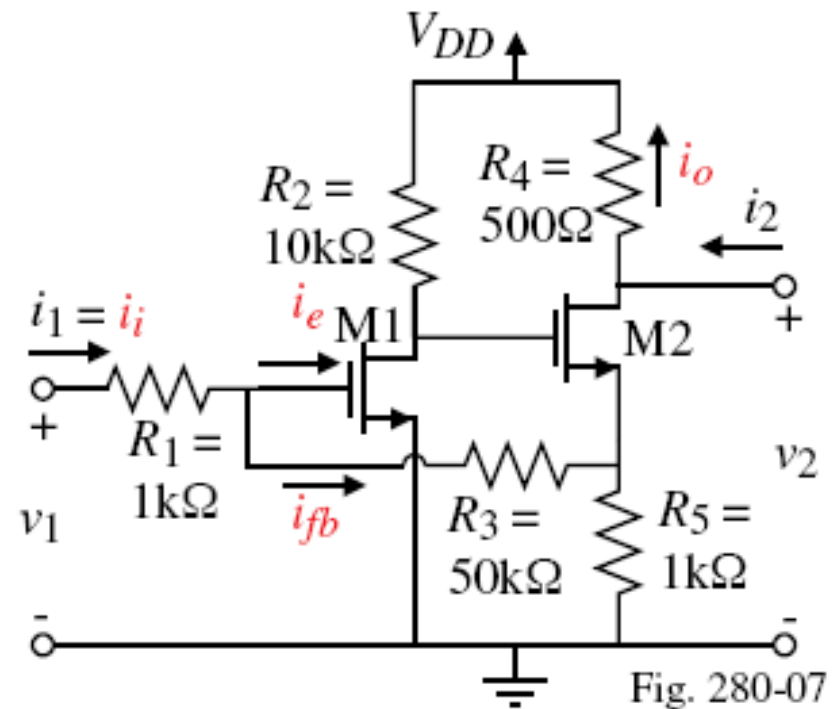

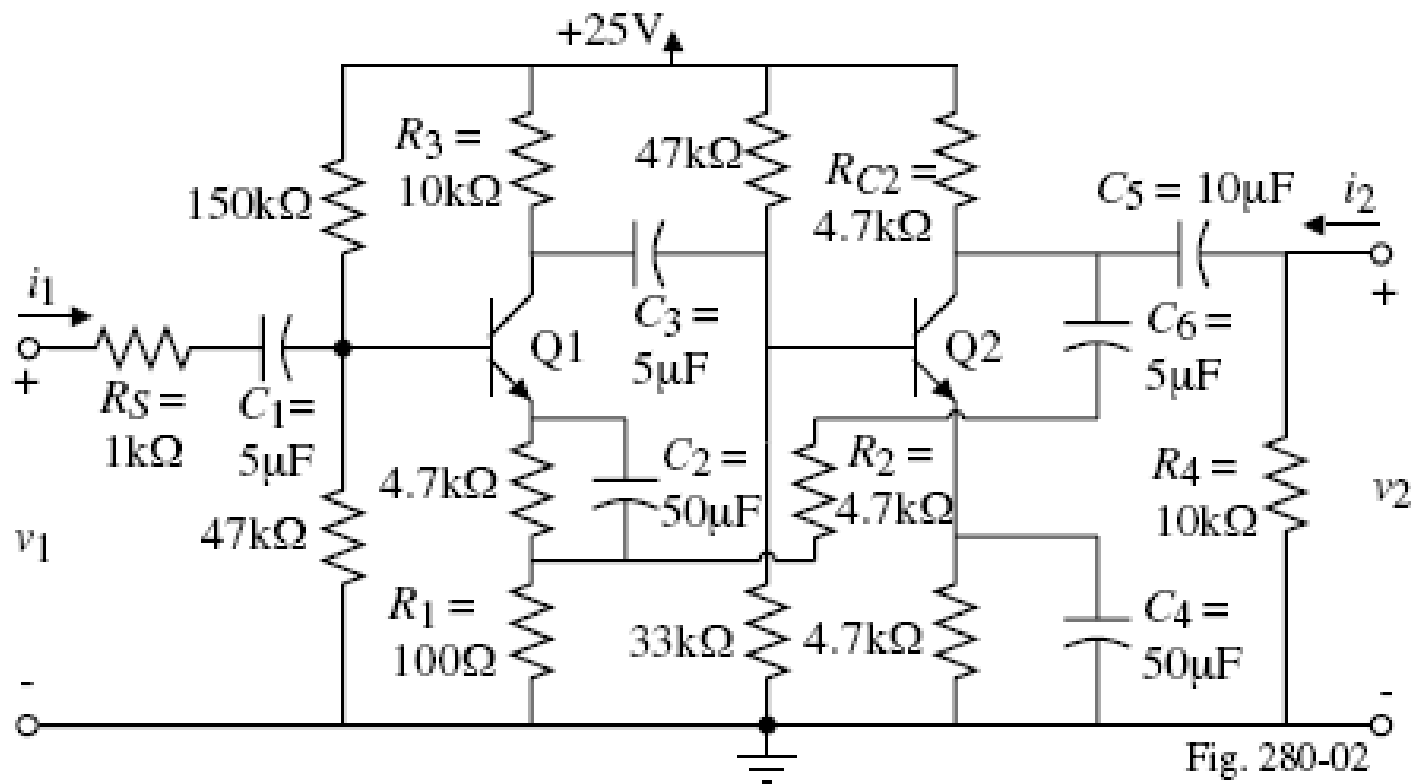


Series- shunt

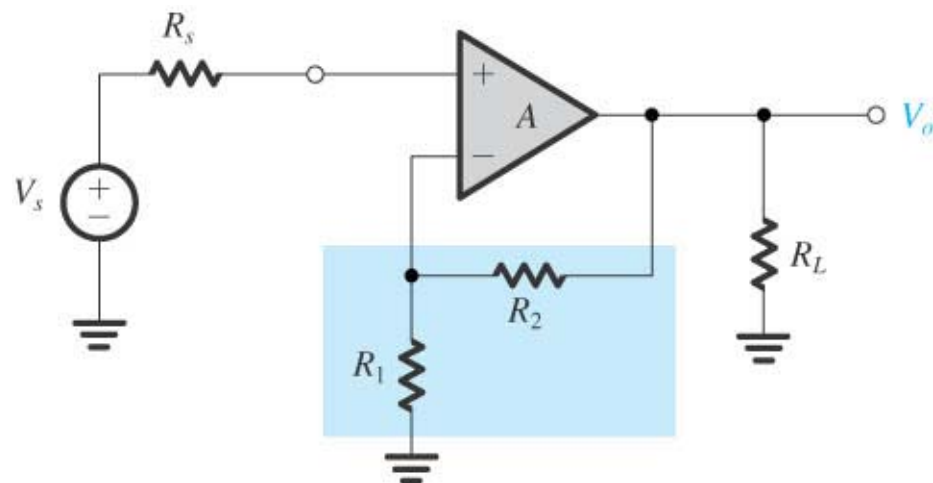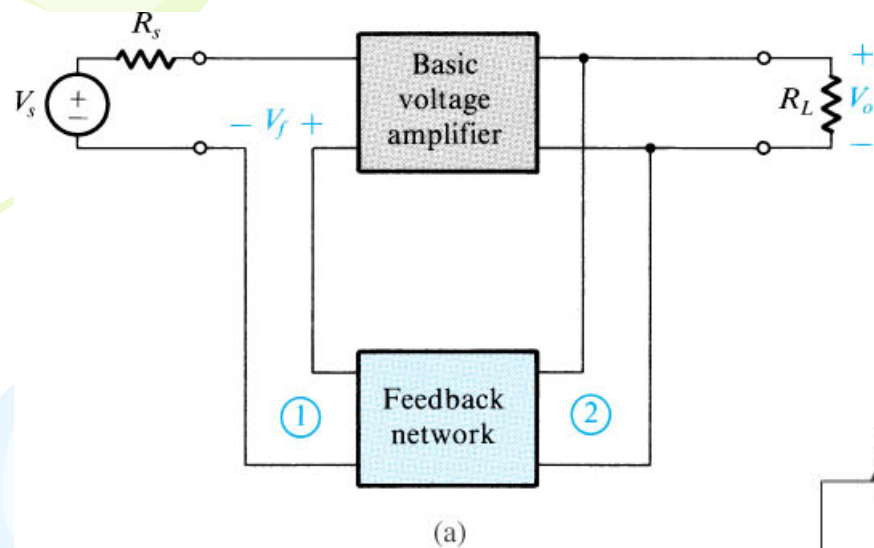
voltage-mixing voltage-sampling (series–shunt) topology



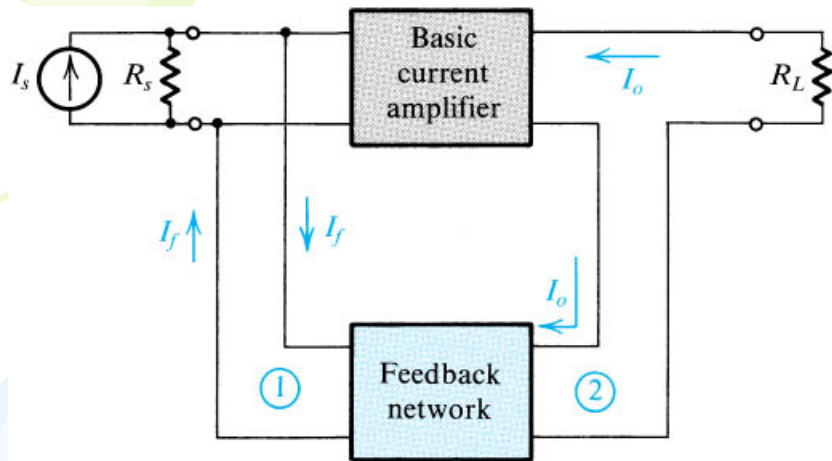
current-mixing current-sampling (shunt-series) topology




(b)

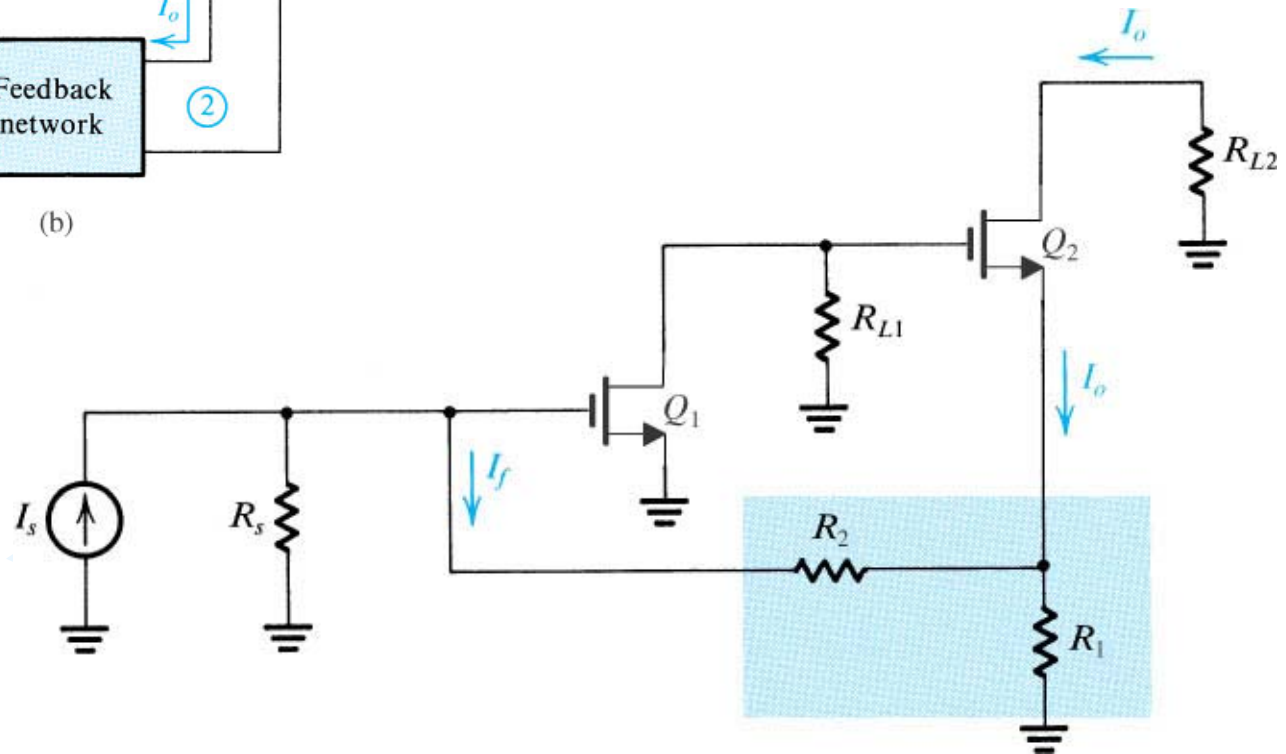


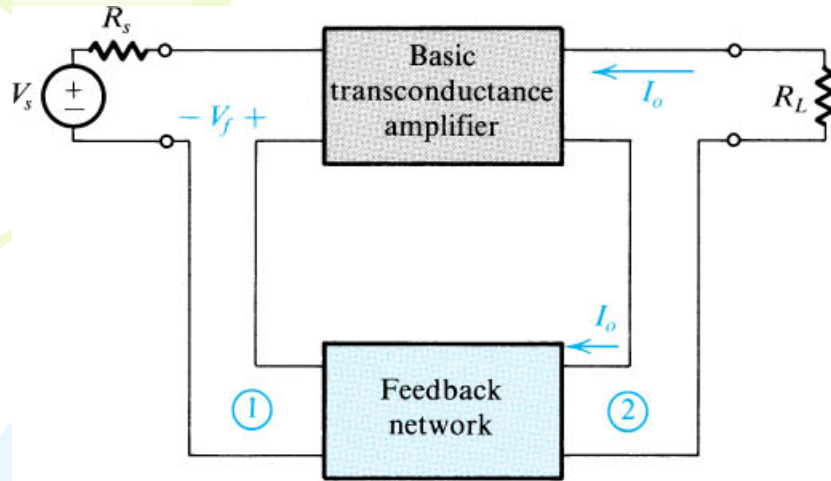
voltage-mixing current-sampling (series-series) topology






(c)

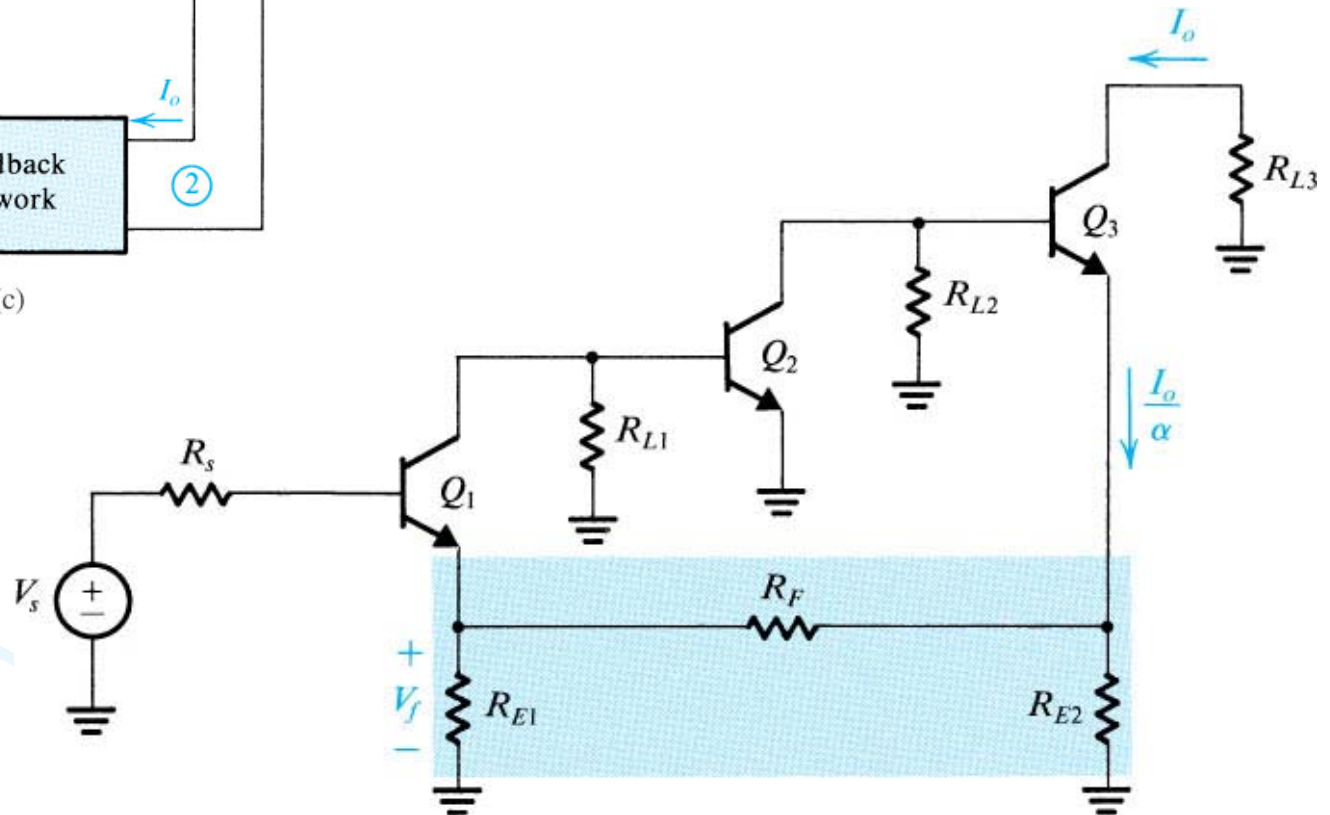

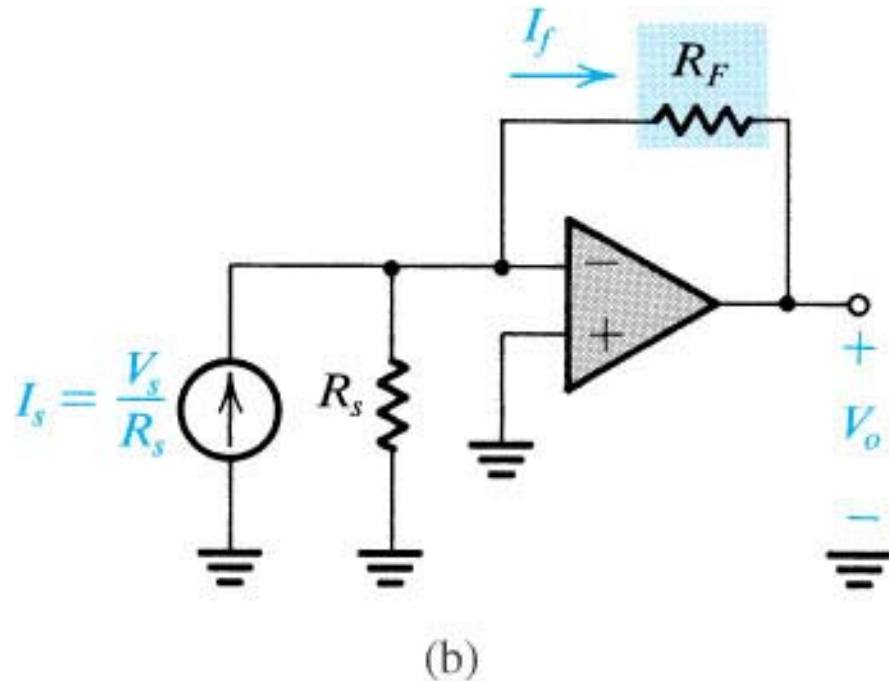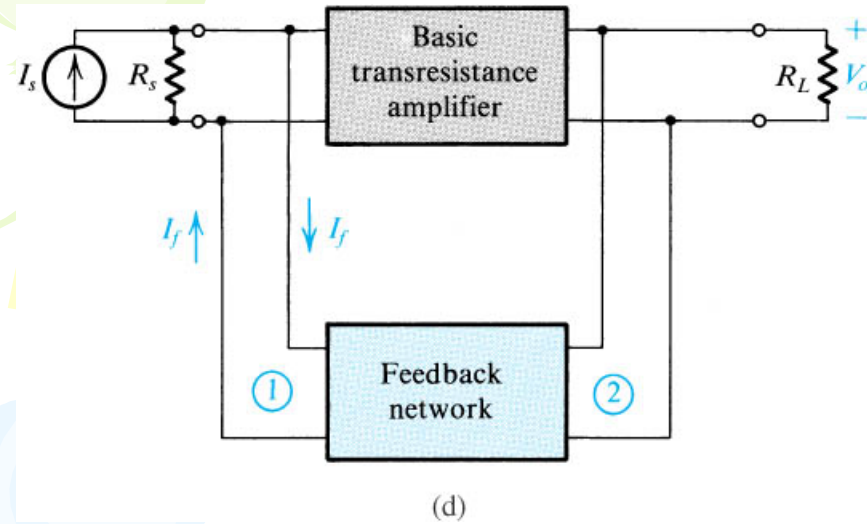current-mixing voltage-sampling (shunt–shunt) topology



The series–shunt feedback amplifier

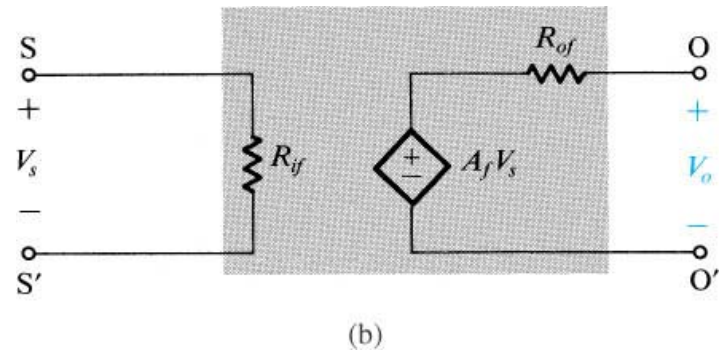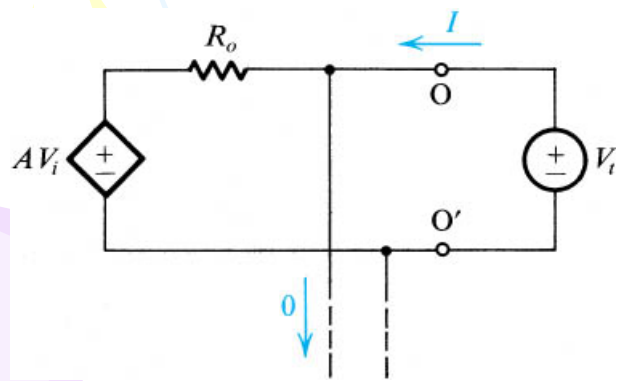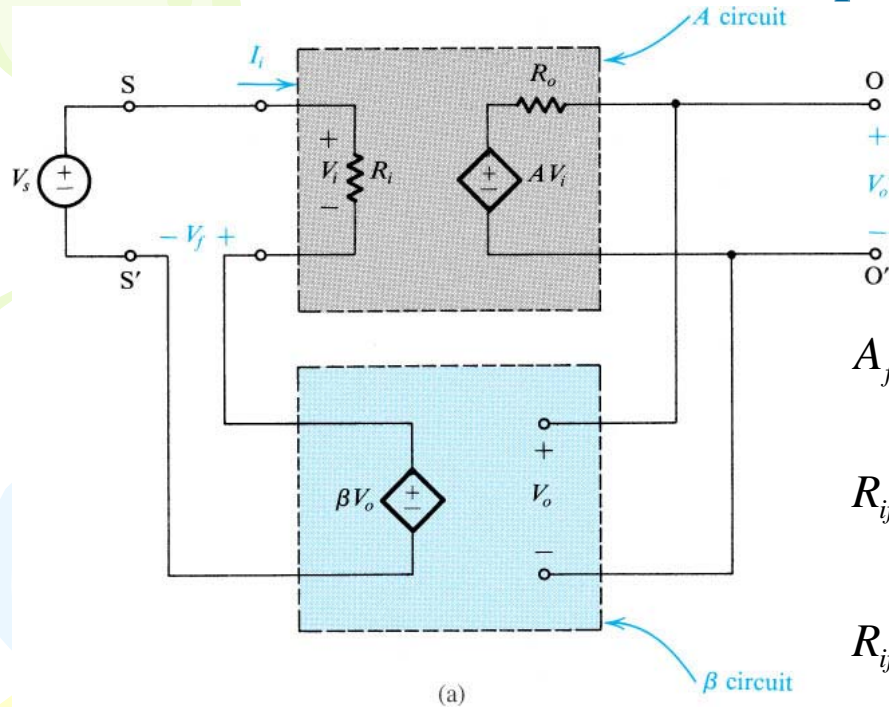

$$A_f \equiv \frac{V_o}{V_s} = \frac{A}{1 + \beta A}$$

$$R_{if} \equiv \frac{V_s}{I_i} = \frac{V_i + \beta V_o}{V_i / R_i} = \frac{V_i + \beta A V_i}{V_i / R_i} = R_i (1 + \beta A)$$


$$R_{if} = R_i (1 + \beta A)$$

$$R_{of} \equiv \left. \frac{V_o}{I_o} \right|_{V_s=0}$$


$$I_o = \frac{V_o - A V_i}{R_o}$$

$$V_i \big|_{V_s=0} = -\beta V_o$$
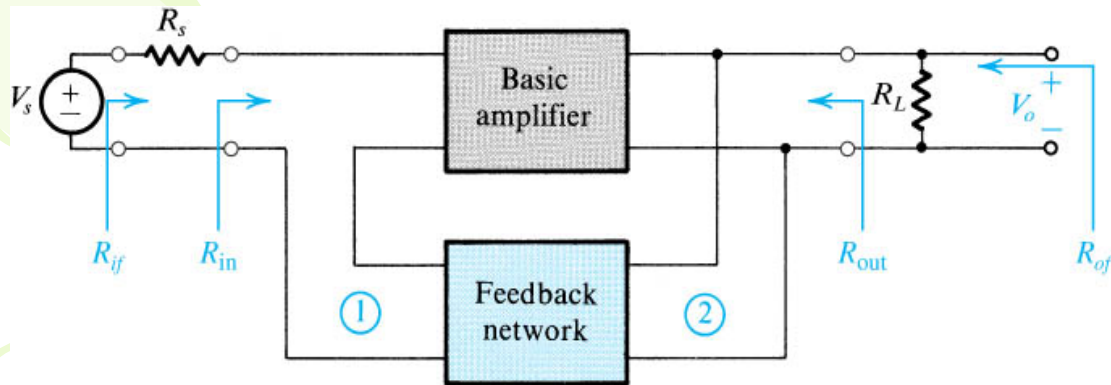
$$I = \frac{V_o + \beta A V_o}{R_o} \Rightarrow R_{of} = \frac{R_o}{1 + \beta A}$$



(a)

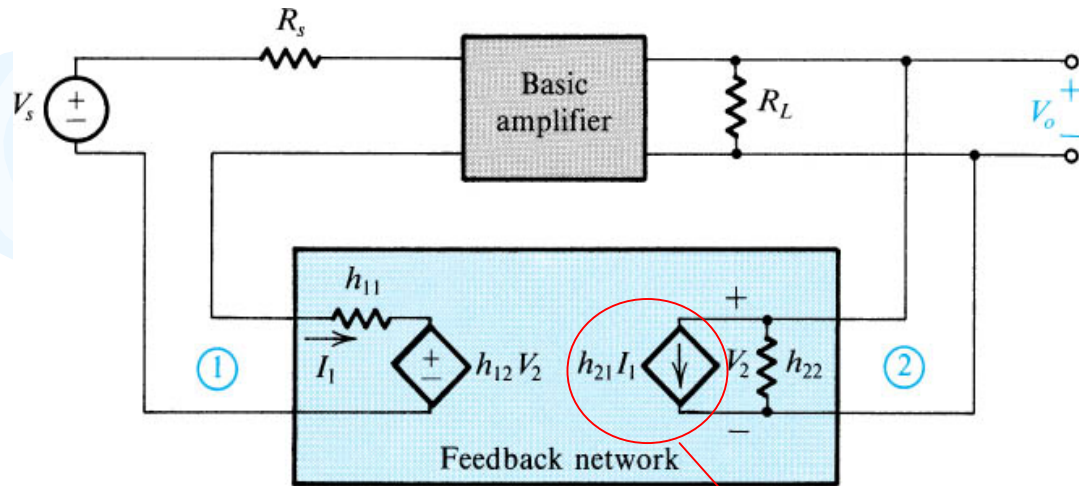

(b)


$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$


$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Passive network h_{21} tends to zero


(a) The A circuit is

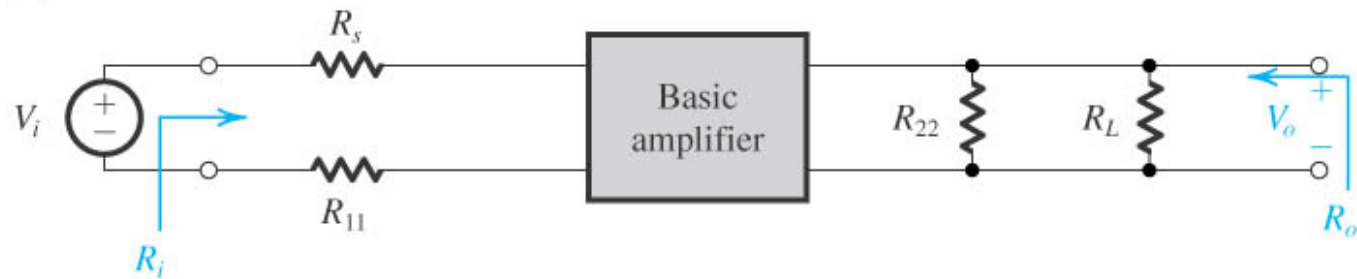

where R_{11} is obtained from

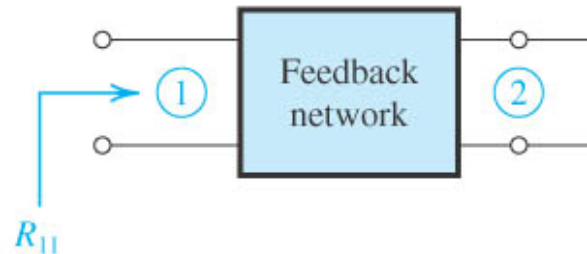


and R_{22} is obtained from

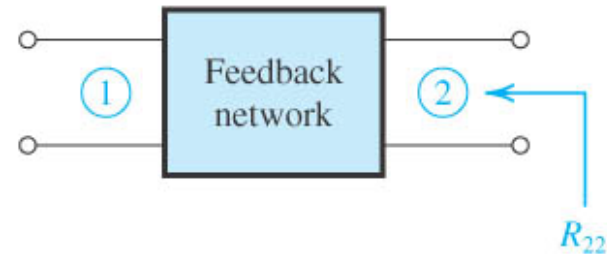


and the gain A is defined $A \equiv \frac{V_o}{V_i}$


(b) β is obtained from

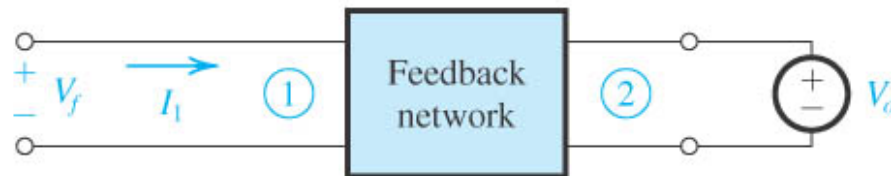

$$\beta \equiv \left. \frac{V_f}{V_o} \right|_{I_i = 0}$$

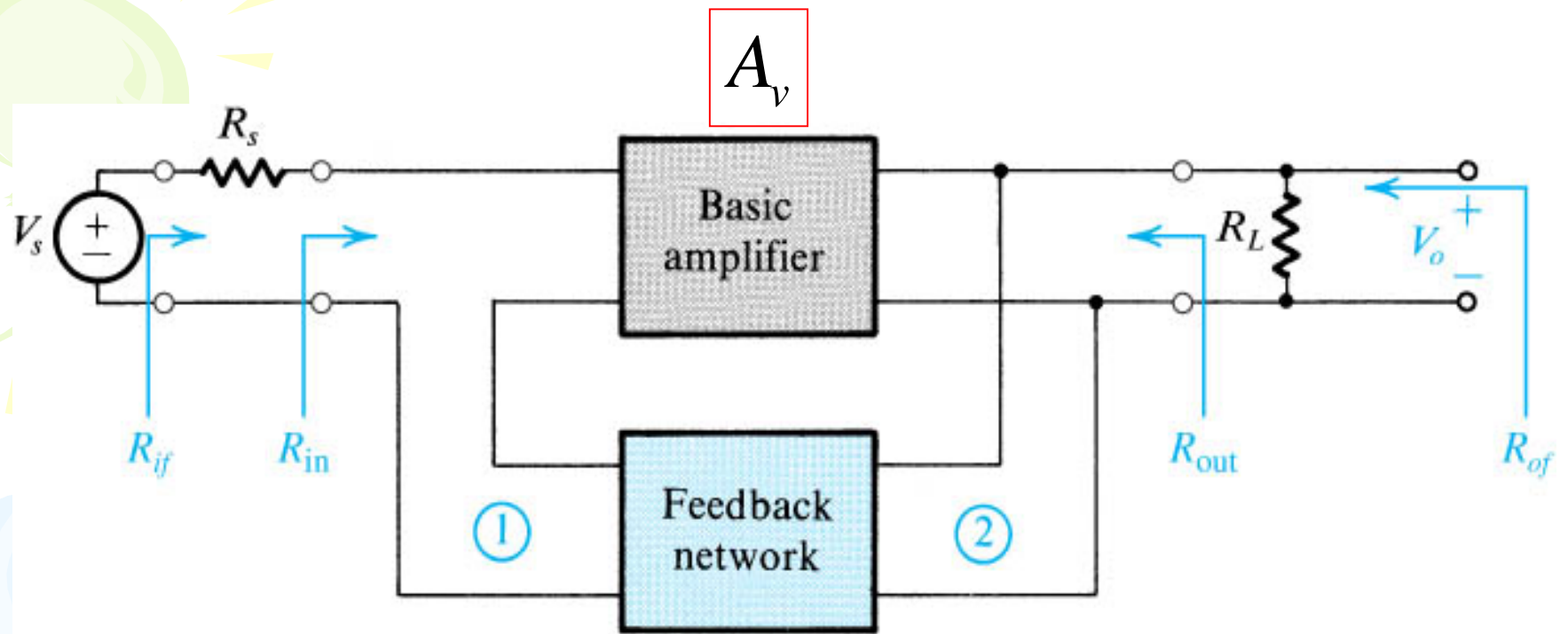

(a)

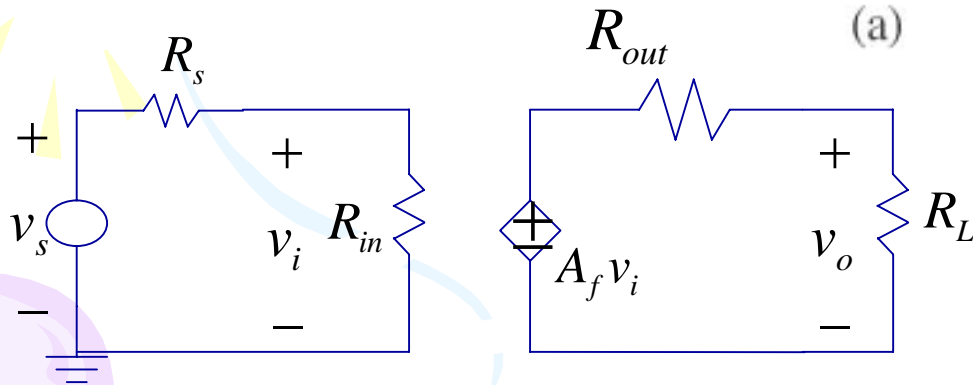


$$R_{if} = (1 + \beta A) R_i = R_s + R_{in}$$

$$R_{of} = \frac{R_o}{(1 + \beta A)} = R_{out} // R_L$$

Series -Shunt


The series-series feedback amplifier

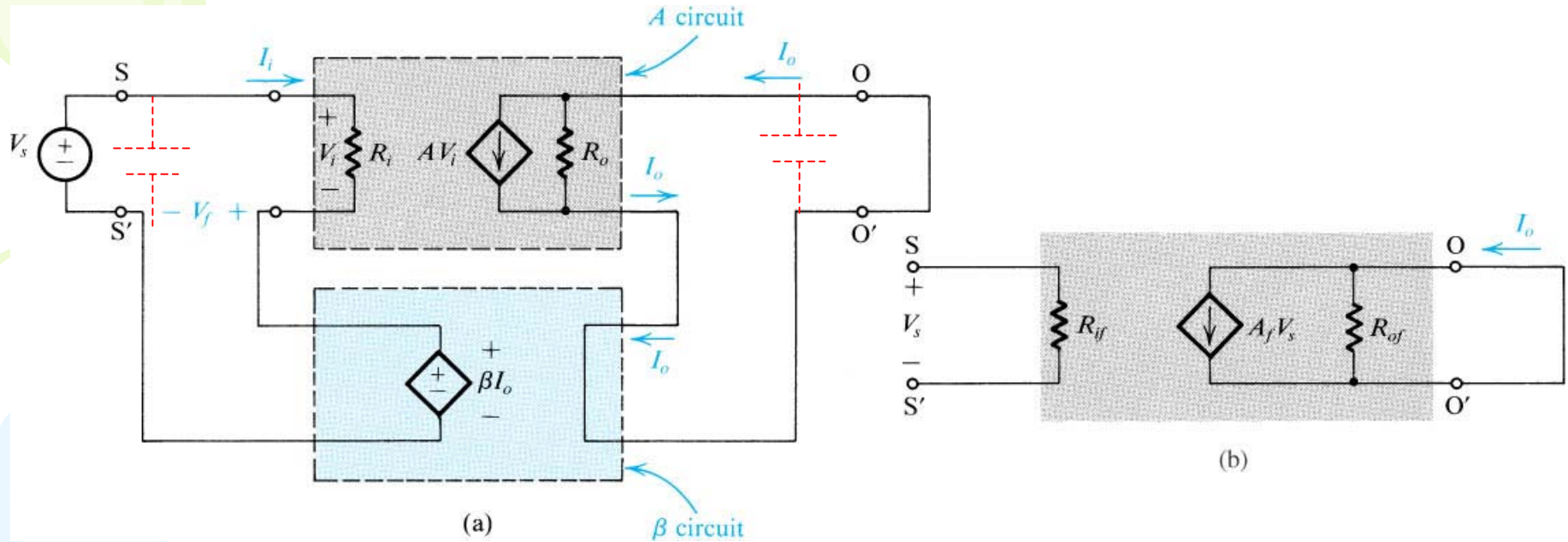


$$R_{if} = \frac{V}{I} \Big|_{V_o=0} = \frac{V_i + \beta I_o}{V_i / R_i} = \frac{V_i + \beta A V_i}{V_i / R_i} = R_i (1 + \beta A)$$

$$R_{of} = \frac{V_o}{I_o} \Big|_{V_s=0} \Rightarrow V_o = (I_o - A V_i) R_o = [I_o - A(-\beta I_o)] R_o = (1 + \beta A) R_o$$

$$R_{of} = (1 + \beta A) R_o$$

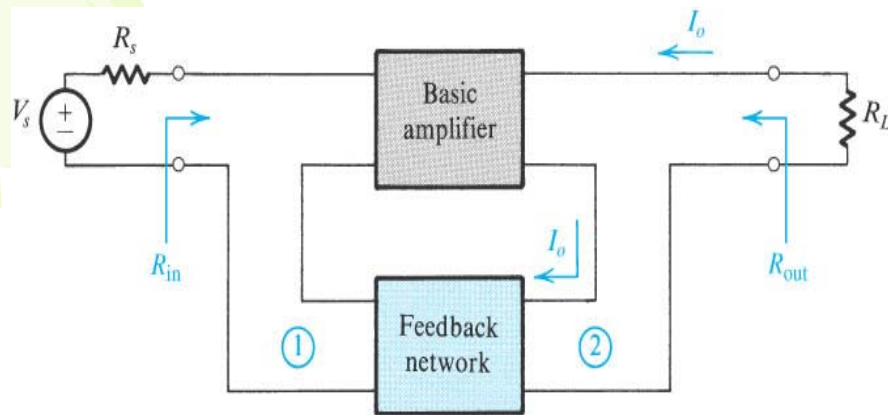

(a)

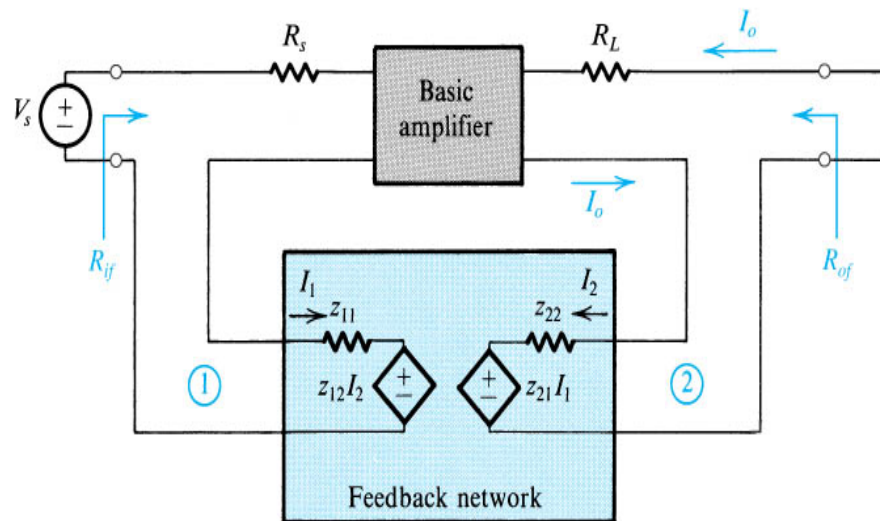


(b)

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$
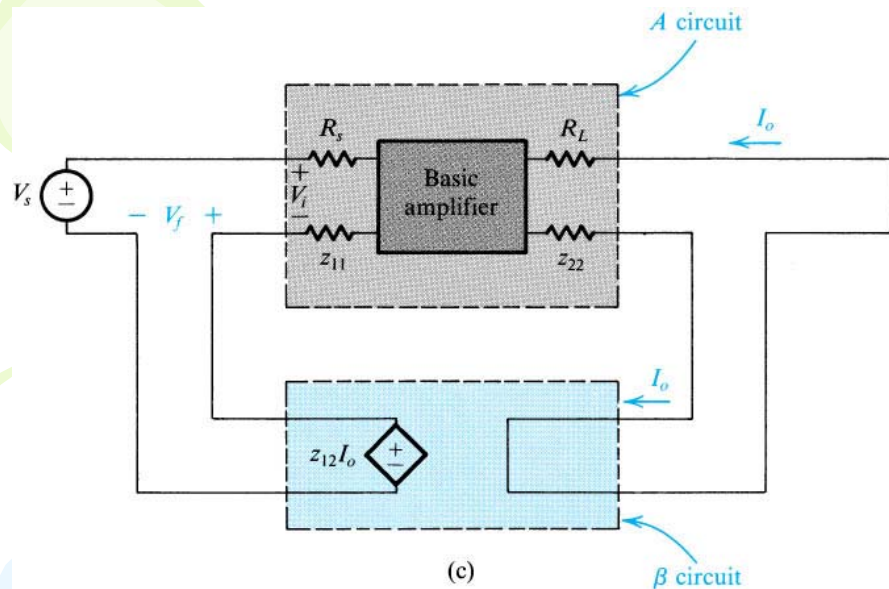
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$




$$A = A_B \times \frac{R_i}{R_s + R_i + z_{11}} \times \frac{R_o}{R_o + R_L + z_{22}}$$

$$R_{if} = (1 + \beta A)(R_s + R_i + z_{11}) = R_s + R_{in}$$

$$R_{of} = (1 + \beta A)(R_L + R_o + z_{22}) = R_{out} + R_L$$

$$A_f = \frac{A}{1 + \beta A}$$

Figure 8.15 (Continued) (c) A redrawing of the circuit in (b) with z_{21} neglected.

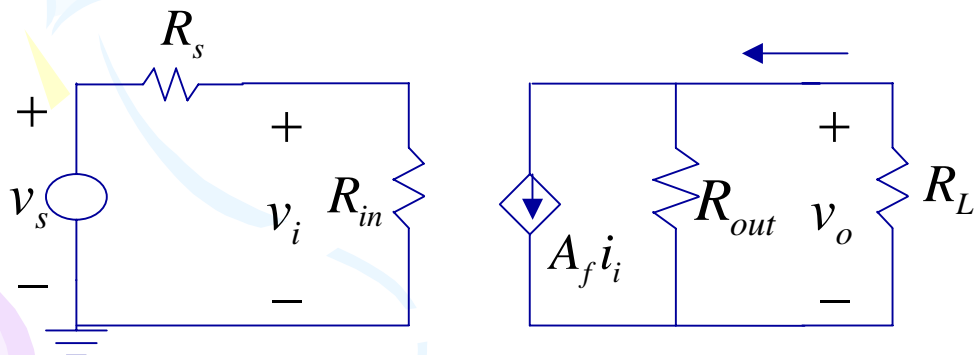


$$R_{if} = R_s + R_{in}$$


$$R_{of} = R_{out} + R_L$$

Series -Series


(a) The A circuit is

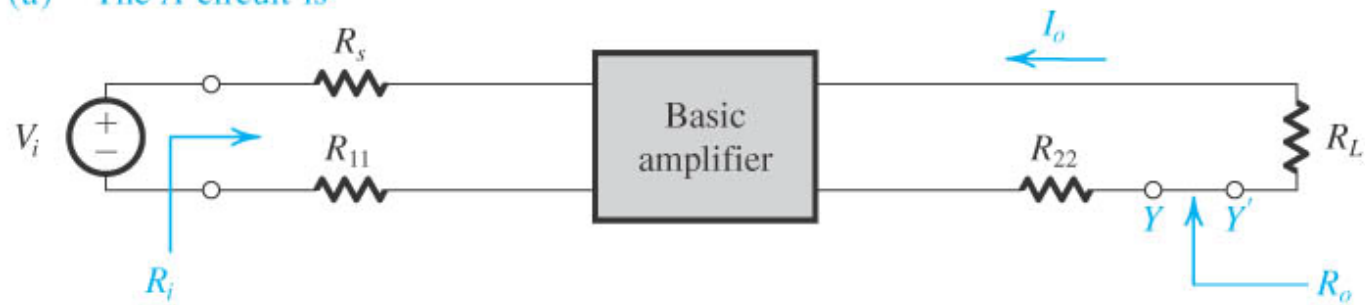

where R_{11} is obtained from

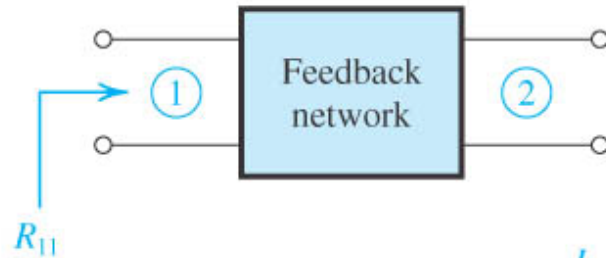


and R_{22} is obtained from

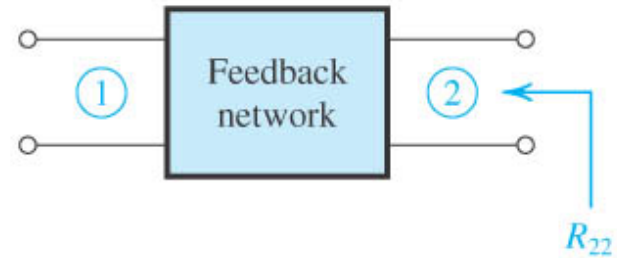


and the gain A is defined $A \equiv \frac{I_o}{V_i}$

(b) β is obtained from

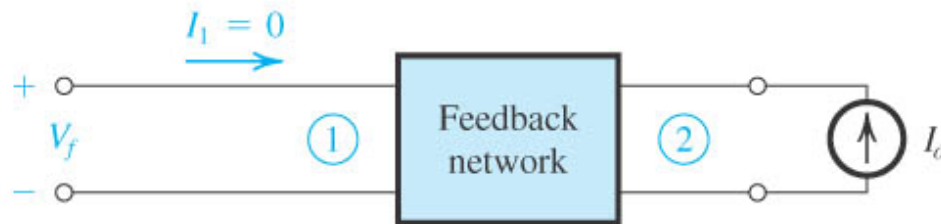

$$\beta \equiv \left. \frac{V_f}{I_o} \right|_{I_1 = 0}$$

the shunt–shunt feedback amplifier

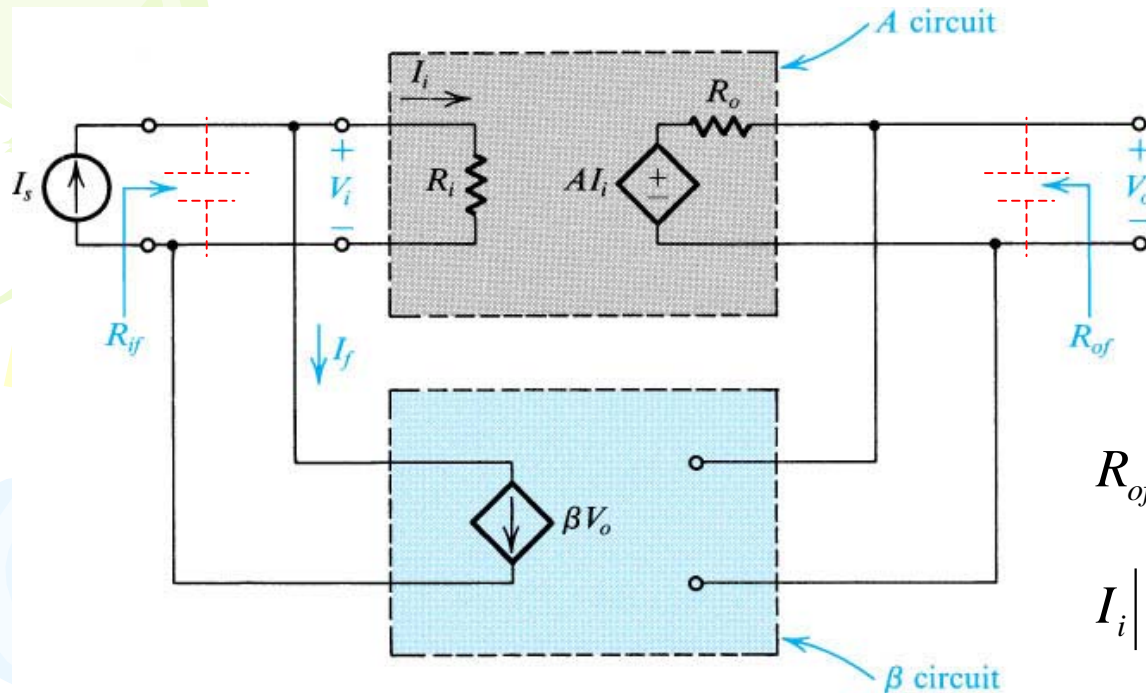

$$A = R_m = \frac{V_o}{I_i}$$

$$R_{if} = \frac{V_s}{I_s} = \frac{V_s}{I_i + \beta V_o} = \frac{V_s}{I_i + \beta A I_i} = \frac{I_i R_i}{I_i + \beta A I_i}$$

$$R_{if} = \frac{R_i}{1 + \beta A}$$


$$R_{of} = \frac{V_o}{I_o} = \frac{I_o R_o + A I_i}{I_o}$$

$$I_i \Big|_{I_s=0} = -\beta V_o = -\beta (I_o R_o + A I_i)$$


$$I_i = \frac{-\beta I_o R_o}{1 + \beta A}$$



$$R_{of} = \frac{V_o}{I_o} = \frac{I_o R_o + A \frac{-\beta I_o R_o}{1 + \beta A}}{I_o}$$
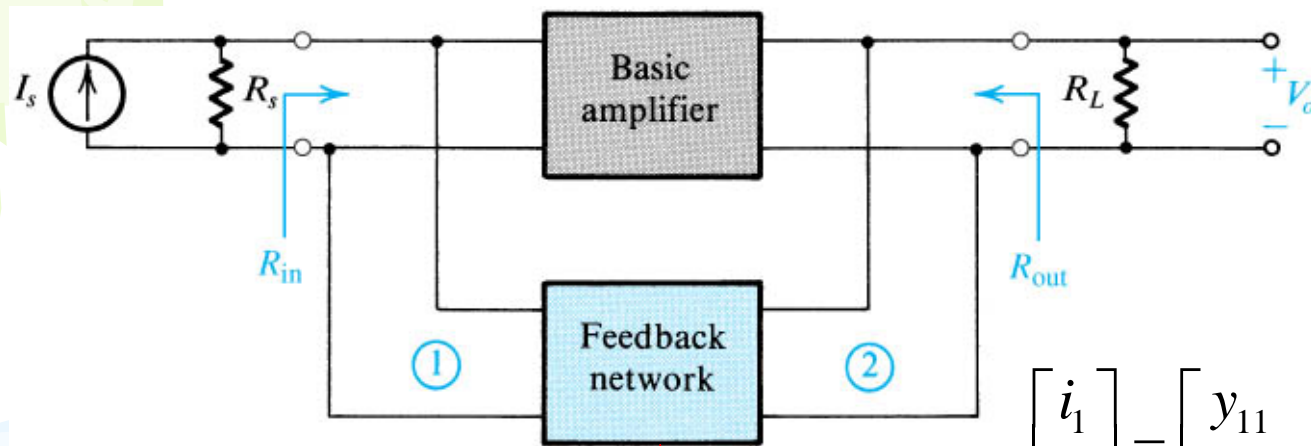
$$= R_o \left(1 + A \frac{-\beta}{1 + \beta A} \right) = R_o \frac{1}{1 + \beta A}$$


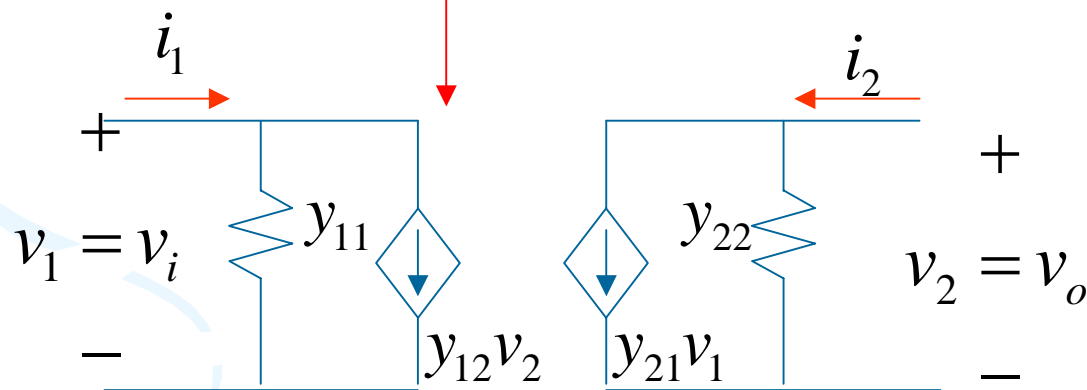
$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$



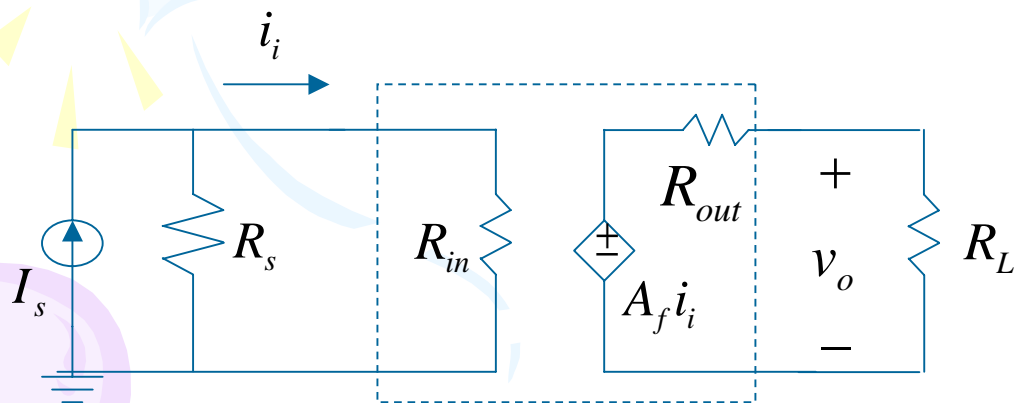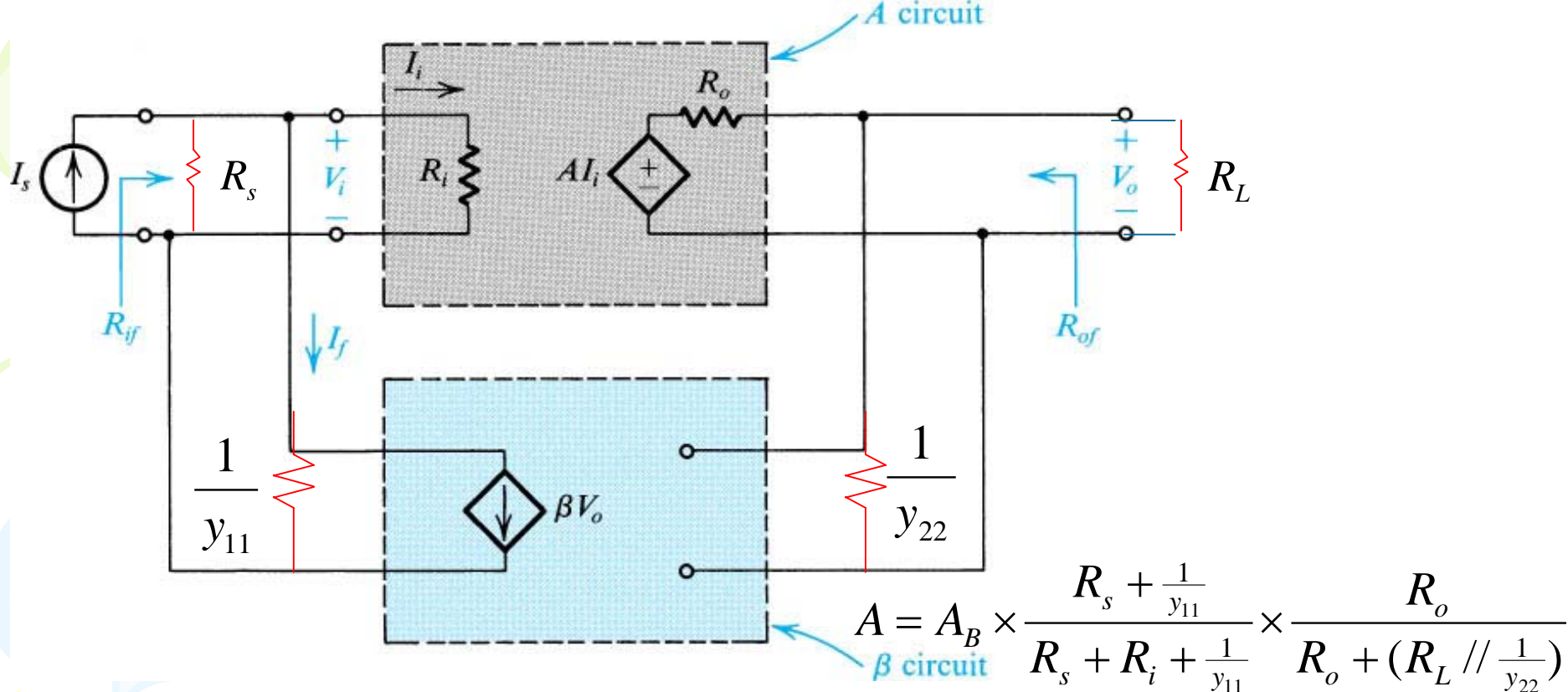


$$R_{if} = \frac{(R_s // R_i // \frac{1}{y_{11}})}{(1 + \beta A)} = R_s // R_{in}$$

$$R_{of} = \frac{R_o // \frac{1}{y_{22}} // R_L}{(1 + \beta A)} = R_{out} // R_L$$


$$A_f = \frac{A}{1 + \beta A}$$

Shunt -Shunt


(a) The A circuit is

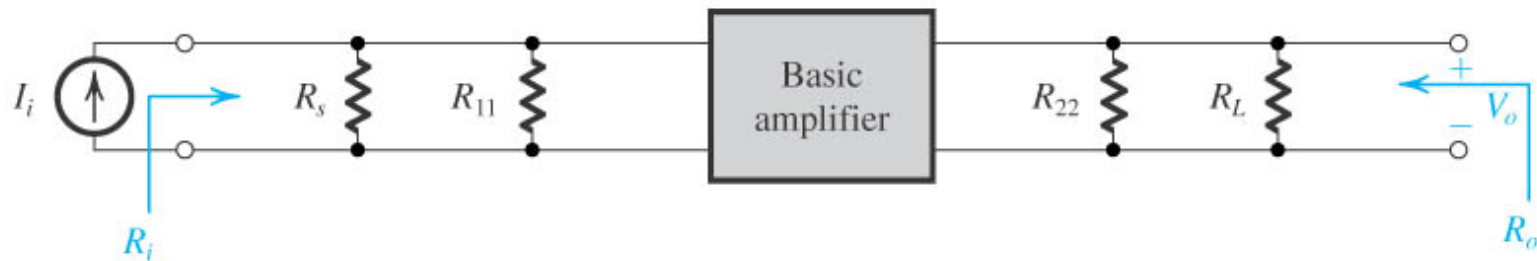

where R_{11} is obtained from

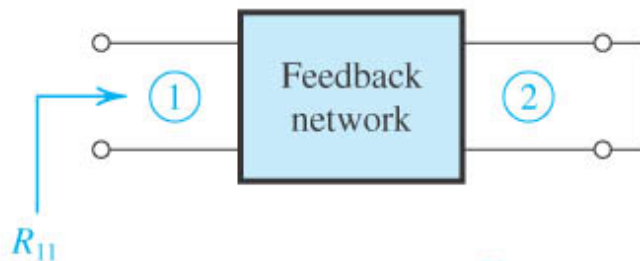


and R_{22} is obtained from

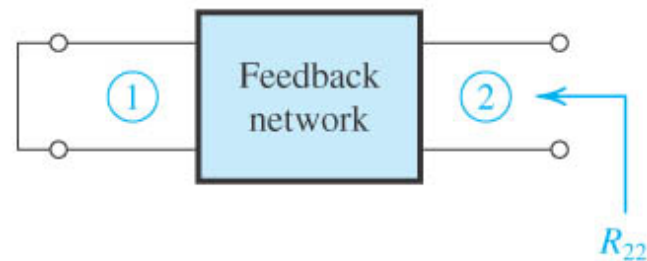


and the gain A is defined $A \equiv \frac{V_o}{I_i}$

(b) β is obtained from

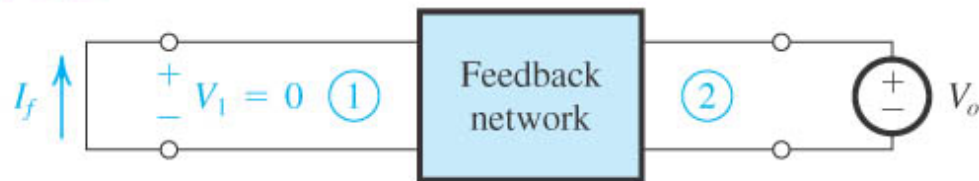

$$\beta \equiv \left. \frac{I_f}{V_o} \right|_{V_1 = 0}$$

The shunt-series feedback amplifier

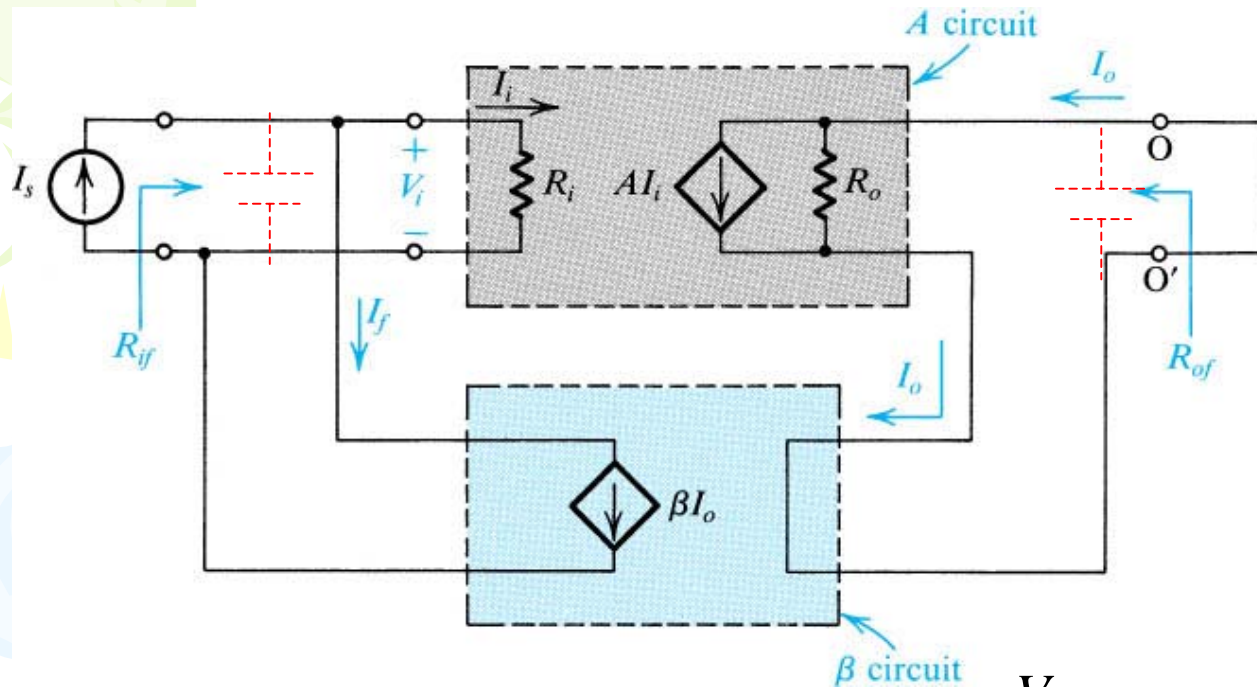

$$I_s = \frac{V_s}{R_i} + \beta I_o$$


$$I_o \big|_{V_o=0} = AI_i \Rightarrow I_s = \frac{V_s}{R_i} + \beta AI_i = \frac{V_s}{R_i} + \beta A \frac{V_s}{R_i}$$

$$R_{if} = \frac{R_i}{1 + \beta A}$$


$$R_{of} = \frac{V_o}{I_o} \bigg|_{I_s=0}$$



$$\Rightarrow V_o = (I_o - AI_i)R_o = [I_o - A(-\beta I_o)]R_o \\ = (1 + \beta A)R_o I_o$$

$$R_{of} = \frac{V_o}{I_o} \bigg|_{I_s=0} = (1 + \beta A)R_o$$

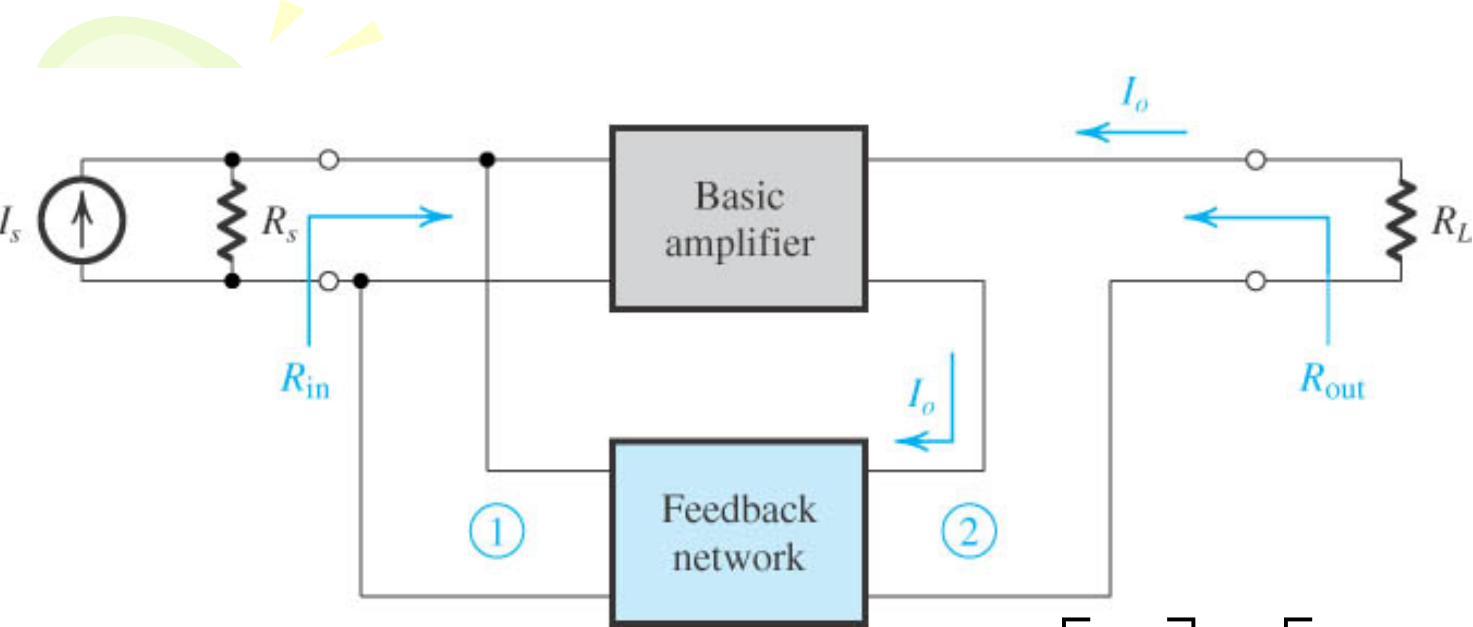
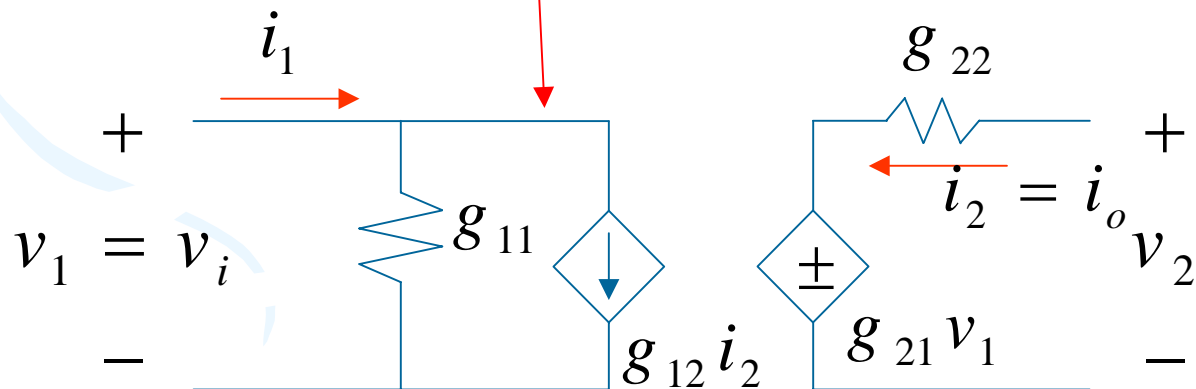
$$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$



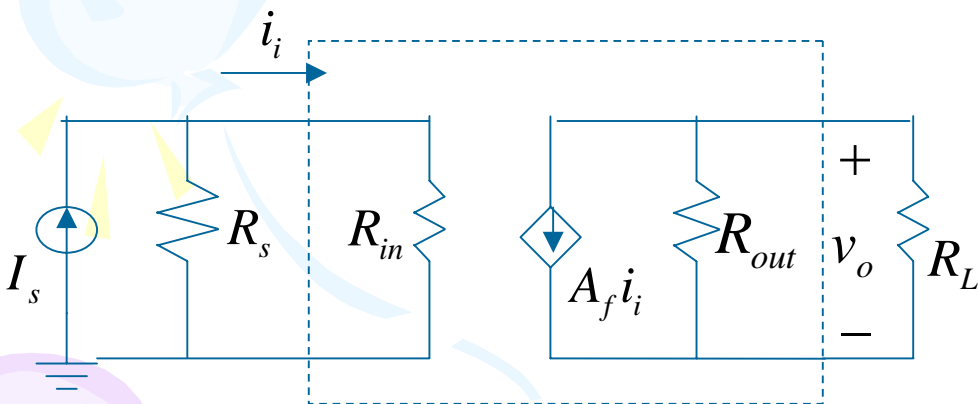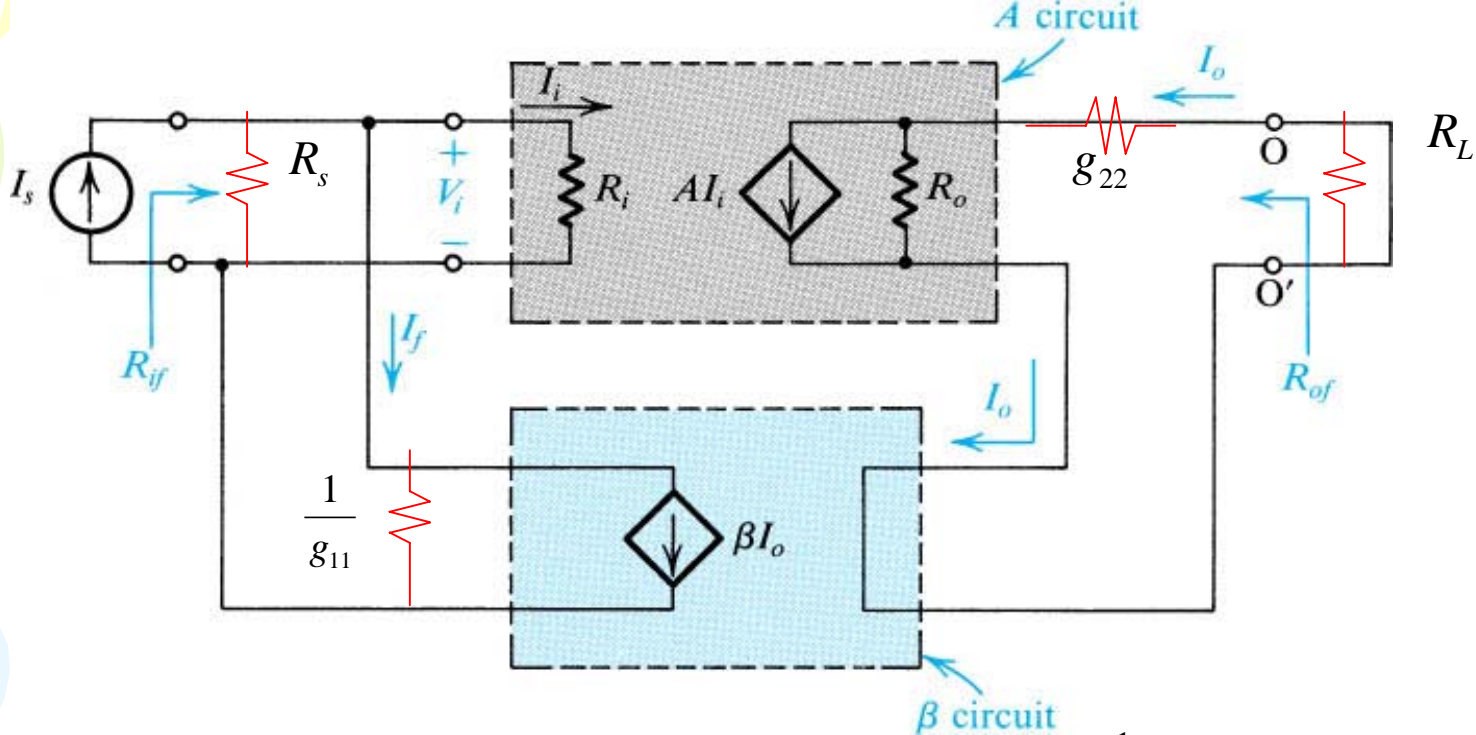

$$A = A_B \times \frac{R_s + \frac{1}{g_{11}}}{R_s + R_i + \frac{1}{g_{11}}} \times \frac{R_o}{R_o + R_L + g_{22}}$$


$$R_{if} = \frac{(R_s // R_i // \frac{1}{y_{11}})}{(1 + \beta A)} = R_s // R_{in}$$

$$R_{of} = (1 + \beta A)(R_o + g_{22} + R_L) = R_{out} + R_L$$


$$A_f = \frac{A}{1 + \beta A}$$

Shunt -Series


(a) The A circuit is

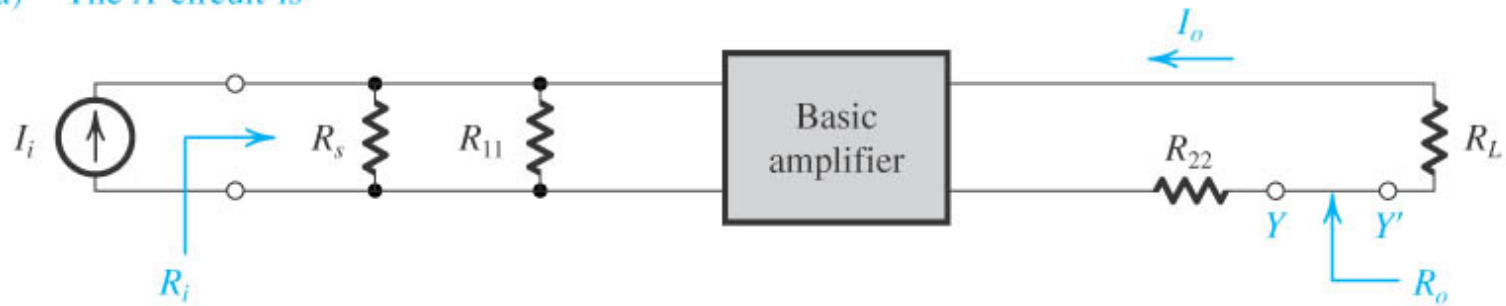

where R_{11} is obtained from

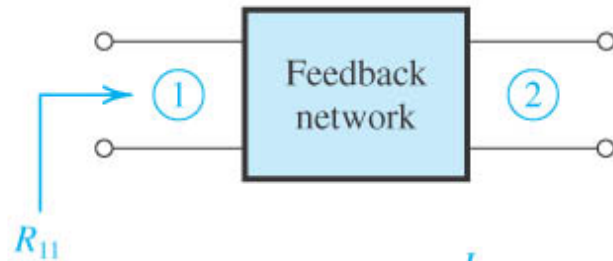


and R_{22} is obtained from

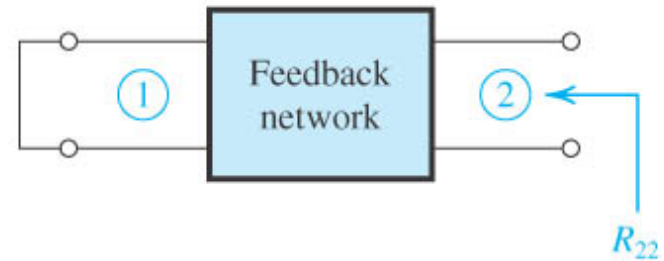

and the gain A is defined as $A \equiv \frac{I_o}{I_i}$


(b) β is obtained from

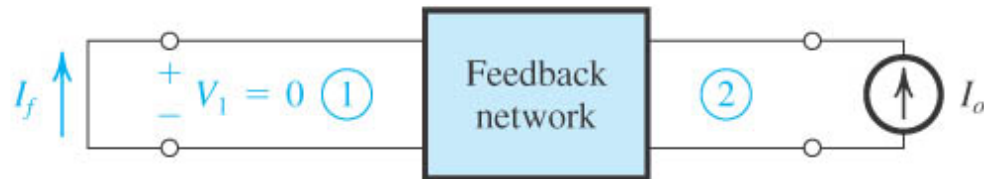

$$\beta \equiv \left. \frac{I_f}{I_o} \right|_{V_1 = 0}$$

Type	Amplifier	Feedback parameter	$A_f = \frac{A}{1 + \beta A}$	R_{if}	R_{of}
Series-Shunt (voltage-voltage)	$A_v = \frac{v_o}{v_i}$	$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = h$	$A_f = \frac{A_v}{1 + h_{12}A_v}$	$R_{if} = (1 + \beta A)R_i$	$R_{of} = \frac{R_o}{1 + \beta A}$
Series-Series (voltage-current)	$G_m = \frac{i_o}{v_i}$	$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = z$	$G_{mf} = \frac{G_m}{1 + z_{12}G_m}$	$R_{if} = R_i(1 + \beta A)$	$R_{of} = R_o(1 + \beta A)$
Shunt-Shunt (current-voltage)	$R_m = \frac{v_o}{i_i}$	$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = y$	$R_{mf} = \frac{R_m}{1 + y_{12}R_m}$	$R_{if} = \frac{R_i}{(1 + \beta A)}$	$R_{of} = \frac{R_o}{(1 + \beta A)}$
shunt-series (current-current)	$A_I = \frac{i_o}{i_i}$	$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = g$	$A_{If} = \frac{A_I}{1 + g_{12}A_I}$	$R_{if} = \frac{R_i}{1 + \beta A}$	$R_{of} = (1 + \beta A)R_o$

Example 8.1

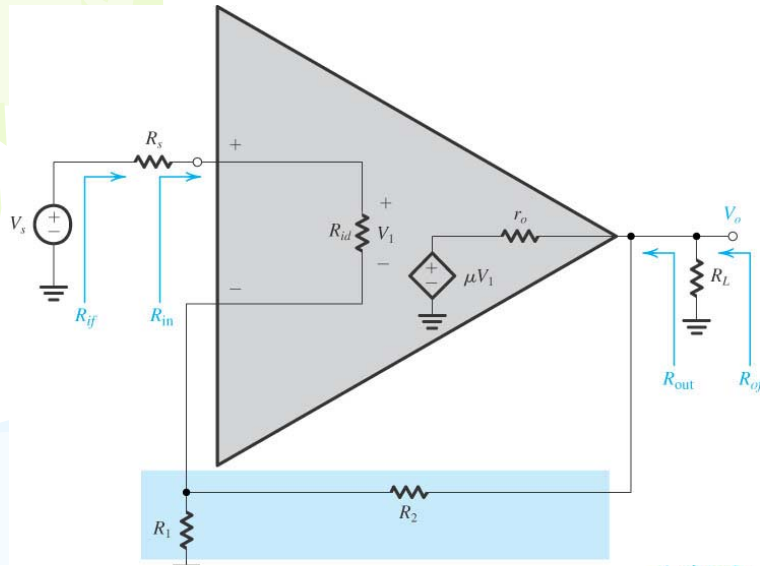


Step 0 : Series-shunt
feedback amplifier

Amplifier → Voltage amplifier
Feedback → h parameters


Step 1 : Amplifier analysis

$$R_i = R_{id}$$

$$R_o = r_o$$

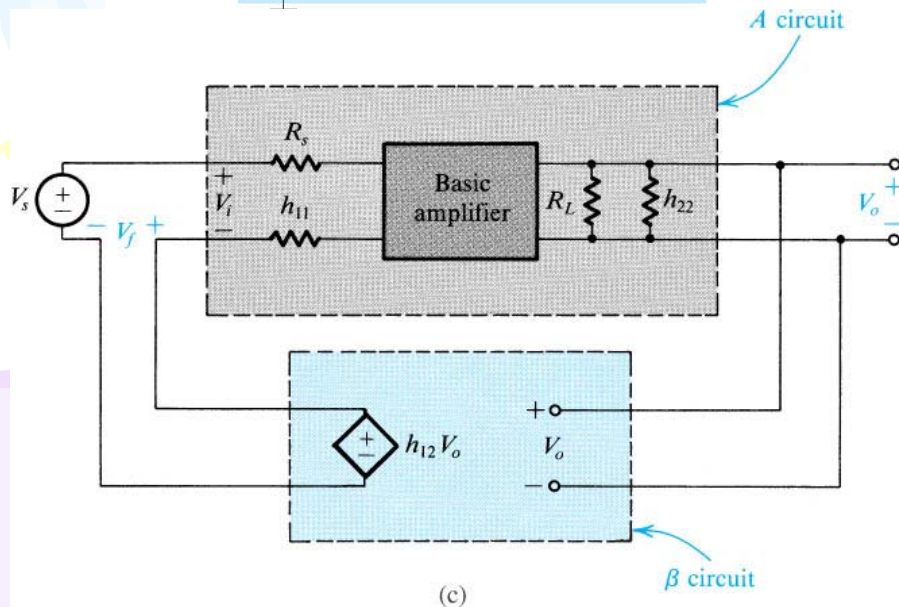
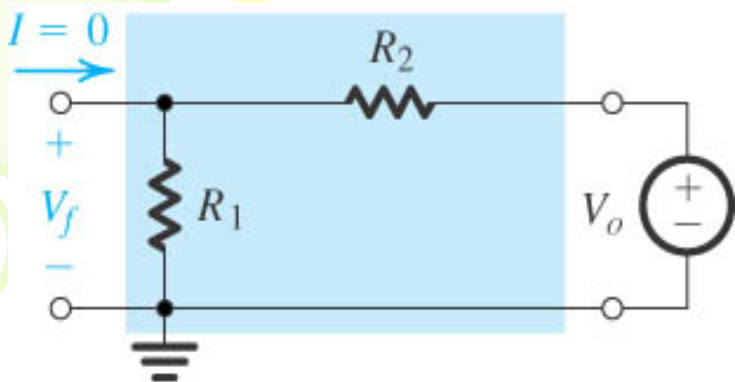
$$A = \frac{V_o}{V_i} = \overset{A_B}{\mu} \frac{(R_L // h_{22})}{(R_L // h_{22}) + r_o} \frac{R_{id}}{R_{id} + R_s + h_{11}}$$



(c)

Step 2 : Feedback network analysis

$$V_1 = h_{11}I_1 + h_{12}V_2$$


$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = R_1 // R_2$$

$$h_{22} = \left. \frac{I_1}{V_2} \right|_{I_1=0} = R_1 + R_2$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{R_1}{R_1 + R_2} = \beta$$

Step 3 : Amp+Feedback analysis

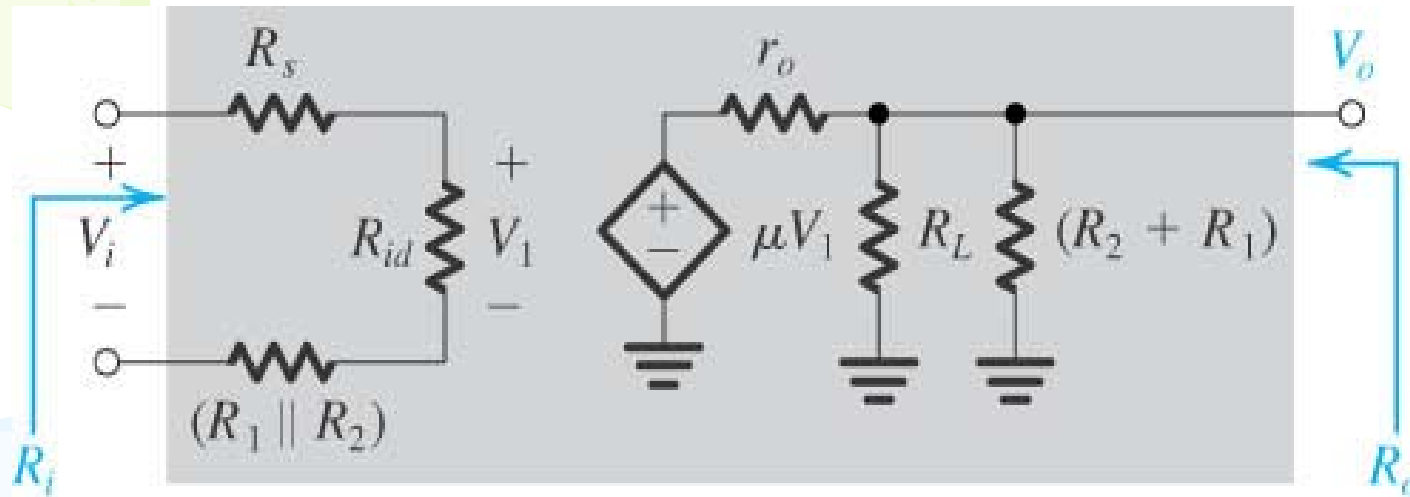

$$R_{if} = (1 + \beta A)(R_s + R_i + h_{11}^{(b)}) = (1 + \beta A)(R_s + R_{id} + (R_1 \parallel R_2)) = R_s + R_{in}$$

$$R_{in} = R_s - R_{if}$$


$$R_{of} = \frac{R_o \parallel \frac{1}{h_{22}} \parallel R_L}{(1 + \beta A)} = \frac{r_o \parallel (R_1 + R_2) \parallel R_L}{(1 + \beta A)} = R_{out} \parallel R_L$$

Feedback AMP

$$R_{out} \Rightarrow \text{find}$$

$$A_f = \frac{A}{1 + \beta A}$$

Example 8.2

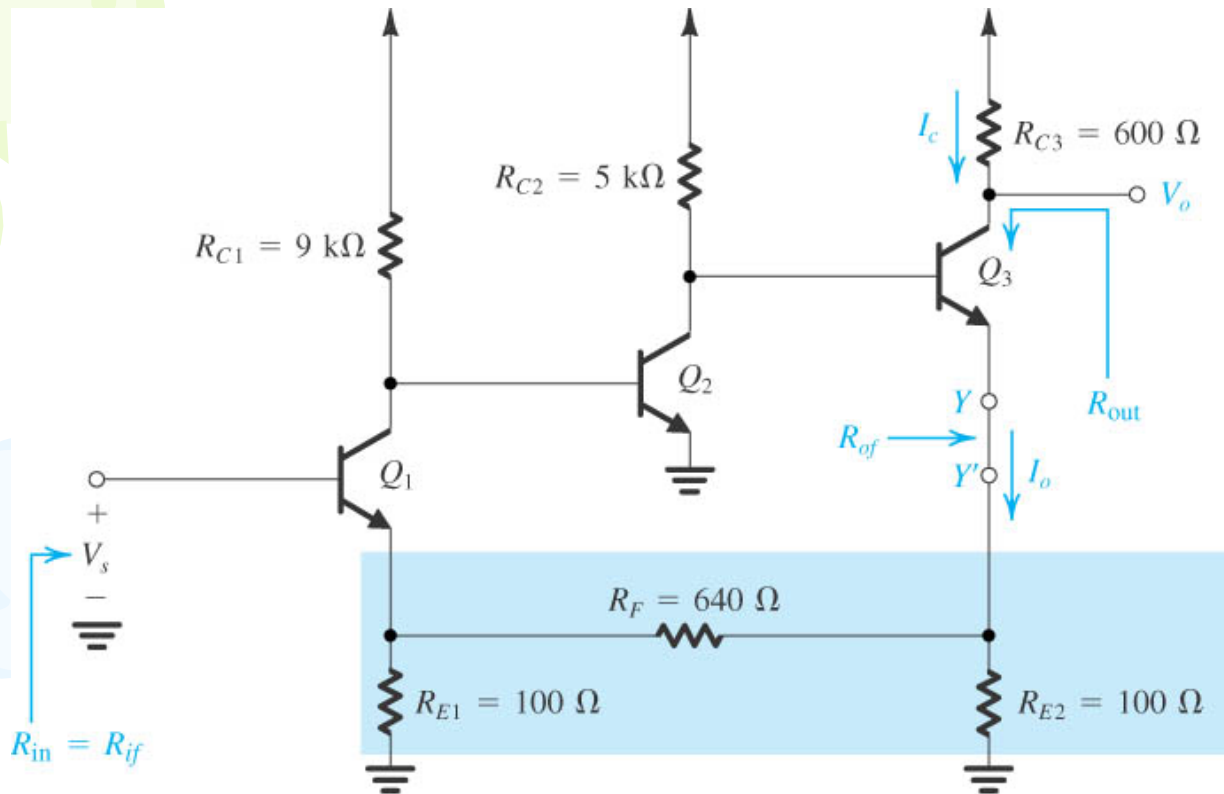




(a)

Step 0 : Series-series feedback amplifier

Amplifier \rightarrow Transconductance amplifier

Feedback \rightarrow z parameters

Step 1 : Amplifier analysis

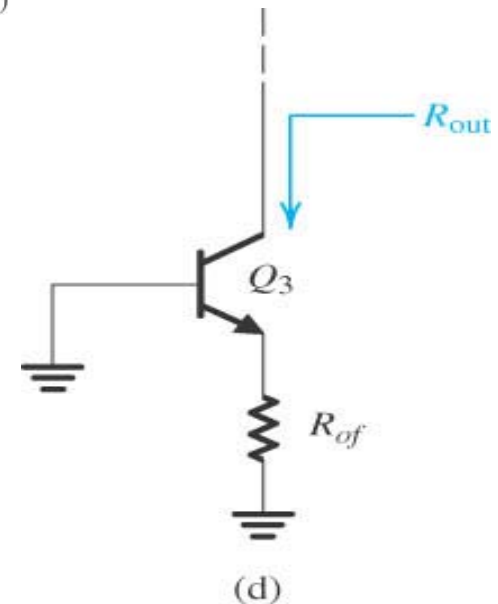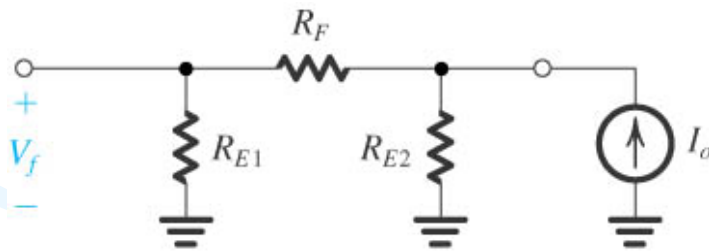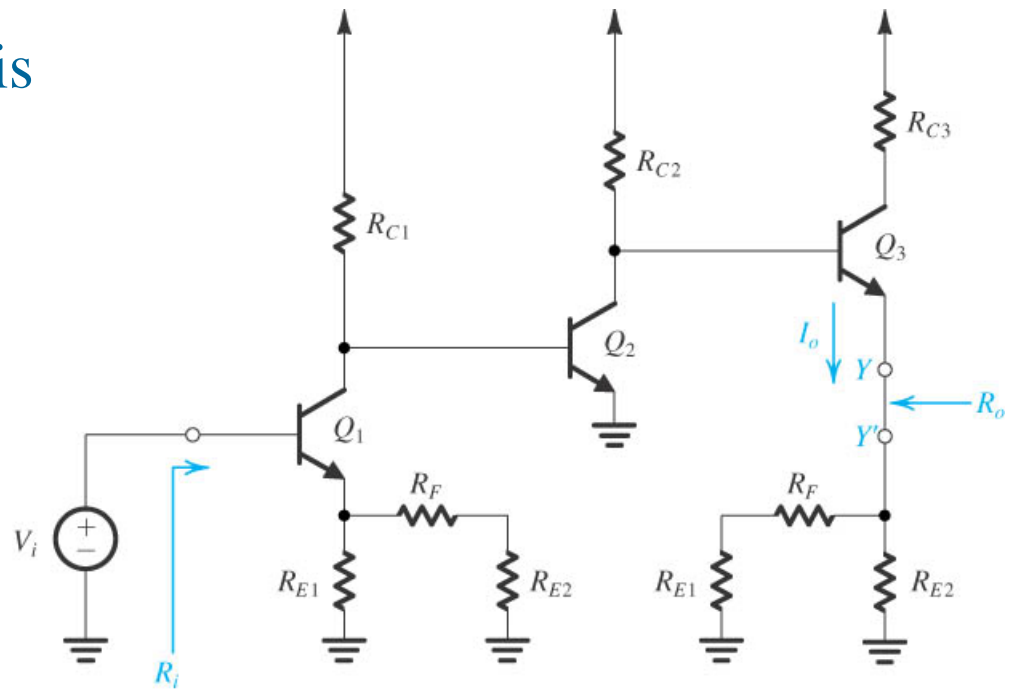


Step 2 : Analysis feedback Amp

$$Z_{11} = R_1 // (R_2 + R_3)$$

$$Z_{22} = R_3 // (R_1 + R_2)$$

The equivalent circuit

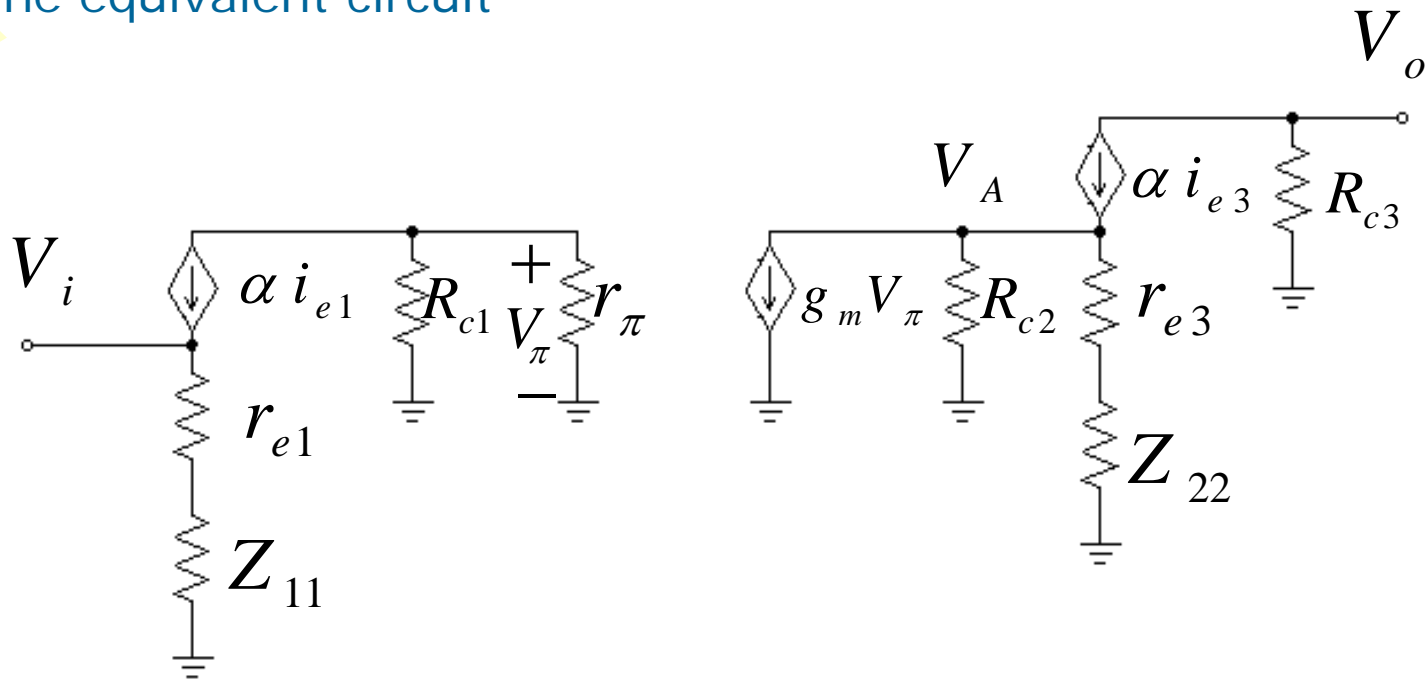

Step 3 : Amp+Feedback analysis

$$V_i = i_{e1} (r_{e1} + Z_{11})$$

$$V_A = -g_m V_\pi [R_{c2} \parallel (1 + hfe)(r_{e3} + Z_{22})]$$

$$I_o = \frac{V_A}{r_{e2} + Z_{22}}$$

$$-\alpha i_{e1} = \frac{V_\pi}{R_{c1} \parallel r_\pi} \Rightarrow A = \frac{I_o}{V_i}$$



$$R_i' = (r_{e1} + Z_{11})(1 + hfe)$$

$$R_o' = r_{e3} + Z_{22} + \frac{R_{c2}}{1 + hfe}$$

$$R_{if} = (1 + \beta A') R_i'$$


$$R_{of} = (1 + \beta A') R_o'$$

Example 8.3

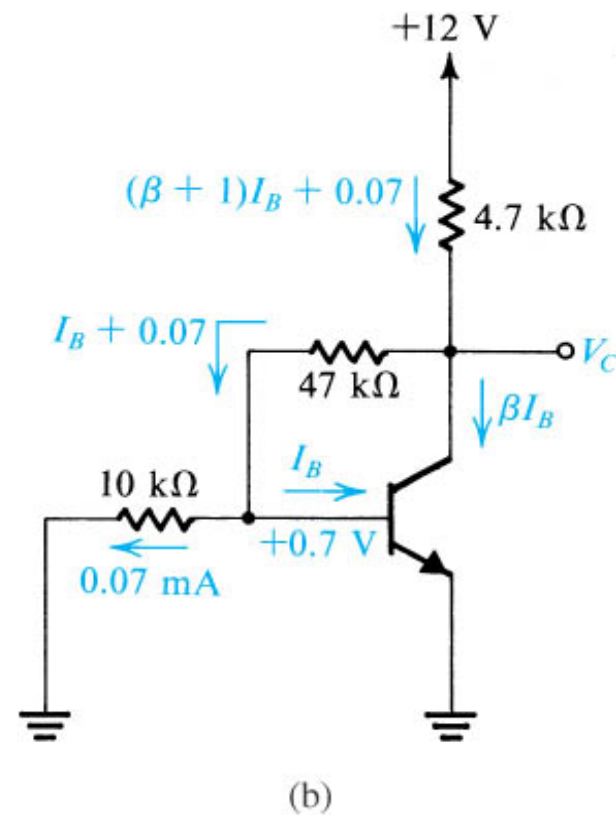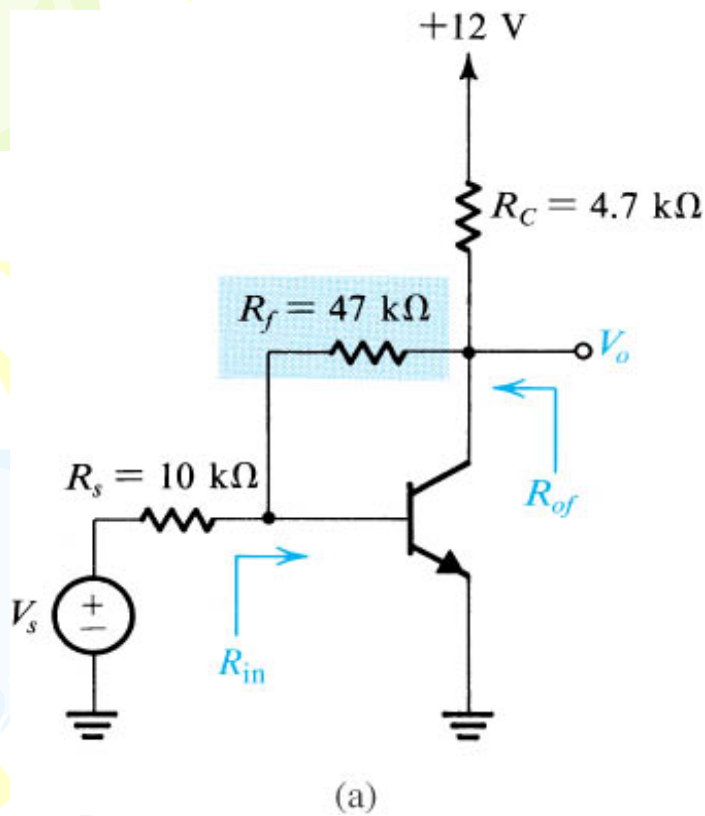


Shunt-shunt: R_m amplifier + y parameter

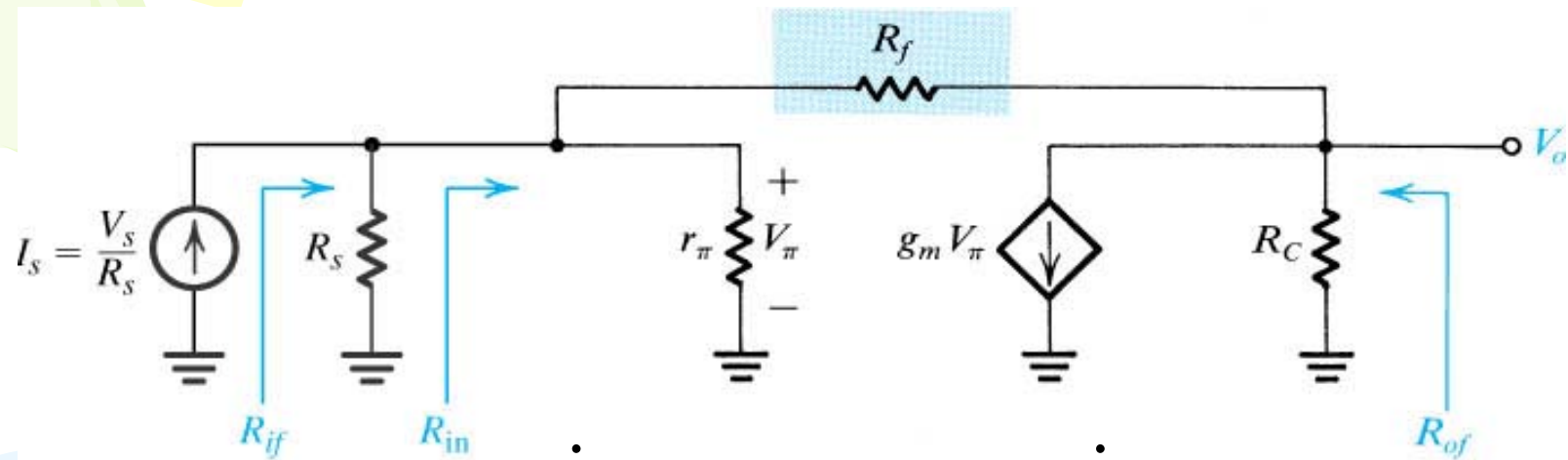
$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$



$$y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0} \quad (c) \quad y_{22} = \frac{i_2}{v_2} \Big|_{v_1=0}$$

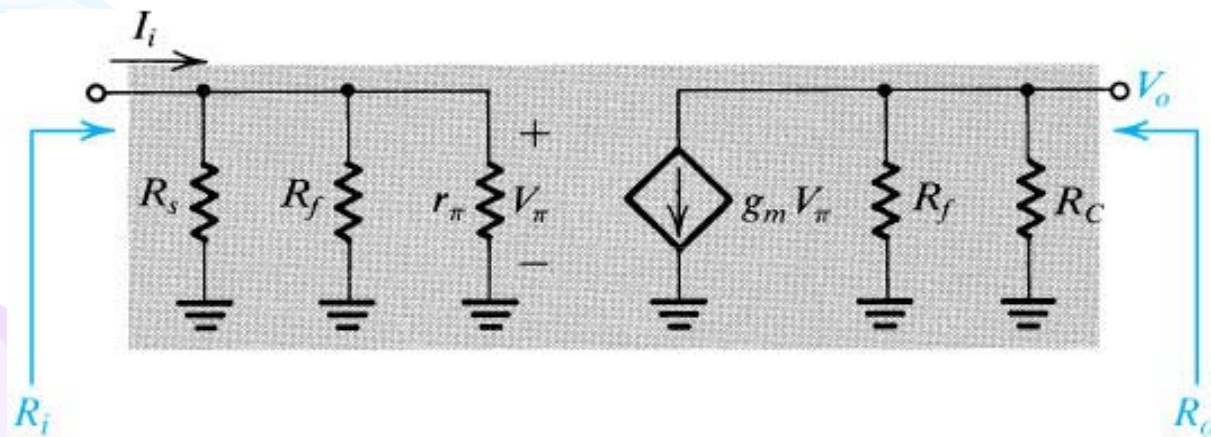

(d)

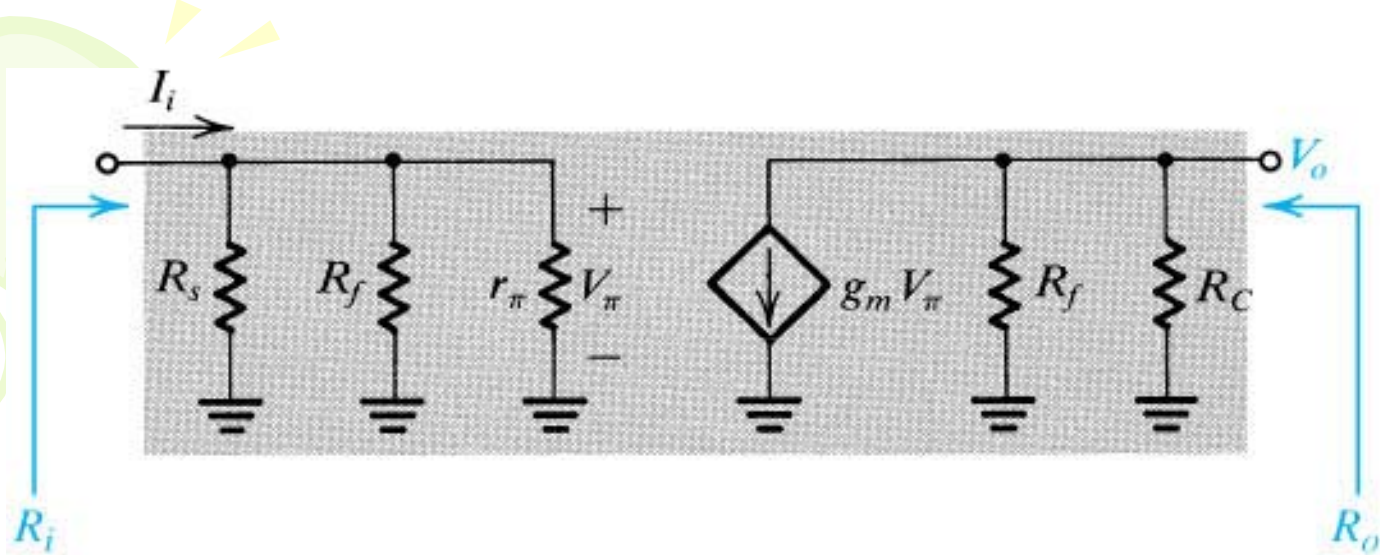


$$R_m = \frac{v_o}{i_i} = \frac{-g_m v_\pi (R_f \parallel R_c)}{v_\pi / (R_f \parallel R_s \parallel r_\pi)} \quad (d) = -358.7k\Omega$$

$$R_i = R_f \parallel R_s \parallel r_\pi = 1.4k$$

$$R_o = R_f \parallel R_c = 4.27k$$

$$\beta = y_{12} = \left. \frac{i_f}{v_o} \right|_{v_s=0} = -\frac{1}{R_f}$$

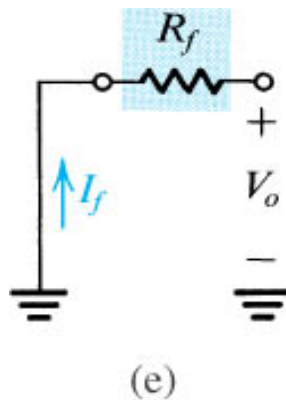


$$A_f \equiv \frac{v_o}{i_s} = R_{mf} = \frac{R_m}{1 + y_{12} R_m} = -41.6k$$

$$R_{if} = \frac{R_i}{1 + y_{12} R_m} = 162.2 = R_s \parallel R_{in}$$

$$R_{of} = \frac{R_o}{1 + y_{12} R_m} = 495$$

Example 8.4

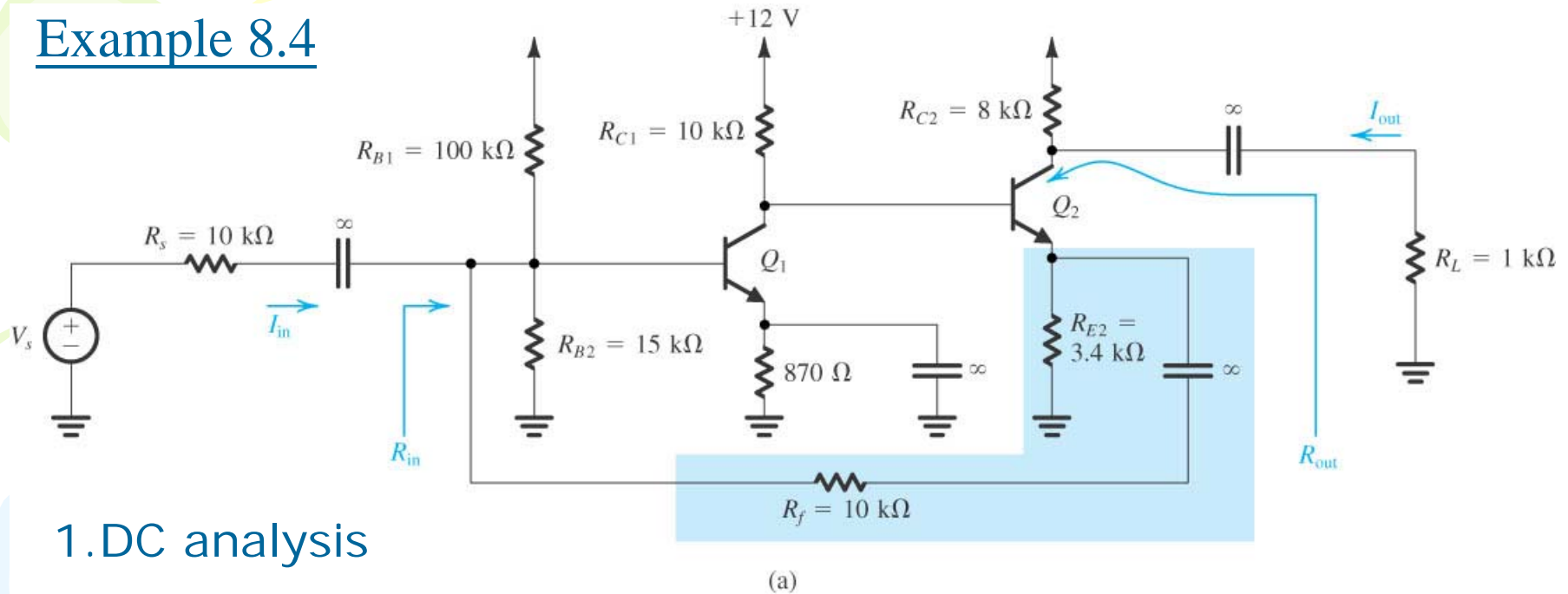

1. DC analysis

$$\frac{15k}{15k + 100k} \times 12V = (100k // 15k)I_{B1} + 0.7 + (1 + \beta)I_{B1} \times 0.87$$

$$I_{B1} = 0.0087mA$$

$$I_{C1} = 0.87mA$$

$$V_{C1} = 12 - 0.87 \times 10k = 3.3V$$

$$I_{E2} = \frac{3.3 - 0.7}{3.4k} = 0.765mA$$

$$g_{m1} = \frac{I_{C1}}{V_T} = 0.0344$$

$$r_{\pi1} = \frac{V_T}{I_{B1}} = 2.9k$$

$$r_{o1} = \frac{75}{I_{C1}}$$

$$g_{m2} = \frac{I_{C2}}{V_T} = 0.030$$

$$r_{\pi2} = \frac{V_T}{I_{B2}} \approx r_{\pi1}$$


$$r_{o2} = \frac{75}{I_{C2}}$$

Shunt-series
current Mixing – current sampling
Amplifier: Current Amplifier
Feedback network: hybrid parameters


$$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$

$$g_{11} = \left. \frac{i_1}{v_1} \right|_{i_2=0}$$

$$g_{22} = \left. \frac{v_2}{i_2} \right|_{v_1=0}$$

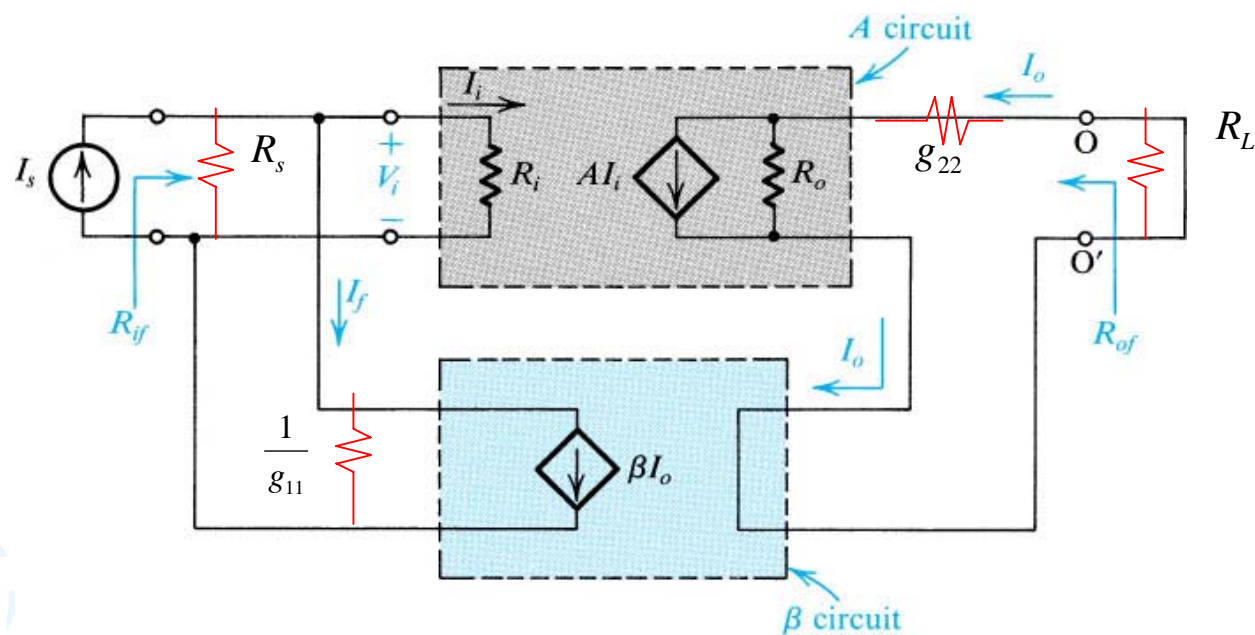



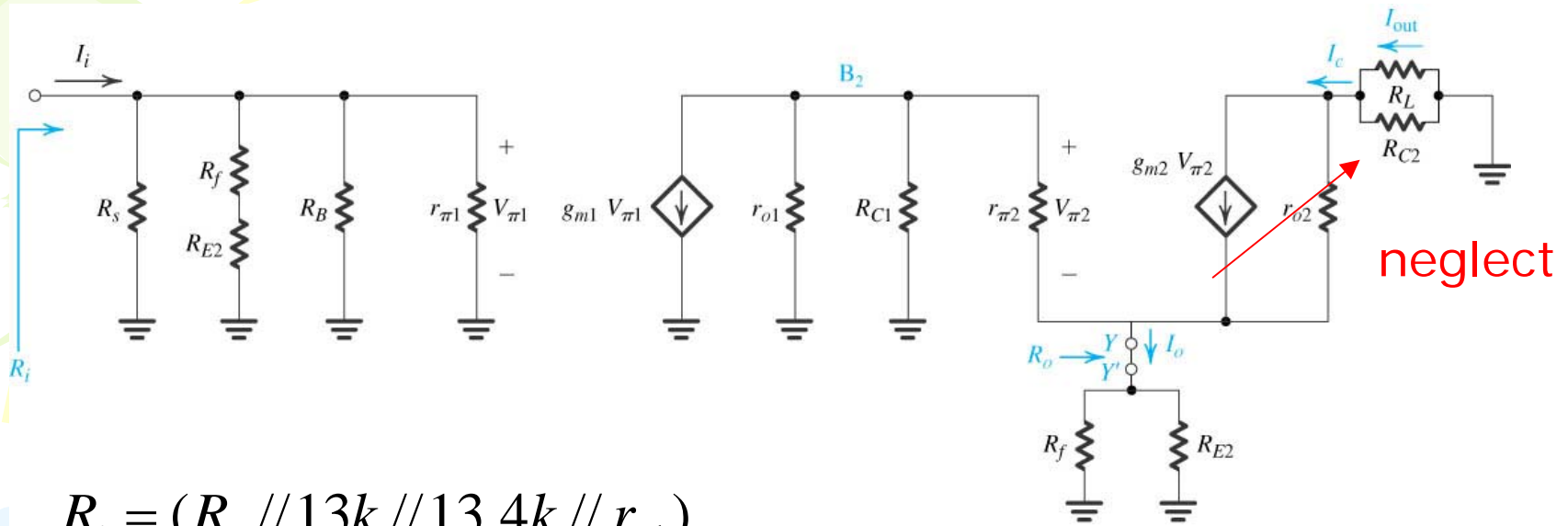


$$R_i = (R_s // 13k // 13.4k // r_{\pi 1})$$

(c)

$$R_{if} = \frac{R_i}{1 + \beta A}$$

$$R_o = r_{e2} + (3.4k // 10k) + \frac{r_{o1} // 10k}{1 + h_{fe}}$$

$$R_{of} = (1 + \beta A) R_o$$

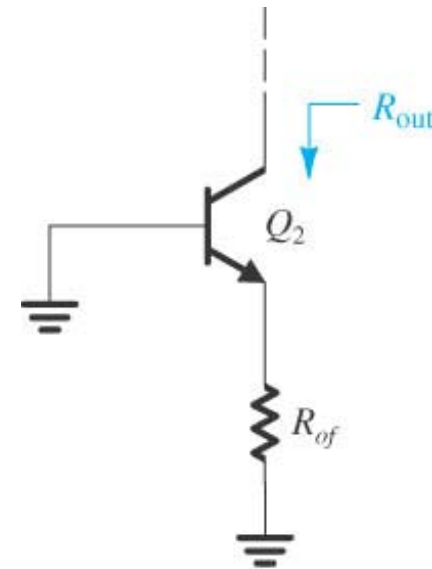

(e)