

Lecture 9

Poles and Zeros

March 30th, 2005

Prof. SeongHwan Cho

2005-03-29

EE301

1

Why Do We Learn Frequency Response?

- Static (DC) signals often do not provide enough information.
 - e.g. voice, video, (still image?)
 - Information is usually stored in time varying signals.
- An easy way to analyze time varying signals is to look at it in the frequency domain.

2005-03-29

EE301

3

Outline

- Meaning of Poles and Zeros
- Analysis of R-C Network
- High frequency model of MOS

2005-03-29

EE301

2

Laplace Transform

- Laplace transform is just one of the many methods to analyze linear system.
- Why Laplace Transform?
 - Differential equations are transformed into algebraic equations.
 - It provides insight. (many techniques are based on s-domain representation of signals)

2005-03-29

EE301

4

Poles and Zeros


- Mathematical Meaning
 - Pole : $D(s_p) = 0$
 - Zero : $N(s_z) = 0$
- Analytical Meaning
 - Pole
 - Determines the stability of the system
 - System Pole determines the natural/transient response
 - Zero
 - Determines the transient behavior
- Physical Meaning from Circuit Standpoint
 - Pole:
 - A low impedance path to ground. (single-ended)
 - Zero:
 - A short to the input source.
 - A multiple path from source to the output.
 - + α

2005-03-29

EE301

5

Analyzing System with Poles and Zeros

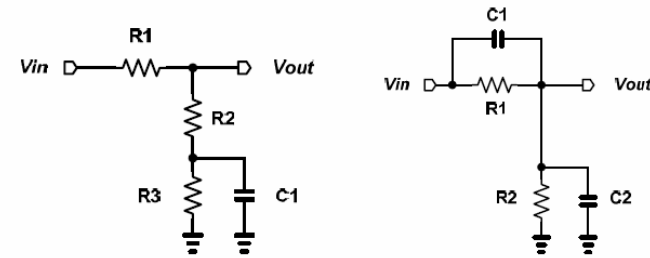



2005-03-29

EE301

7

Bode Plot

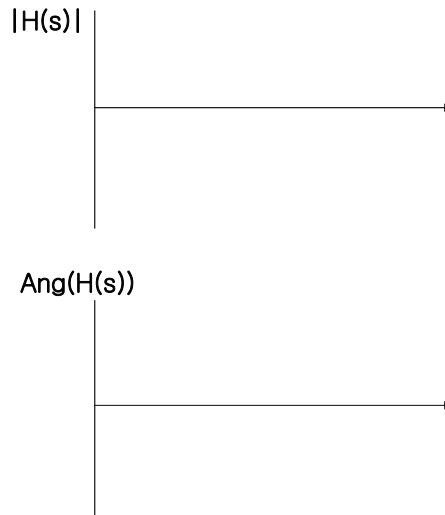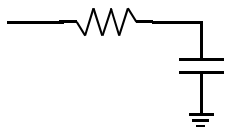- Poles:
 - @pole \rightarrow -3dB
 - 20dB/decade
 - $\pi/4$ /decade
 - $\pi/2$ total phase shift
- Zeros:
 - @zero \rightarrow +3dB
 - +20dB/decade
 - + $\pi/4$ /decade
 - + $\pi/2$ total phase shift




2005-03-29

EE301

6

Miller Theorem

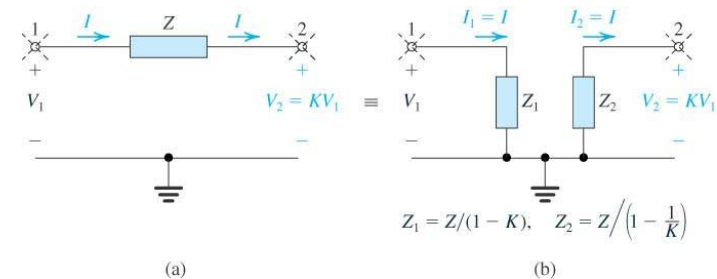


2005-03-29



EE301

8

Impedance Multiplication

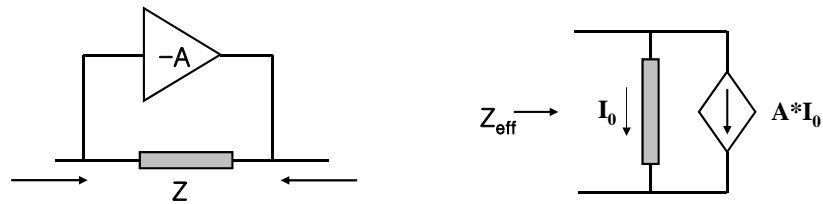

Small-Signal High Frequency Model

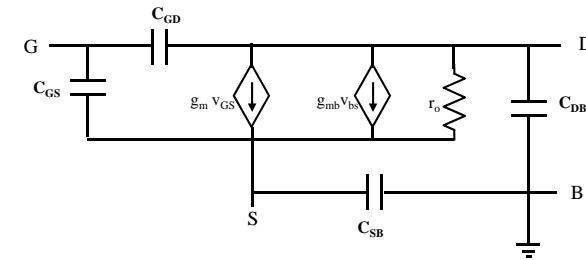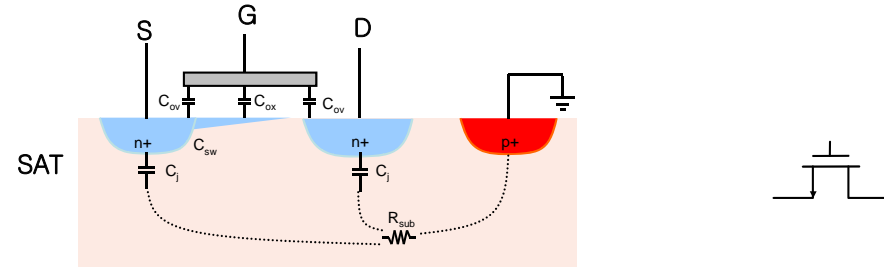

2005-03-29

EE301



9

2005-03-29

EE301

11

High Frequency Model of MOS

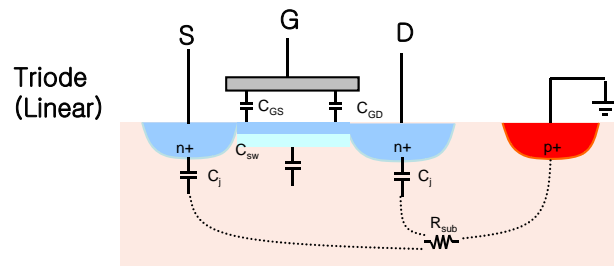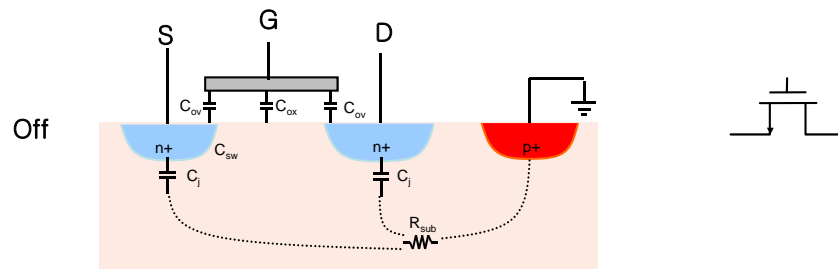


2005-03-29

EE301

10

MOS Capacitance

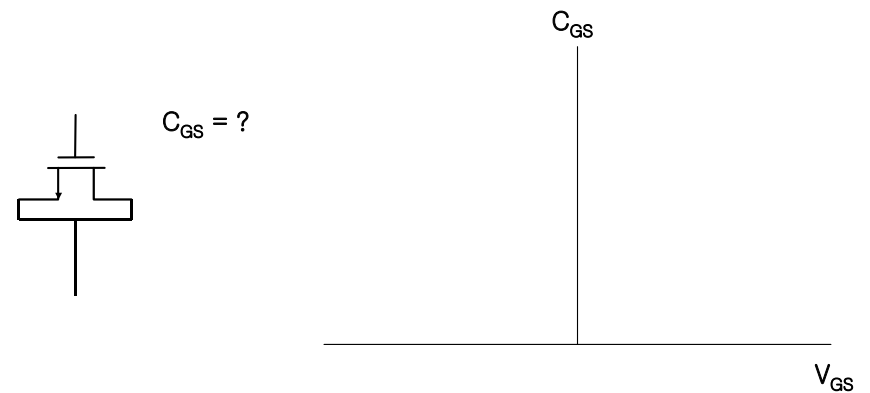

2005-03-29

EE301

12