

Lecture 6 – 7

Differential Amplifier



March 21, 2005

Prof. SeongHwan Cho

2005-03-20

EE301

1

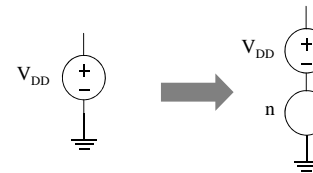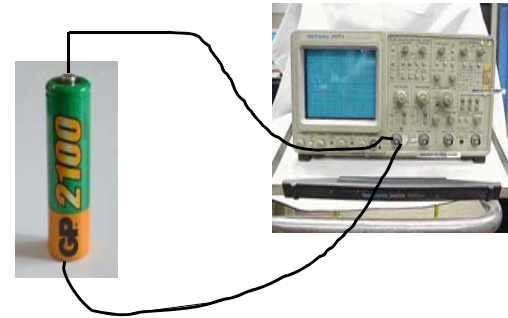

Noise degrades information quality!

2005-03-20

EE301

3

Outline

Why differential amplifier?

Differential amplifier


- Large signal analysis
- Small signal analysis
- Gain
- CMRR
- Active load

2005-03-20

EE301

2

Noise in Single-Ended Systems

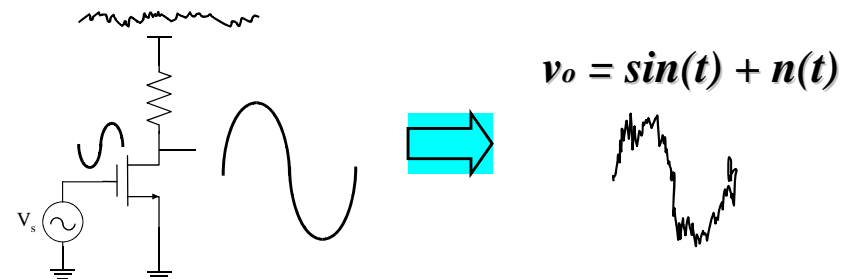

$$\begin{aligned} \because V_o &= \tilde{V}_{DD} - R_D I_D = V_{DD} + n(t) - R_D I_D \\ &= V_{DD} + n(t) - R_D (g_m \cdot v_s) \end{aligned}$$


How can we get rid of this noise?

2005-03-20

EE301


4

Getting rid of noise

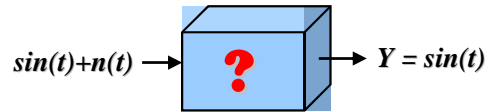

Need to subtract $n(t)$,
but not the signal.
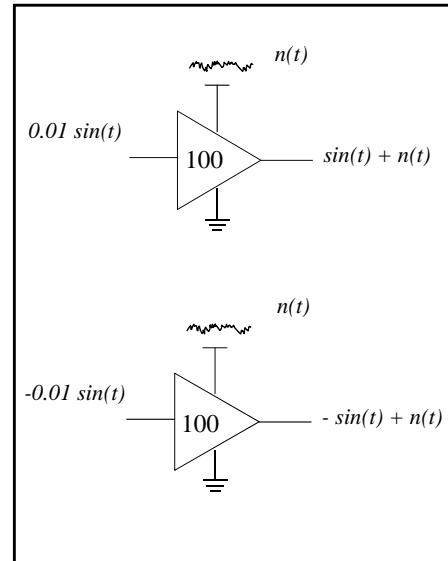
$$\begin{aligned} Y_p &= Y_{\text{signal}} + n(t) \\ - Y_n &= -Y_{\text{signal}} + n(t) \\ \hline Y_p - Y_n &= 2 Y_{\text{signal}} \end{aligned}$$




2005-03-20

EE301

5

Differential Signaling

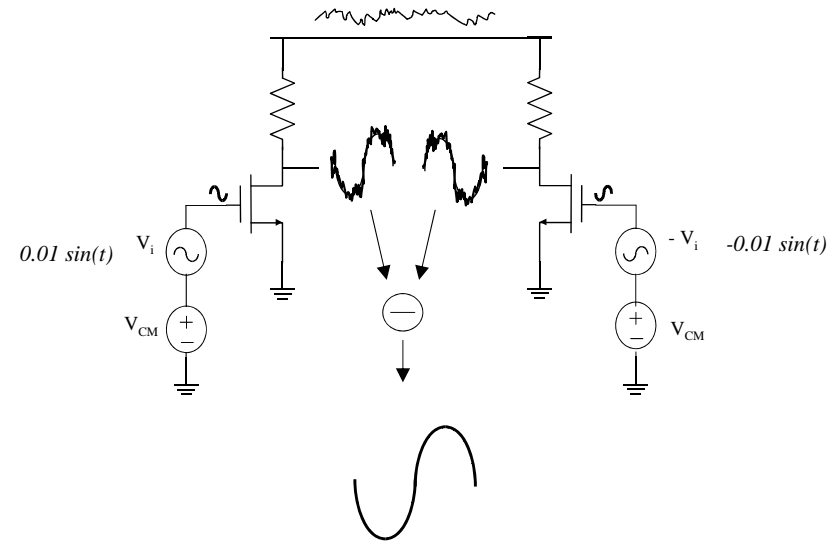


2005-03-20

EE301

7

Differential Signaling

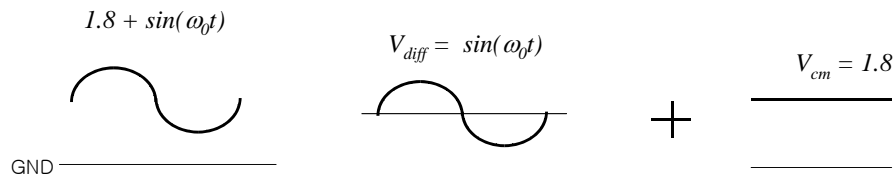

$$V_{\text{signal}} = V_{\text{diff}} + V_{\text{cm}}$$

$$V_{\text{diff}} = V_p - V_n$$

$$V_{\text{CM}} = 0.5(V_p + V_n)$$

$$V_p = 0.5 V_{\text{signal}} + V_{\text{cm}}$$


$$V_n = -0.5 V_{\text{signal}} + V_{\text{cm}}$$

2005-03-20

EE301

6

How about non-common mode noise?

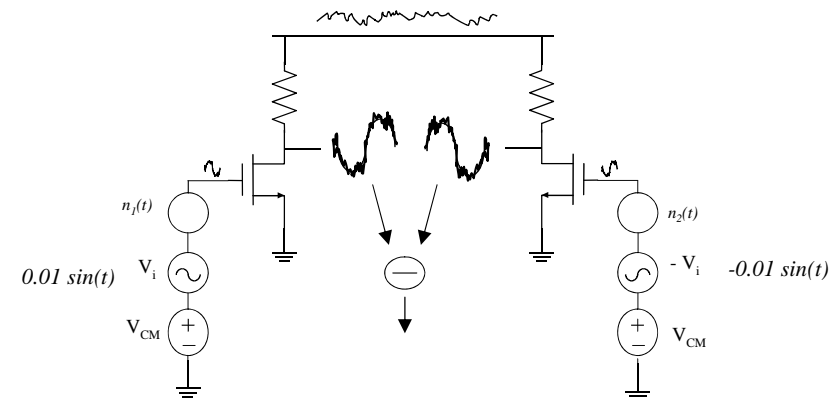


Differential amplifier is ONLY immune to common-mode noise !

2005-03-20

EE301

8

Differential Pair Configuration

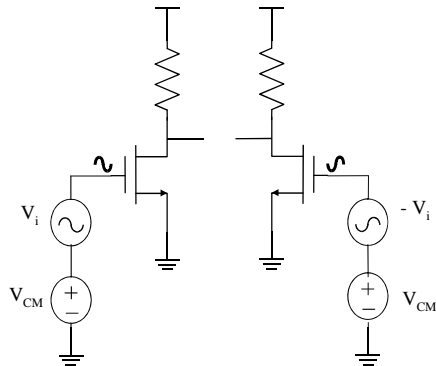

< Differential Gain >

$$\begin{aligned} g_m R_D &\propto \sqrt{I} \cdot R_D \\ &\propto (V_{GS} - V_T) \cdot R_D \\ &\propto (V_{CM} - V_T) \cdot R_D \end{aligned}$$

Gain is dependent on common mode voltage.


How do we make gain independent of common mode voltage ?

2005-03-20

EE301

9

Differential Pair Configuration

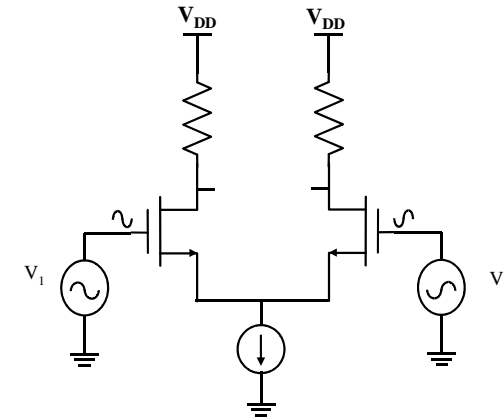


Differential gain is independent of common mode voltage.

2005-03-20

EE301

11

Differential Pair Configuration

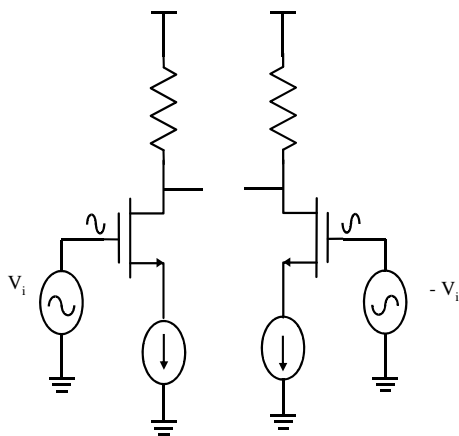

What is the gain?


$$-g_m R_D ?$$

2005-03-20

EE301

10

Common-mode Input Voltage

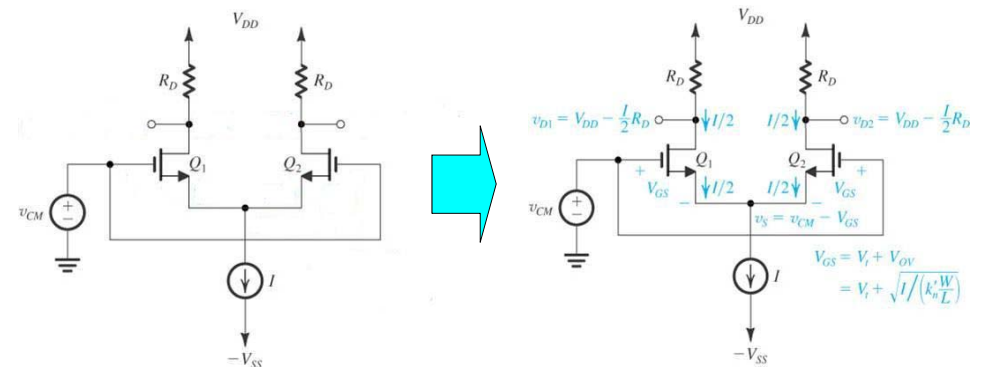


2005-03-20

EE301

12

Differential Input Voltage

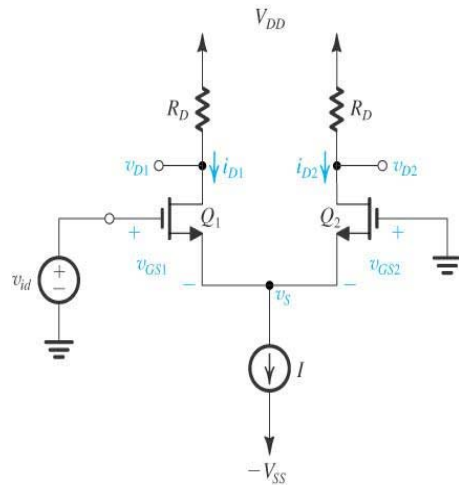

With v_{id} positive

$v_{GS1} > v_{GS2}$, $i_{D1} > i_{D2}$, and $v_{D1} < v_{D2}$
 $(v_{D2} - v_{D1})$ will be positive.

With v_{id} negative


$v_{GS1} < v_{GS2}$, $i_{D1} < i_{D2}$, and $v_{D1} > v_{D2}$
 $(v_{D2} - v_{D1})$ will be negative.

2005-03-20

EE301

13

Large Signal Operation

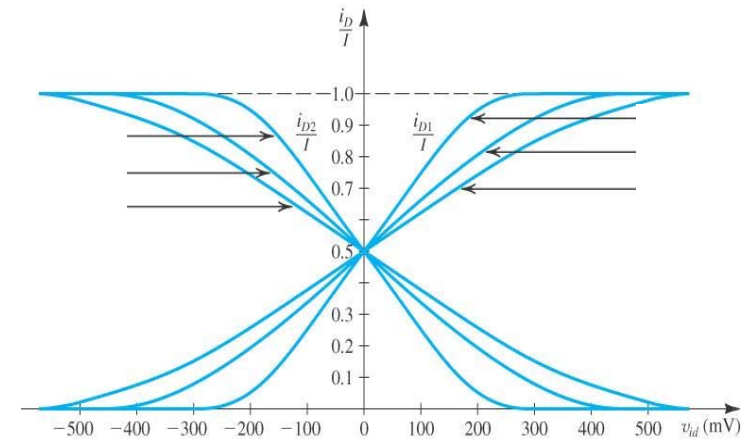



The linear range of operation of the MOS differential pair can be extended by reducing (W/L) .

2005-03-20

EE301

15

Large Signal Operation

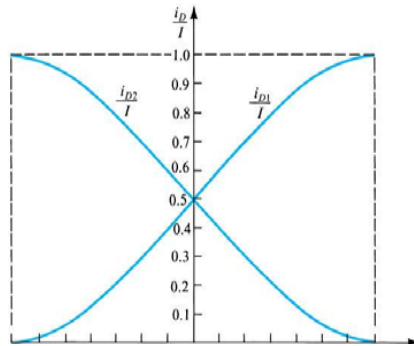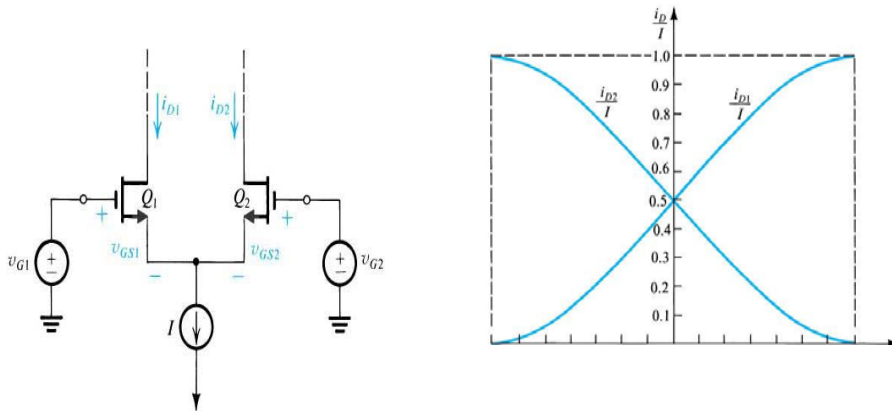


2005-03-20

EE301

14

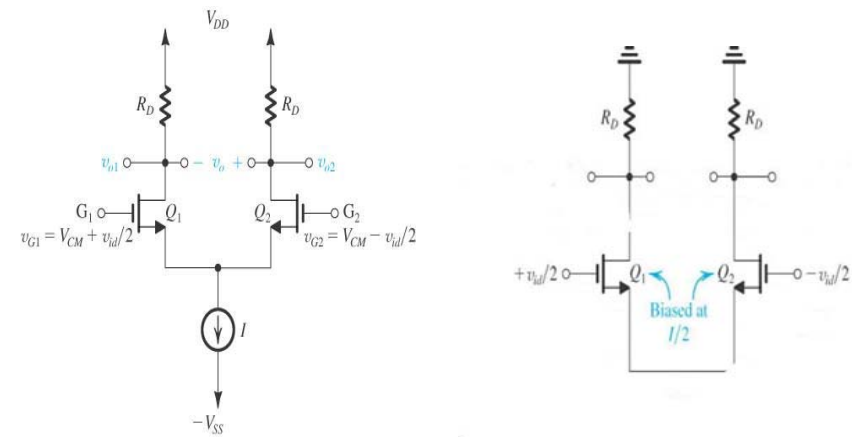Differential Gain in Small Signal Operation




2005-03-20

EE301

16

Virtual Ground

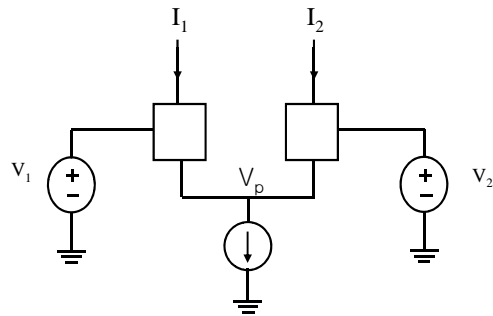


For differential input, V_p does not change only if the circuit is **linear**.
(refer to Razavi pp. 114)

2005-03-20

EE301

17

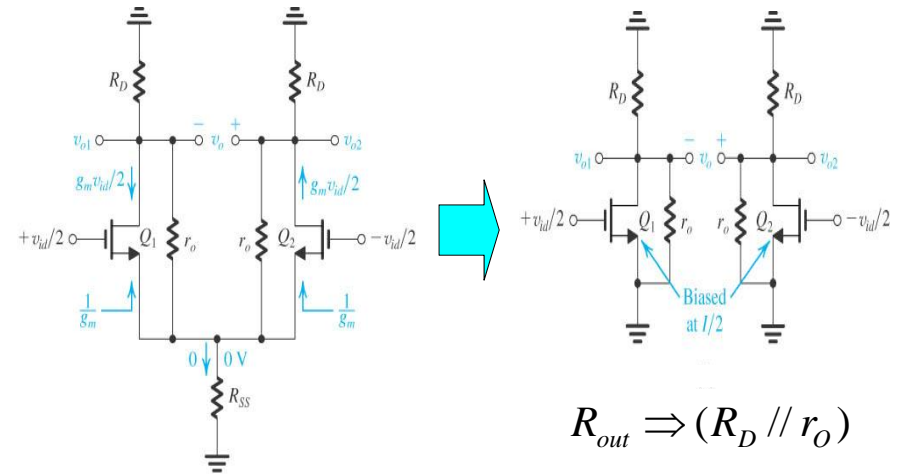Differential Gain due to Output Resistance




2005-03-20

EE301

19

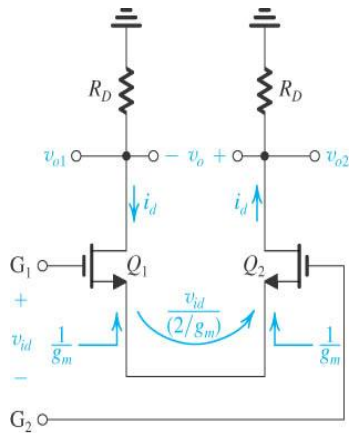Differential Gain in Small Signal Operation




$$A_d = \frac{v_{o2} - v_{o1}}{v_{id}} = g_m R_D$$

2005-03-20

EE301

18

Common-mode Gain

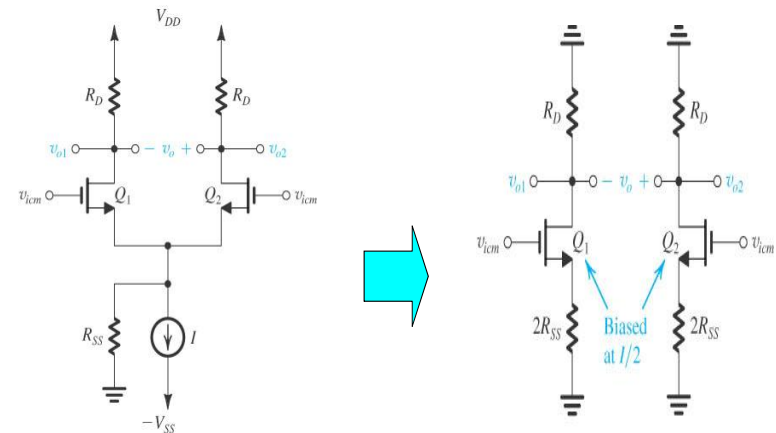

Common-mode gain : differential & single-ended


2005-03-20

EE301

20

Common-mode Rejection Ratio


$$CMRR = \left| \frac{A_d}{A_{CM}} \right|$$

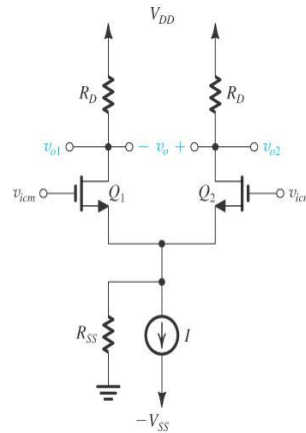

CMRR can be considered as Signal-to-Noise Ratio!

Offset Voltage due to Mismatch

- Mismatch in R

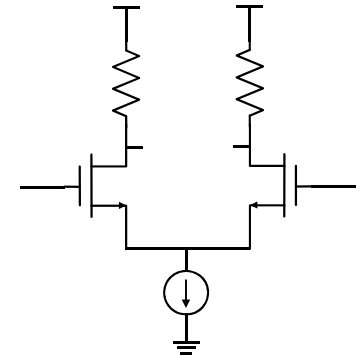

- Mismatch in W/L

Input Offset Voltage

- Input offset voltage


$$V_{OS} = V_O / A_d$$

(V_O: output voltage when V_{in} = 0)


- Mismatch

Offset Voltage due to Mismatch

- Mismatch in V_{th}

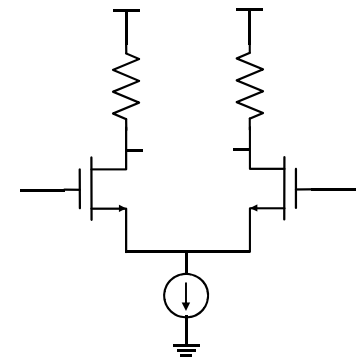

Differential Amplifier with active load

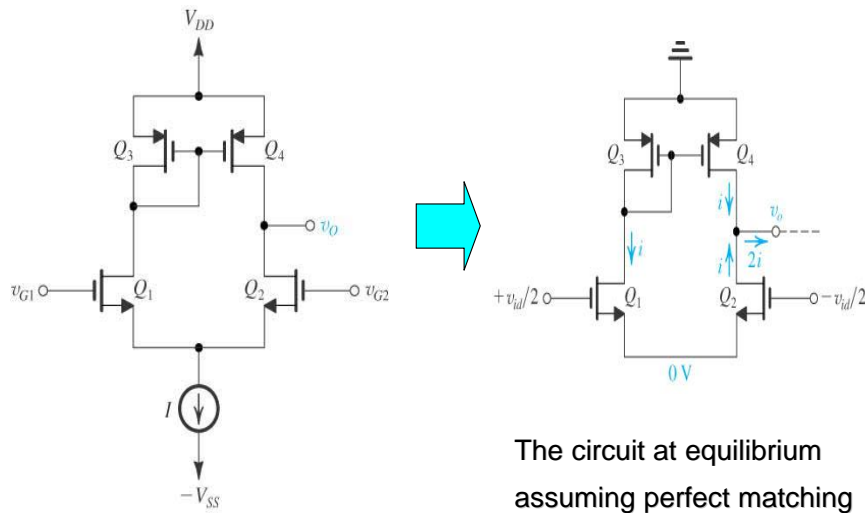


2005-03-20

EE301

25

Determining the Output Resistance

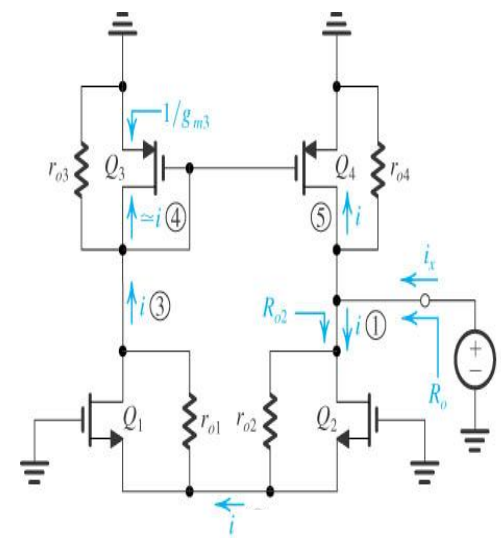


2005-03-20

EE301

27

Determining the Transconductance

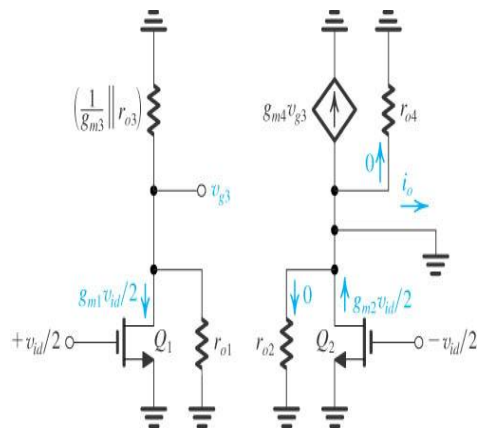


2005-03-20

EE301

26

Common-mode Gain and CMRR

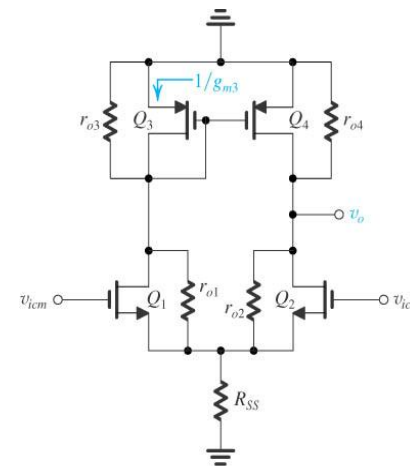

2005-03-20

EE301

28