

The background features several large, stylized, overlapping swirls in light green, light blue, and light purple. Scattered throughout are numerous small, yellow, starburst-like shapes, some of which are larger and more prominent than others, creating a dynamic and celebratory feel.


Lecture 10

Frequency response

Three balloons (green, blue, and purple) with yellow streamers and triangular flags are positioned on the left side of the slide.

topics

- Bode diagram
- BJT's Frequency response
- MOSFET Frequency response


$$v_i(t) = V_i \sin \omega t$$

Amplifier

$$v_o(t) = V_o \sin(\omega t + \phi)$$

Magnitude: $\frac{V_o}{V_i}$ Phase: ϕ

$$T(s) = \frac{V_o(s)}{V_i(s)}$$

$$s = \sigma + j\omega \Rightarrow s = j\omega$$

Steady-state response

$$T(\omega) = \frac{V_o(\omega)}{V_i(\omega)}$$

Magnitude: $\frac{|V_o(j\omega)|}{|V_i(j\omega)|}$ Phase: $\frac{\angle V_o(j\omega)}{\angle V_i(j\omega)}$


dB (decibel)= Decimal + Bell

$$dB \equiv 10 \log_{10} \frac{p_1}{p_2}$$

$$\because p = i^2 z = \frac{v^2}{z}$$


$$\Rightarrow dB = 20 \log_{10} \frac{v_1}{v_2} = 20 \log_{10} \frac{i_1}{i_2}$$

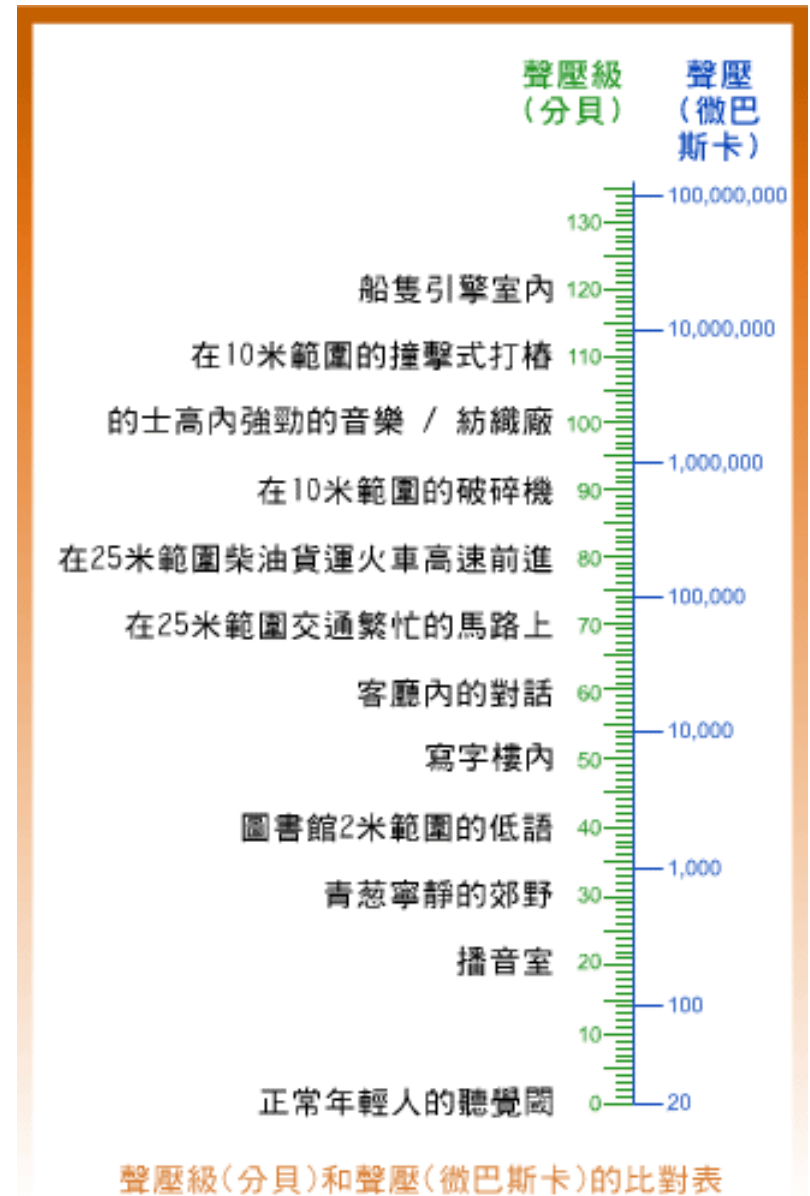Human hearing frequency zone : 10Hz~24kHz
Most Sensitive frequency zone : 2kHz~5kHz




圖表來自http://www.epd.gov.hk/epd/noise_education/web/CHI_EPD_HTML/m1/intro_5.html

Logarithmic coordinate

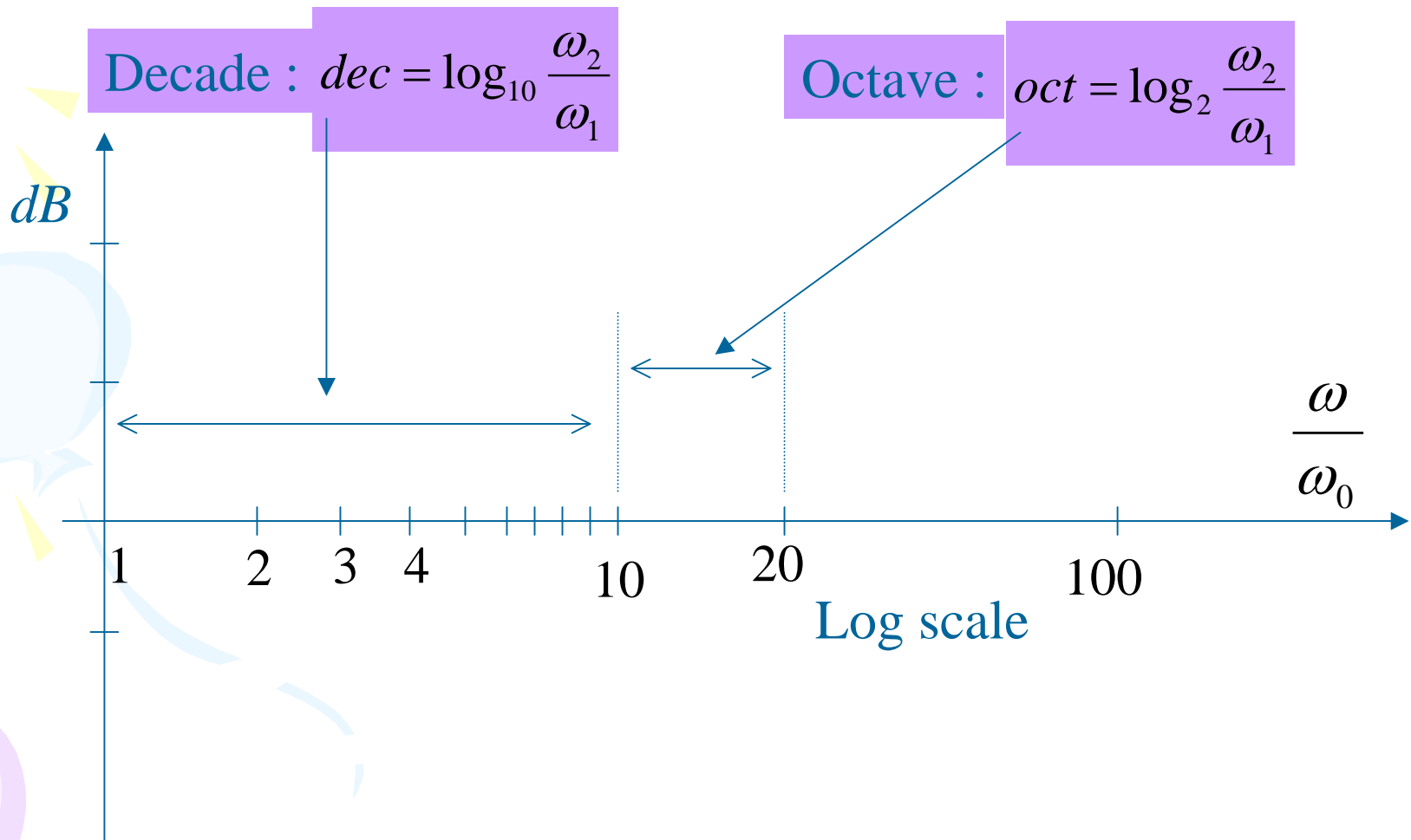

Example(low pass)

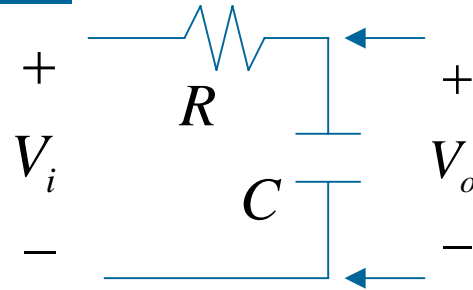

$$V_o = \frac{1/sC}{R + 1/sC} V_i \Rightarrow T(\omega) = \frac{1}{1 + (j\omega)RC}$$

$$\text{let } \omega_0 = \frac{1}{RC} \Rightarrow T(\omega) = \frac{1}{1 + (j\omega)RC} = \frac{1}{1 + \left(\frac{j\omega}{\omega_0}\right)}$$

$$\text{if } \omega = \omega_0 \Rightarrow |T(\omega)| = \frac{1}{\sqrt{2}}$$

$$\Rightarrow \angle T(\omega) = 0 - \tan^{-1} 1 = -45^\circ$$

$$T(\omega) = \frac{1}{1 + (\frac{s}{\omega_0})} = \frac{1}{1 + (\frac{j\omega}{\omega_0})}$$

Magnitude:

$$\left| (1 + j\frac{\omega}{\omega_0})^{-1} \right|_{dB} = -20 \log \sqrt{1 + (\frac{\omega}{\omega_0})^2}$$

$$= -10 \log [1 + (\frac{\omega}{\omega_0})^2]$$

$$\omega \ll \omega_0 \Rightarrow \frac{\omega}{\omega_0} \approx 0$$

$$\Rightarrow dB = -10 \log 1 = 0$$

$$\omega \gg \omega_0 \Rightarrow 1 + j\frac{\omega}{\omega_0} \approx \frac{\omega}{\omega_0}$$

$$\Rightarrow dB \approx -20 \log \frac{\omega}{\omega_0}$$

$$dB = -[20 \log \omega - 20 \log \omega_0]$$

$$\omega = \omega_0 \Rightarrow 1 + j1 \Rightarrow dB = -10 \log 2 = -3.01$$

Phase:

$$\angle(1 + j\frac{\omega}{\omega_0}) = 0^\circ - \tan^{-1} \frac{\omega}{\omega_0}$$

$$\omega \ll \omega_0 \Rightarrow \frac{\omega}{\omega_0} \approx 0 \Rightarrow \angle T(\omega) \approx \tan^{-1} 0 = 0^\circ$$

$$\omega \gg \omega_0 \Rightarrow \frac{\omega}{\omega_0} \approx \infty \Rightarrow \angle T(\omega) \approx -\tan^{-1} \infty = -90^\circ$$

$|T(\omega)|(dB)$

$$T(\omega) = \frac{\omega_0}{\omega_0 + s}$$

0dB

0.1

1

10

$\frac{\omega}{\omega_0}$

$-20dB / decade$

$\angle T(\omega)$

180°


90°

-90°


-180°

$$\omega = \omega_0 \Rightarrow -45^{\circ}$$

$\frac{\omega}{\omega_0}$

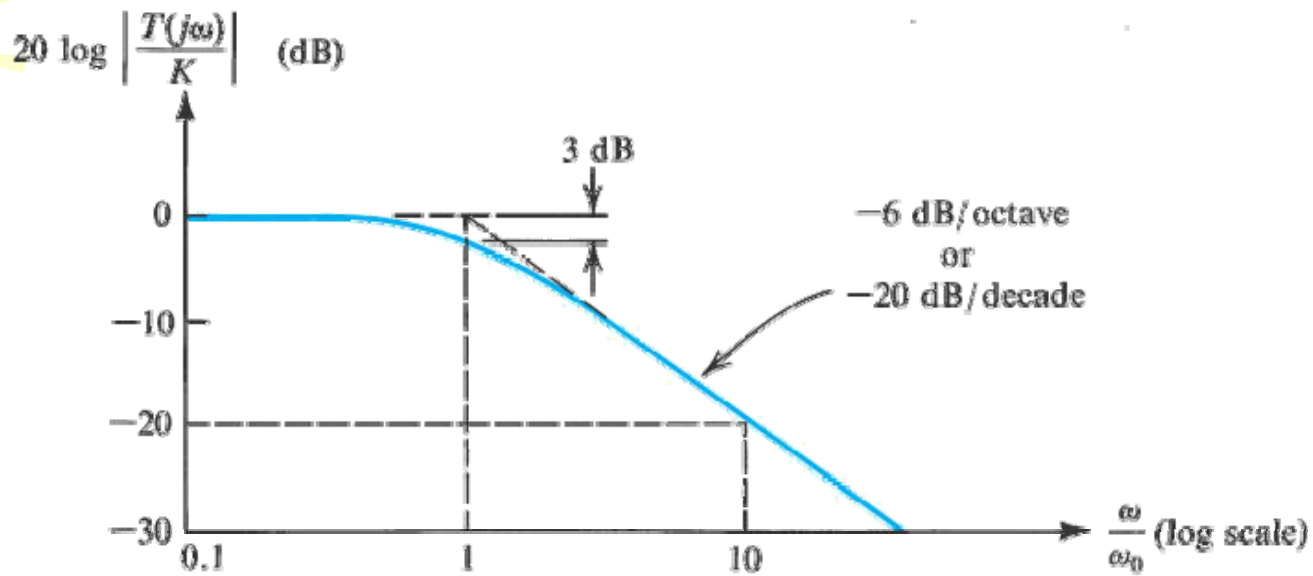


(a)

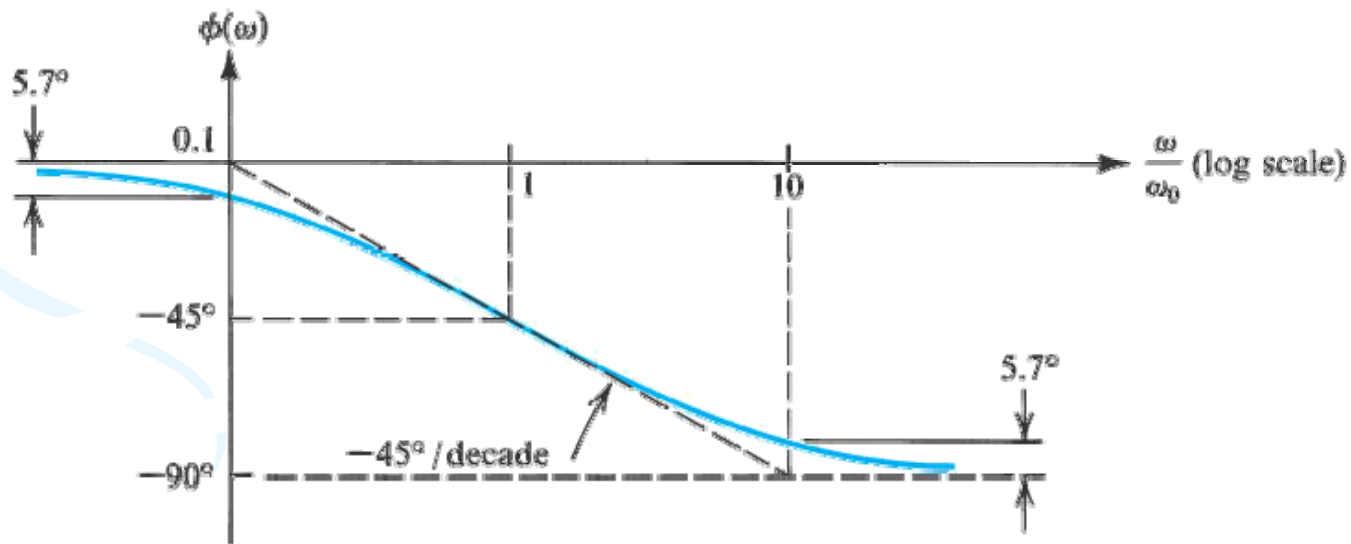

(b)

Example(high pass)

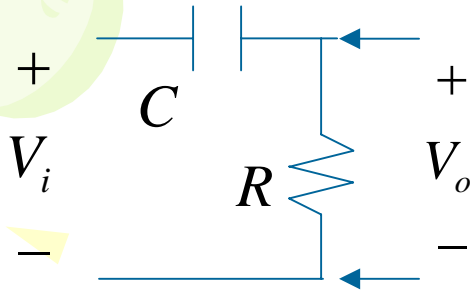

$$V_o = \frac{R}{R + 1/sC} V_i \Rightarrow T(\omega) = \frac{j\omega RC}{1 + (j\omega)RC}$$

$$\text{let } \omega_0 = \frac{1}{RC} \Rightarrow T(\omega) = \frac{j\omega RC}{1 + (j\omega)RC} = \frac{(\frac{j\omega}{\omega_0})}{1 + (\frac{j\omega}{\omega_0})}$$

$$\text{if } \omega = \omega_0 \Rightarrow |T(\omega)| = \frac{1}{\sqrt{2}}$$

$$\Rightarrow \angle T(\omega) = 90 - \tan^{-1} 1 = 45^\circ$$

$$T(s) = \frac{s}{s + \omega_0} \quad T(\omega) = \frac{j\omega}{j\omega + \omega_0}$$

Magnitude:

$$\left| \frac{j\omega}{j\omega + \omega_0} \right|_{dB} = 20\log \omega - 20\log \sqrt{\omega^2 + \omega_0^2}$$

$$= 20\log \omega - 10\log[\omega^2 + \omega_0^2]$$

$$\omega \gg \omega_0 \Rightarrow 20\log \frac{1}{1 + \frac{\omega_0}{j\omega}}$$

$$\Rightarrow -20\log(1 + \frac{\omega_0}{j\omega})$$

$$\Rightarrow dB = -20\log 1 = 0$$

Phase:

$$\angle \frac{j\omega}{j\omega + \omega_0} = 90 - \tan^{-1} \frac{\omega}{\omega_0}$$

$$\omega \gg \omega_0 \Rightarrow \frac{\omega}{\omega_0} \approx \infty \Rightarrow \angle T(\omega) \approx 90 - \tan^{-1} \infty = 0^\circ$$

$$\omega \ll \omega_0 \Rightarrow \frac{\omega}{\omega_0} \approx 0 \Rightarrow \angle T(\omega) \approx 90 - \tan^{-1} 0 = 90^\circ$$

$$\omega \ll \omega_0 \Rightarrow dB \approx 20\log \frac{\omega}{\omega_0}$$


$$dB = 20\log \omega - 20\log \omega_0$$

$$\omega = 0.1\omega_0 \Rightarrow dB = 20\log 0.1 = -20$$

$$\omega = \omega_0 \Rightarrow \frac{1}{1 + j1} \Rightarrow dB = -20\log \sqrt{2} = -3.01$$

$|T(\omega)|(dB)$

$$T(s) = \frac{s}{s + \omega_0}$$

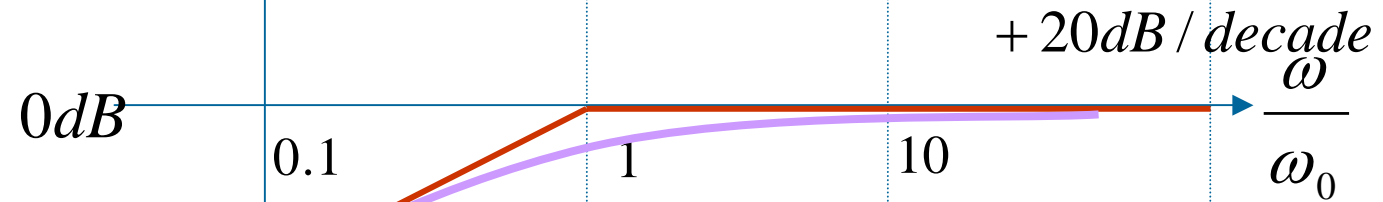

$\angle T(\omega)$

180^0

90^0


-90^0

-180^0


$$\omega = \omega_0 \Rightarrow 45^0$$

$\frac{\omega}{\omega_0}$


$\frac{\omega}{\omega_0}$	$\angle T(\omega)$
0.1	90
1	45
10	0

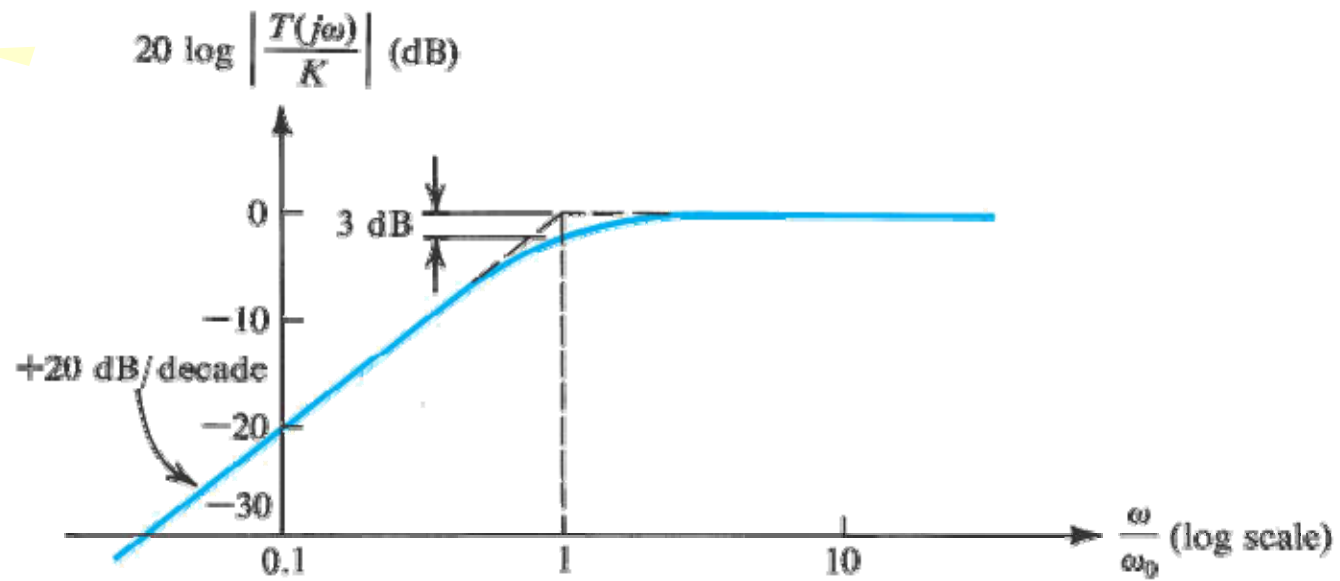

(a)

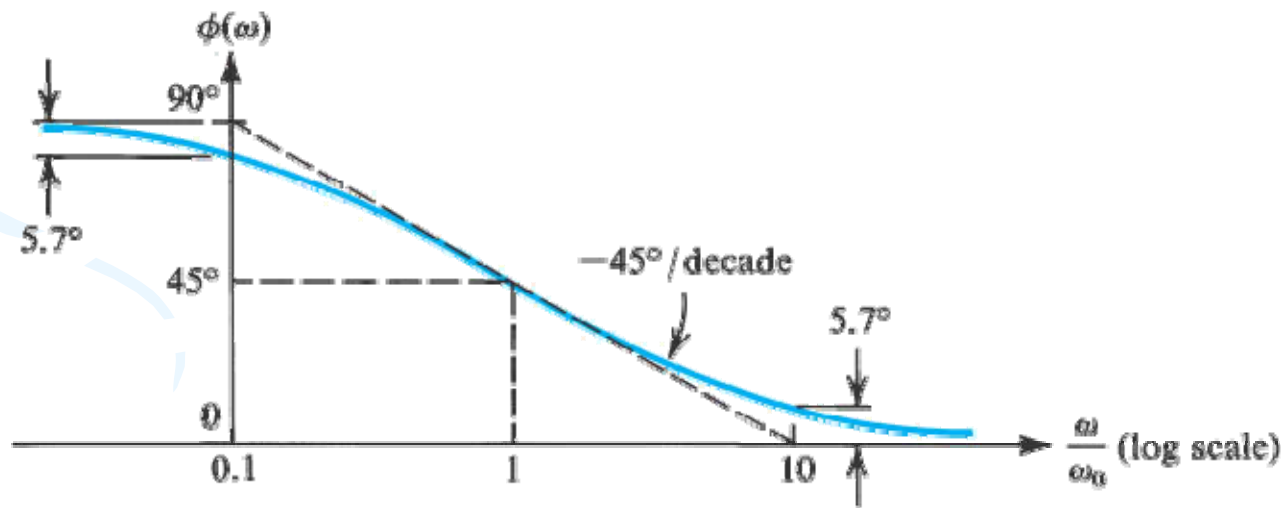

(b)

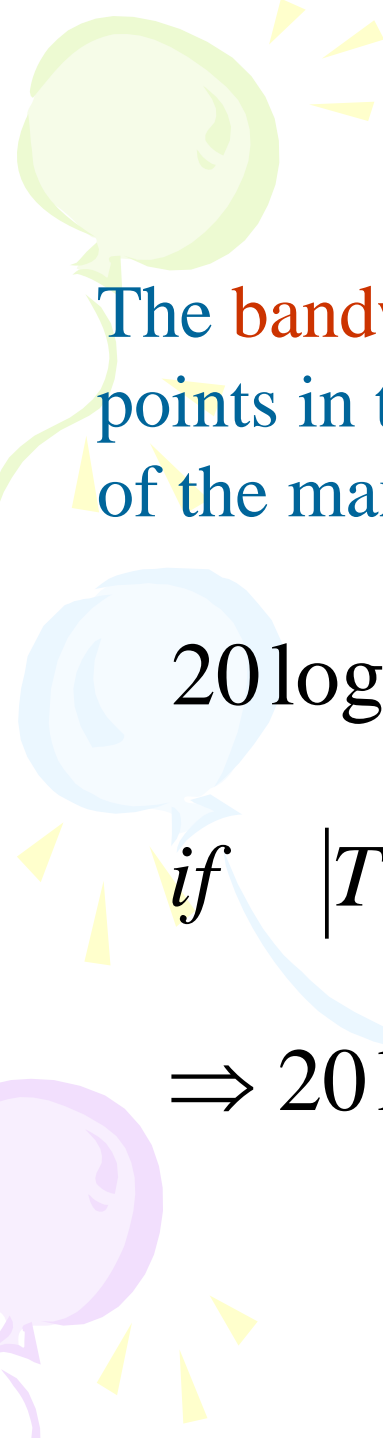
$$dB \equiv 20 \log |T(\omega)|$$


The **bandwidth** represents the distance between the two points in the frequency domain where the signal is $\frac{1}{\sqrt{2}}$ of the maximum signal strength.

$$20 \log |T(\omega)|$$

$$\text{if } |T(\omega)| = \frac{1}{\sqrt{2}}$$

$$\Rightarrow 20 \log |T(\omega)| = 10 \log 2 = 3dB$$


$\text{if } \omega = \omega_0 \Rightarrow |T(\omega)| = \frac{1}{\sqrt{2}}$



BJT high frequency model

Splitting resistance (refinement the lumped-component circuit)

Depletion capacitance

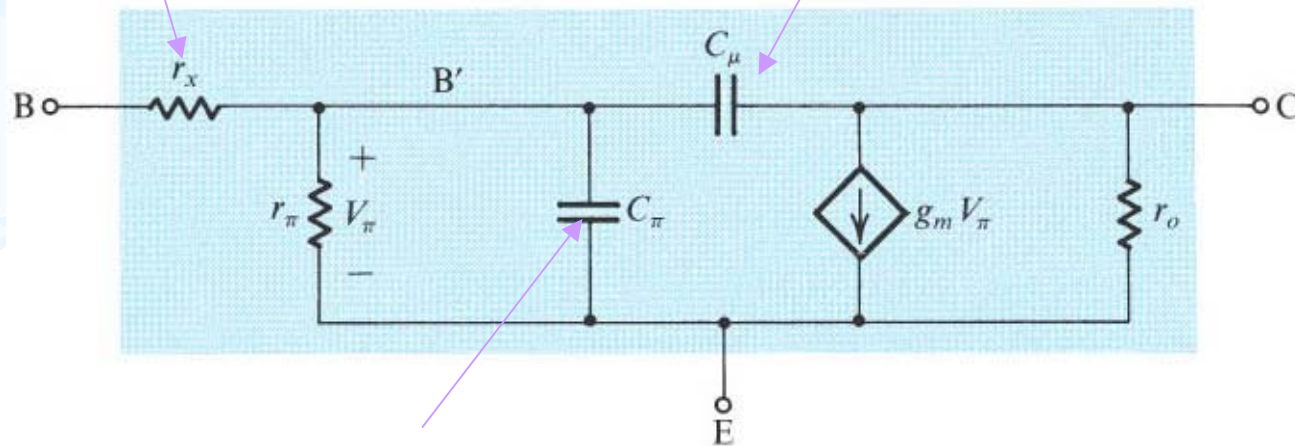

$$C_\pi \gg C_\mu$$

Emitter-base capacitance
= diffusion capacitance + Base-Emitter junction capacitance


KTC9013 Technical data

ELECTRICAL CHARACTERISTICS ($T_a=25^\circ\text{C}$)

CHARACTERISTIC	SYMBOL	TEST CONDITION	MIN.	TYP.	MAX.	UNIT
Collector Cut-off Current	I_{CBO}	$V_{CB}=35\text{V}, I_E=0$	-	-	0.1	μA
Emitter Cut-off Current	I_{EBO}	$V_{EB}=5\text{V}, I_C=0$	-	-	0.1	μA
DC Current Gain	$h_{FE}(\text{Note})$	$V_{CE}=1\text{V}, I_C=50\text{mA}$	64	-	246	
Collector-Emitter Saturation Voltage	$V_{CE(\text{sat})}$	$I_C=100\text{mA}, I_B=10\text{mA}$	-	0.1	0.25	V
Base-Emitter Voltage	V_{BE}	$I_C=100\text{mA}, V_{CE}=1\text{V}$	-	0.8	1.0	V
Transition Frequency	f_T	$V_{CE}=6\text{V}, I_C=20\text{mA}, f=100\text{MHz}$	140	-	-	MHz
Collector Output Capacitance	C_{ob}	$V_{CB}=6\text{V}, I_E=0, f=1\text{MHz}$	-	7.0	-	pF

Note : h_{FE} Classification D:64 ~ 91, E:78 ~ 112, F:96 ~ 135,
 G:118 ~ 166, H:144 ~ 202, I:176 ~ 246

How to find C_π by datasheet ?

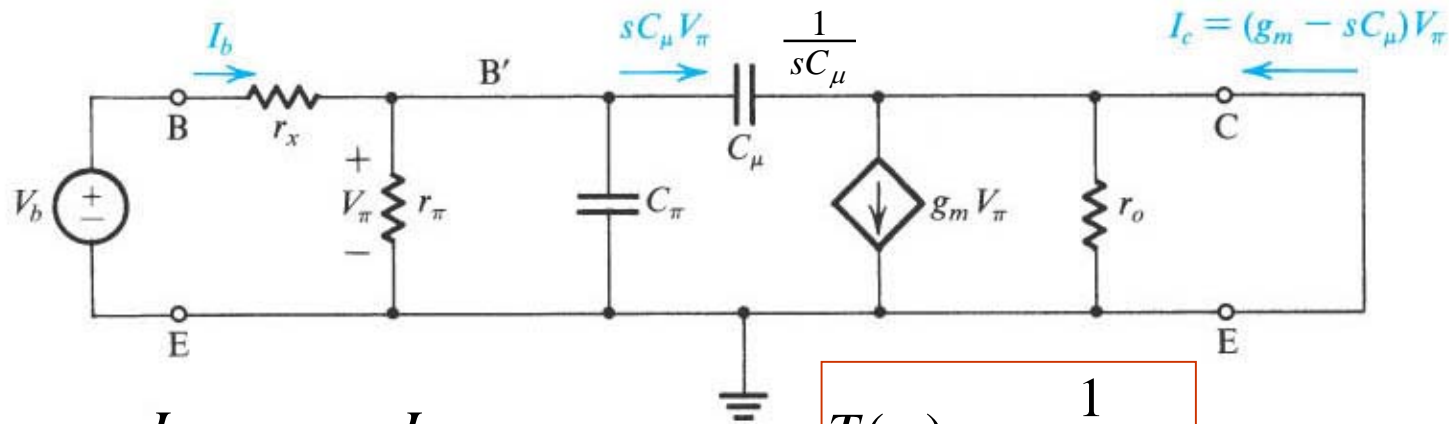

$$h_{fe} \equiv \frac{I_c}{I_b} \Leftrightarrow \beta = \frac{I_c}{I_b}$$

$$T(\omega) = \frac{1}{1 + \left(\frac{s}{\omega_0}\right)}$$

$$I_c = g_m V_\pi - \frac{V_\pi}{1/sC_\mu} = (g_m - sC_\mu)V_\pi$$

3-dB frequency


$$\omega_\beta = \frac{1}{(C_\pi + C_\mu)r_\pi}$$

$$I_b = \frac{V_\pi}{(r_\pi // C_\pi // C_\mu)}$$

$$h_{fe} \equiv \frac{I_c}{I_b} = \frac{g_m - sC_\mu}{1/r_\pi + s(C_\pi + C_\mu)}$$

Low frequency β
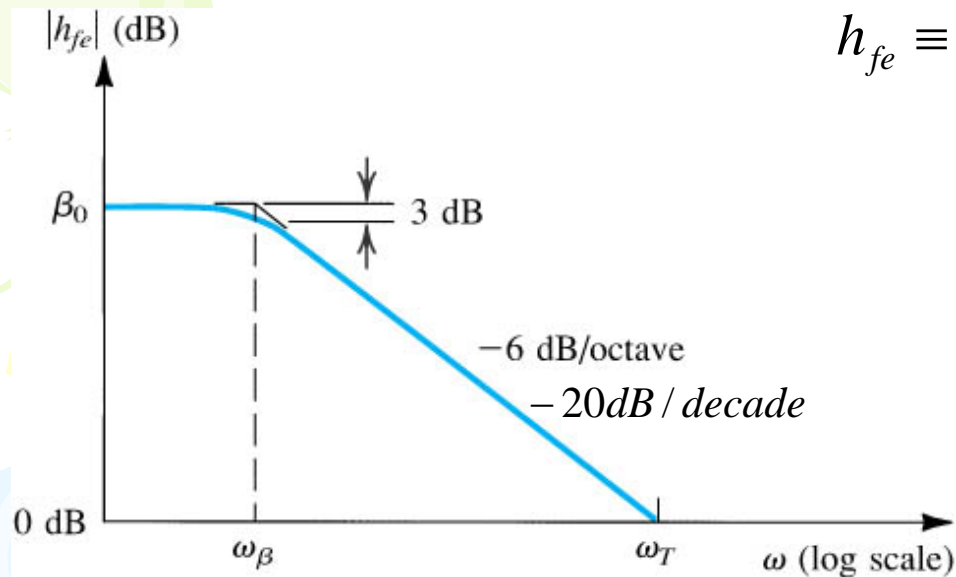
$$\Rightarrow h_{fe} \approx \frac{g_m r_\pi}{1 + s(C_\pi + C_\mu)r_\pi} = \frac{\beta_0}{1 + s(C_\pi + C_\mu)r_\pi}$$



$$h_{fe} \equiv \frac{I_c}{I_b} = \frac{\beta_0}{1 + s(C_\pi + C_\mu)r_\pi} \Leftrightarrow \frac{1}{1 + s/\omega_\beta}$$

$$20\log \beta - 20\log \sqrt{1 + (\omega_T/\omega_\beta)^2} = 0$$


$$\beta = \sqrt{1 + (\omega_T/\omega_\beta)^2}$$

$$\omega_T \approx \omega_\beta \beta \because \beta \gg 1$$


Unity-gain bandwidth

$$\omega_T \approx \omega_\beta \beta = \frac{g_m}{C_\pi + C_\mu}$$

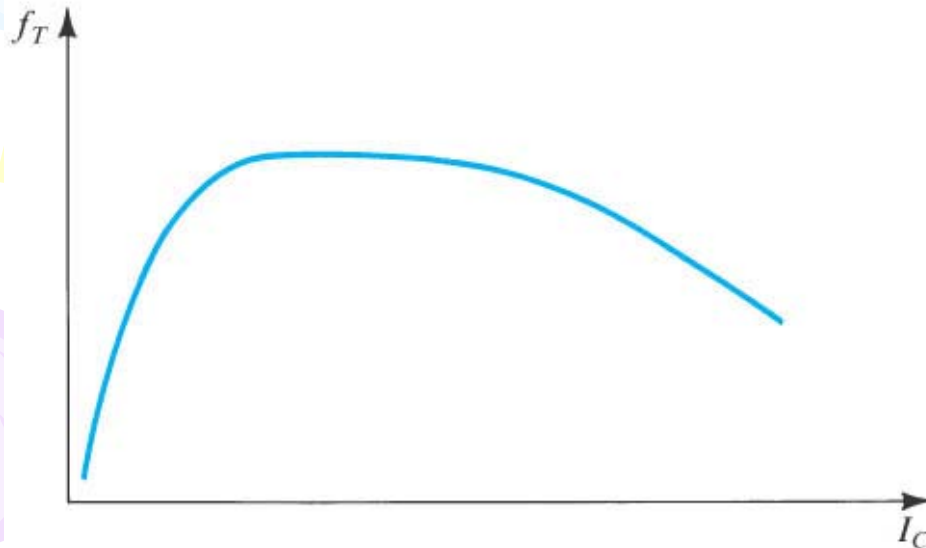
$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$




CE Amplifier

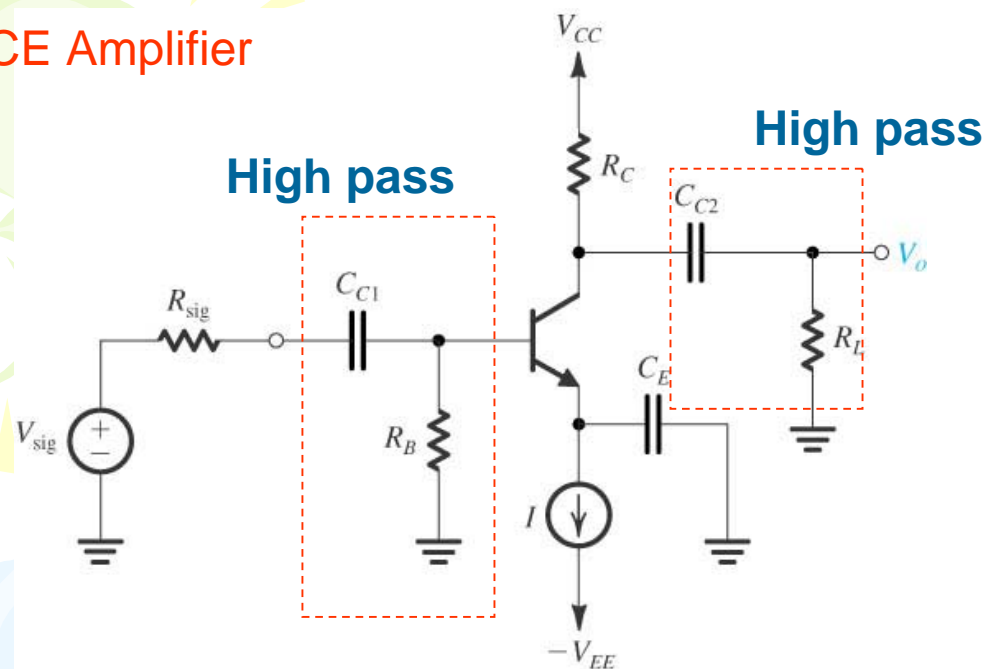

(a)

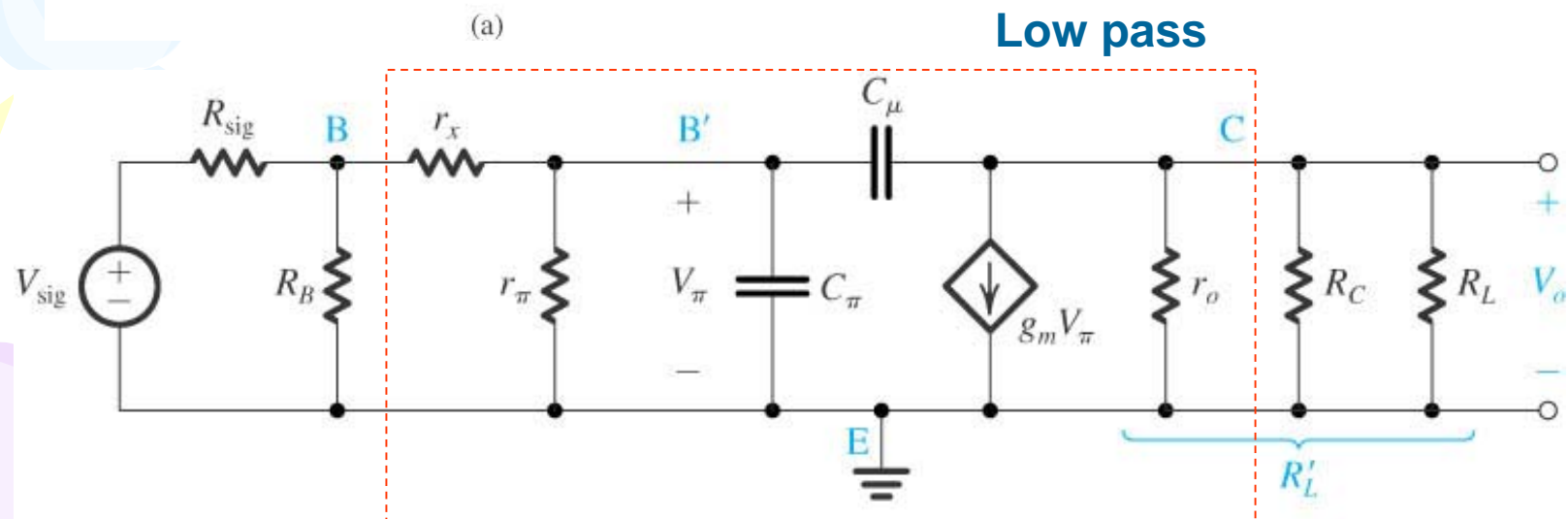



(a)

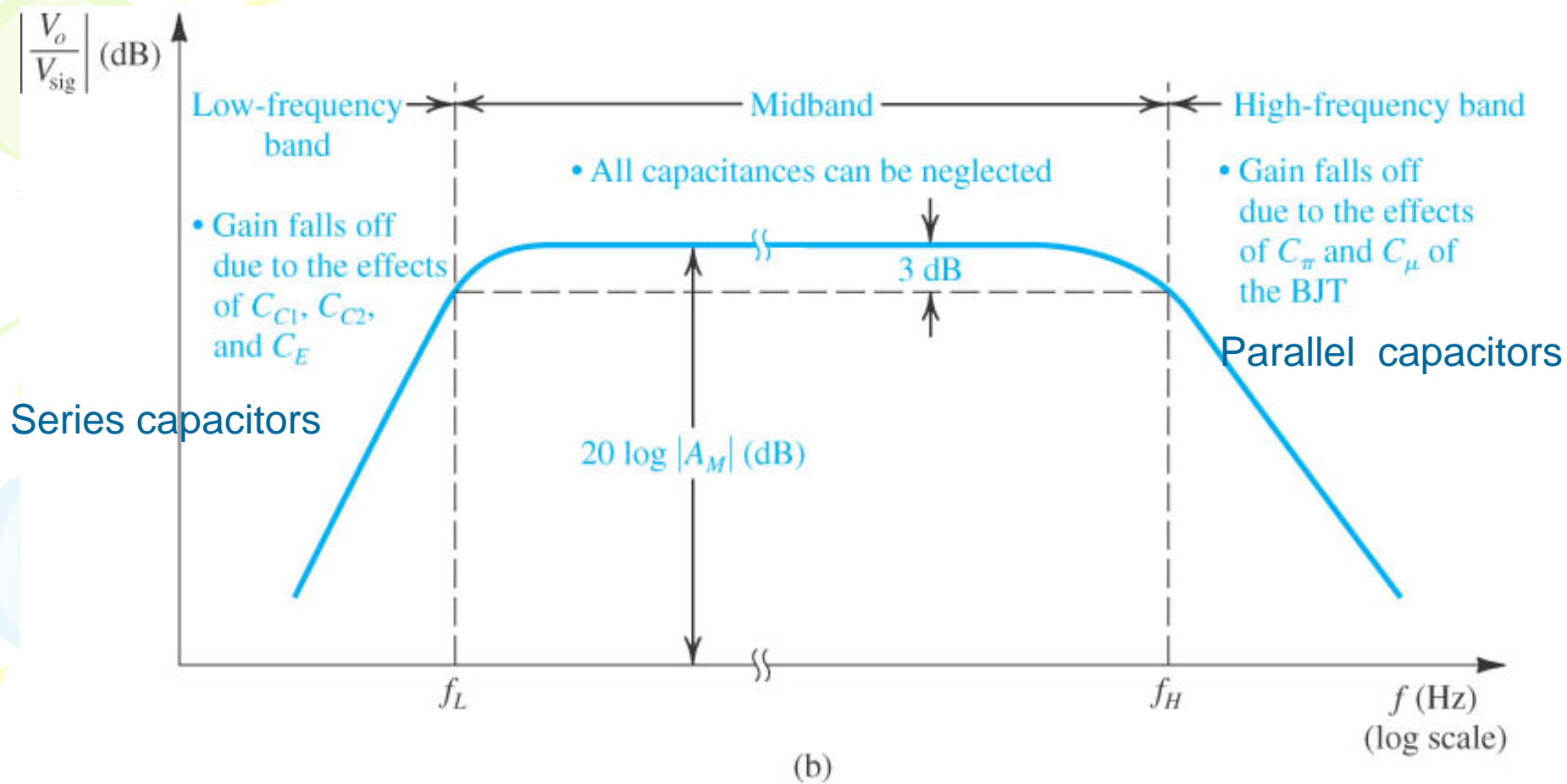

Bandwidth $BW \equiv f_H - f_L \approx f_H (\because f_L \ll f_H)$

Midband amplitude $A_M = \frac{v_o}{v_{sig}} = - \frac{(R_B // r_\pi)}{(R_B // r_\pi) + R_s} g_m (r_o // R_C // R_L)$

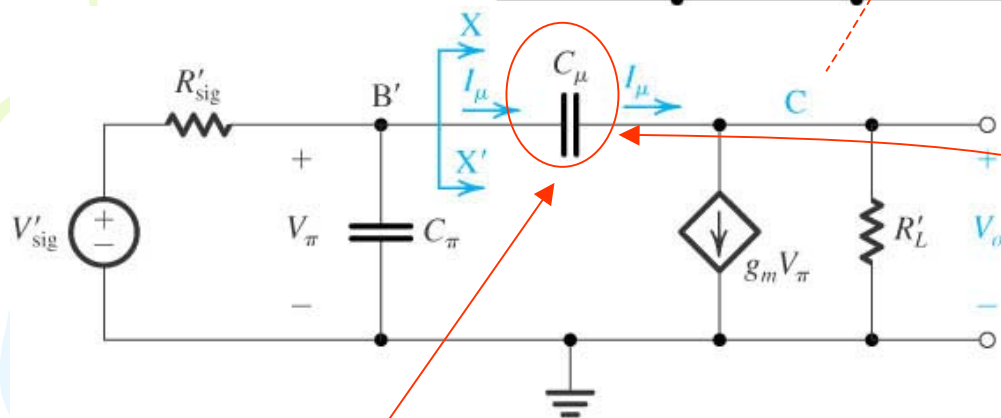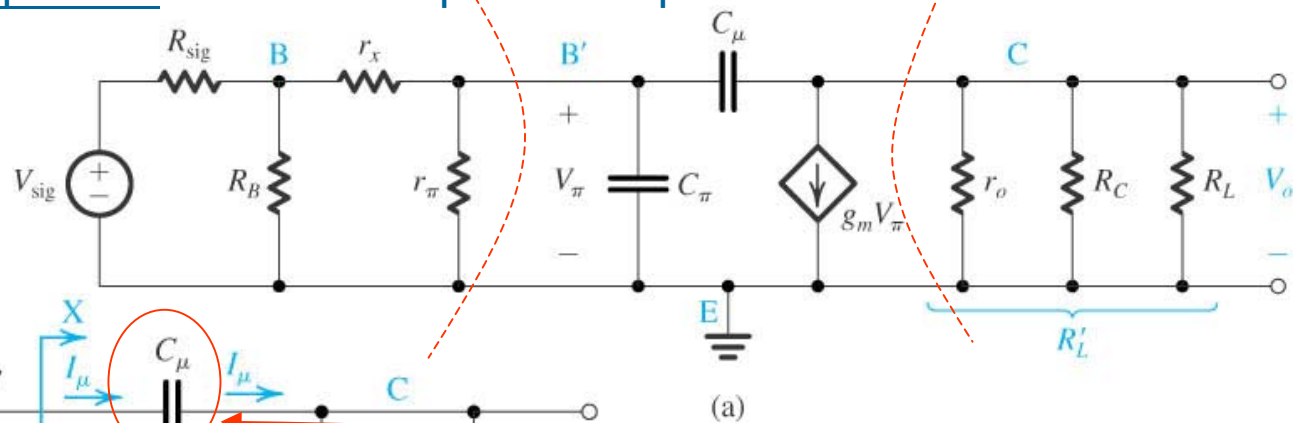High frequency response: The effect of parallel capacitors



$$V'_{sig} = V_{sig} \frac{R_B}{R_B + R_{sig}} \frac{r_{\pi}}{r_{\pi} + r_x + (R_{sig} \parallel R_B)}$$


$$R'_{sig} = r_{\pi} \parallel [r_x + (R_B \parallel R_{sig})]$$

$$i_{\mu} = sC_{\mu}(v_{\pi}^{(b)} - v_o)$$

$$v_o = -g_m R'_L v_{\pi}$$

$$i_{\mu} = sC_{eq} v_{\pi}$$


$$C_{eq} = C_{\mu}(1 + g_m R'_L)$$

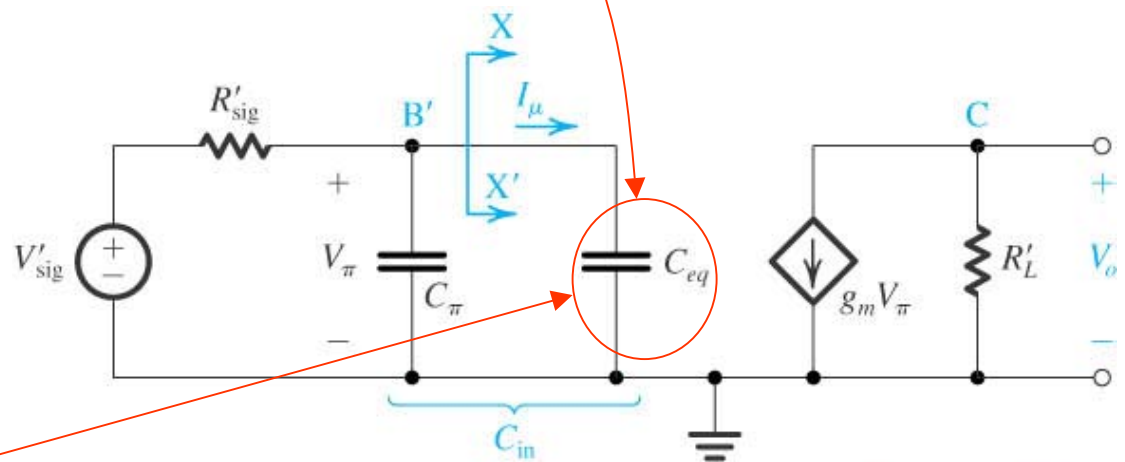

$$C_{in} = C_{\pi} + C_{eq} \\ = C_{\pi} + C_{\mu}(1 + g_m R'_L)$$

$$V_o = -g_m R'_L V_{\pi}$$

Miller's theorem

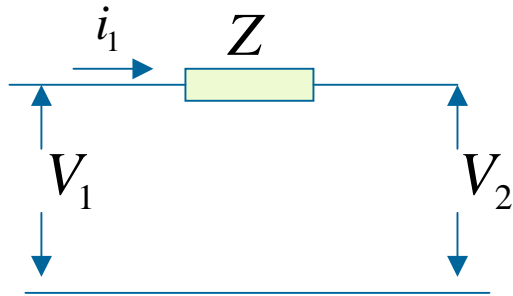



$$\frac{V_2}{V_1} = k$$

$$i_1 = \frac{V_1 - V_2}{Z} = \frac{V_1}{Z_1}$$

$$\frac{V_2}{V_1} = k \Rightarrow Z_1 = \frac{Z}{1 - k}$$

$$Z_2 = \frac{k}{k - 1} Z$$

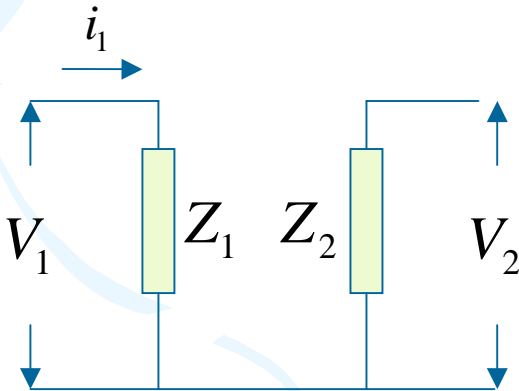

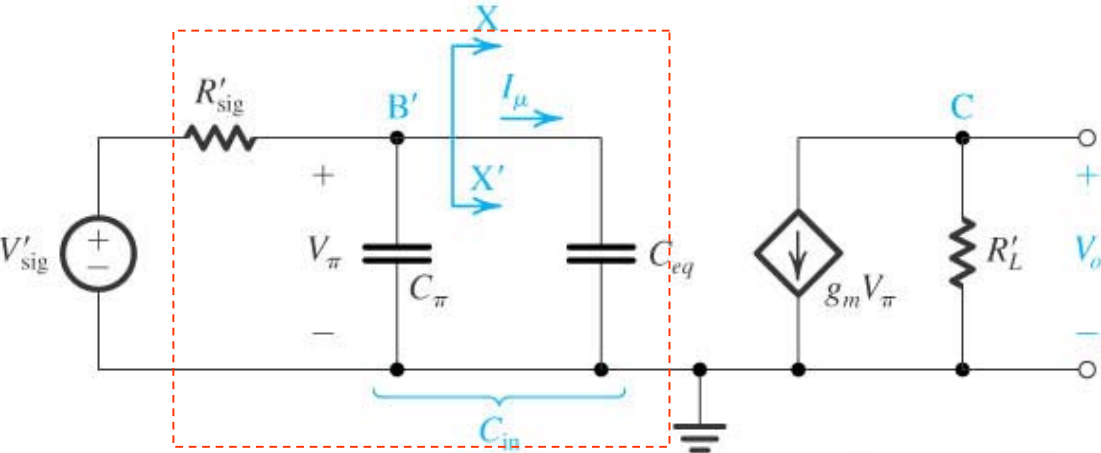

$$C_{in} = C_{\pi} + C_{eq}$$

$$= C_{\pi} + C_{\mu}(1 + g_m R'_L)$$

$$V_o = -g_m R'_L V_{\pi}$$

(c)


$$v_{\pi} = v'_s \frac{1}{1 + \left(\frac{s}{\omega_0}\right)}$$

$$\omega_0 = \frac{1}{R'_s (C_{\pi} + C_{eq})}$$

$$f_H = \frac{1}{2\pi R'_s (C_{\pi} + C_{eq})}$$

$$C_{eq} = C_{\mu} (1 + g_m R'_L)$$

Miller multiplier

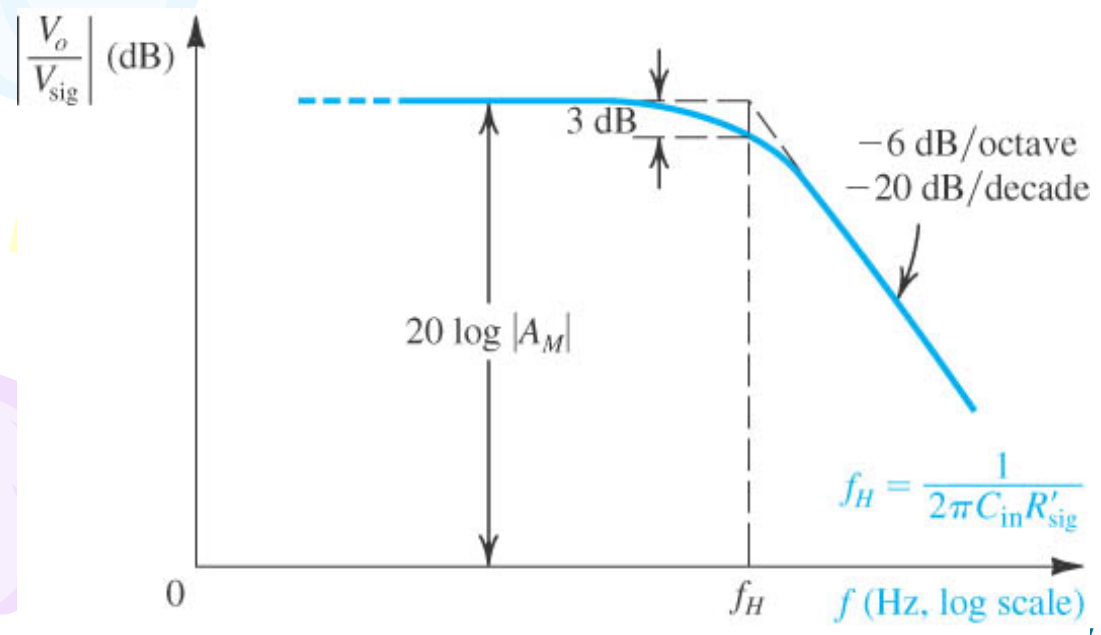

(d)

Example 5.18 Find the Midband gain and upper 3 dB frequency of CE amplifier.

The parameters of Hybrid π model


$$g_m = \frac{I_C}{V_T} = 40 \text{ mA/V}$$

$$r_\pi = \frac{V_T}{I_B} = 2.5 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = 100 \text{ k}\Omega$$

$$C_\pi + C_\mu = \frac{g_m}{\omega_T} = 8 \text{ pF} = C_\pi + 1$$

$$C_\pi = 7 \text{ pF}$$

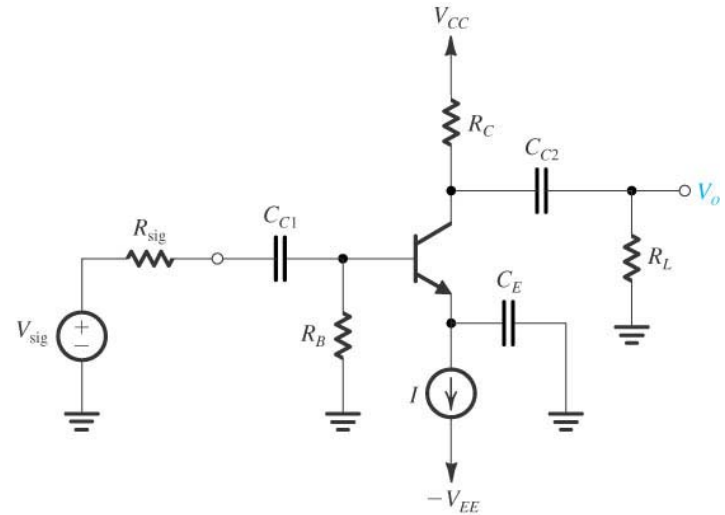

$$V_{CC} = V_{EE} = 10 \text{ V}$$

$$I = 1 \text{ mA}$$

$$R_B = 100 \text{ k}\Omega, R_C = 8 \text{ k}\Omega$$

$$R_s = 5 \text{ k}\Omega, R_L = 5 \text{ k}\Omega$$

$$\beta = 100, V_A = 100 \text{ V}$$

$$C_\mu = 1 \text{ pF}, r_x = 50 \Omega$$

$$f_T = 800 \text{ MHz}$$

$$A_M = \frac{v_o}{v_{sig}} = -\frac{R_B}{R_B + R_s} \frac{r_\pi}{(R_B // R_s) + r_\pi + r_x} g_m (r_o // R_C // R_L) = -39$$

$$C_{eq} = C_\mu (1 + g_m R_L')$$


$$C_{in} = C_\pi + C_{eq} = 128 pF$$

$$R_s' = r_\pi // [r_x + (R_B // R_S)] = 1.65 k\Omega$$



$$\omega_0 = \frac{1}{R_s' (C_\pi + C_{eq})}$$

$$f_H = \frac{1}{2\pi R_s' (C_\pi + C_{eq})} = 754 kHz$$

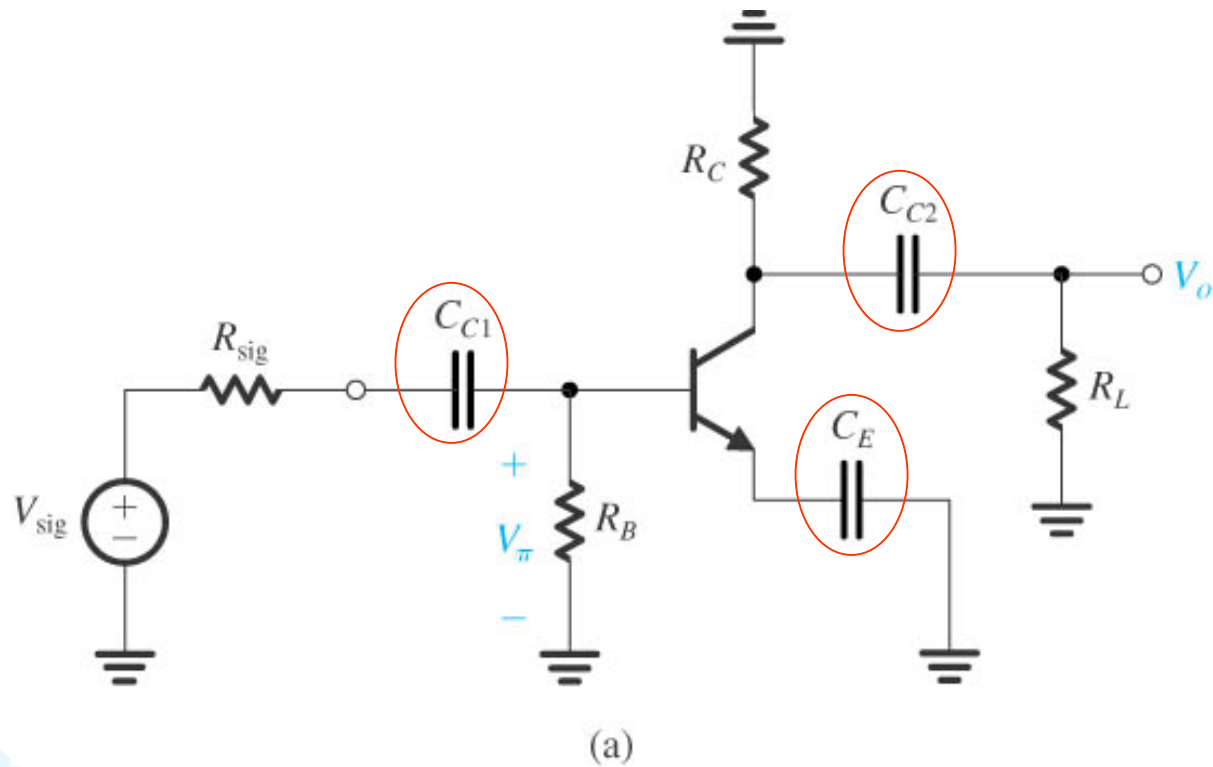Low frequency response: The effects of the series capacitors



Consider C_{C1}

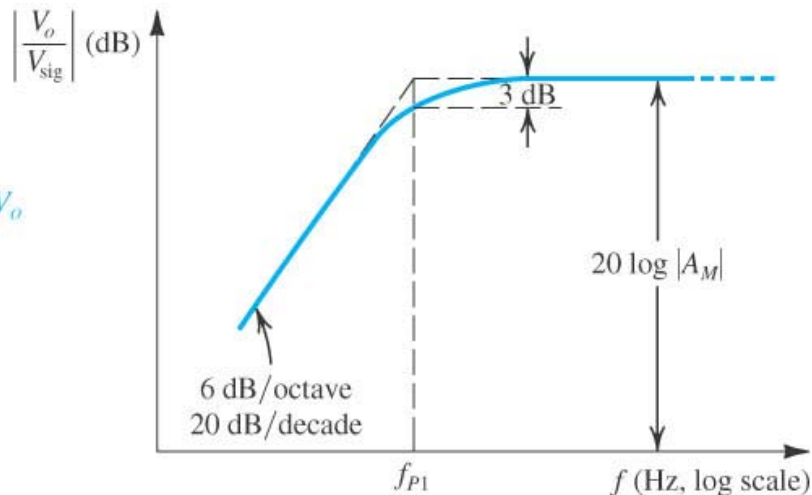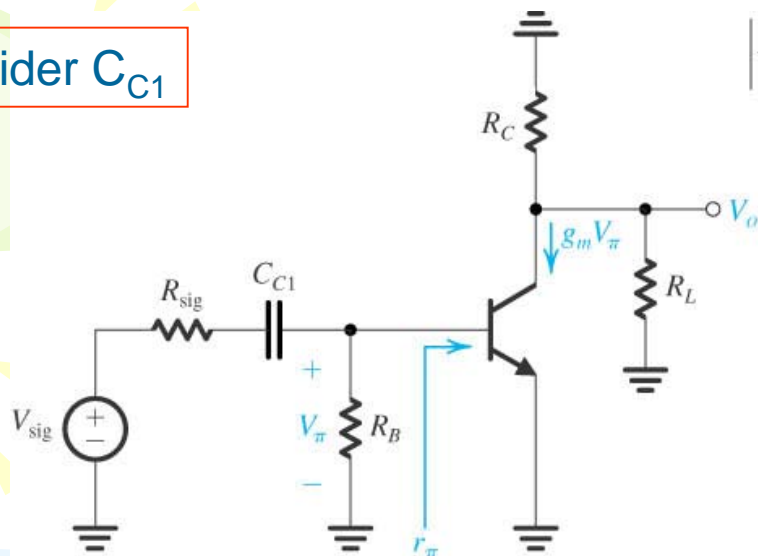

$$f_{P1} = 1/2\pi C_{C1} [(R_B // r_{\pi}) + R_{sig}]$$

$$v_{\pi} = v_s \frac{R_B // r_{\pi}}{(R_B // r_{\pi}) + R_s + 1/sC_{C1}}$$


$$v_o = -g_m v_{\pi} (R_C // R_L)$$

$$\frac{v_o}{v_s} = \frac{-(R_B // r_{\pi})}{(R_B // r_{\pi}) + R_s + 1/sC_{C1}} g_m (R_C // R_L)$$



$$= g_m (R_C // R_L) \frac{-(R_B // r_{\pi}) s C_{C1}}{s C_{C1} [(R_B // r_{\pi}) + R_s] + 1}$$

$$= -g_m (R_C // R_L) \frac{(R_B // r_{\pi})}{[(R_B // r_{\pi}) + R_s]} \left\{ \frac{s}{s + 1/C_{C1} [(R_B // r_{\pi}) + R_s]} \right\}$$
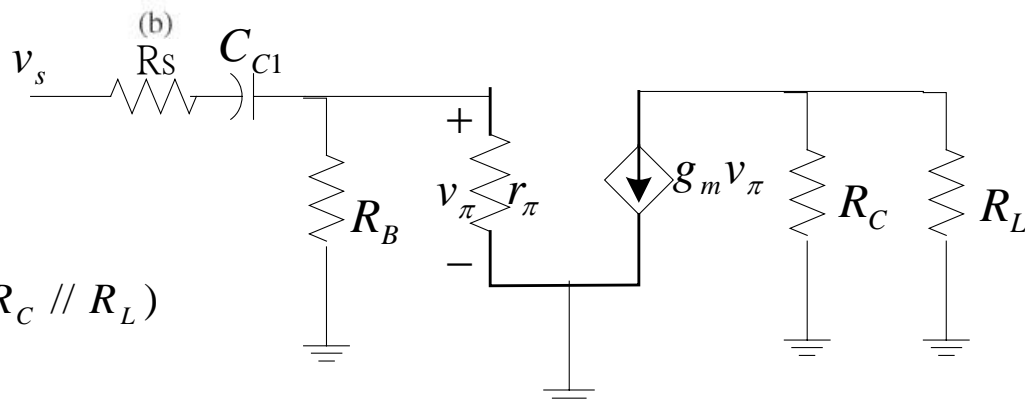
$$\omega_{p1} = \frac{1}{C_{C1} [(R_B // r_{\pi}) + R_s]}$$



Consider C_E

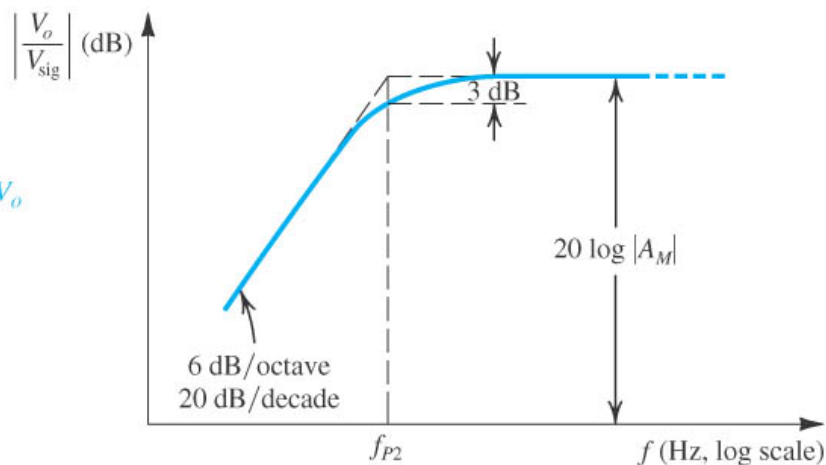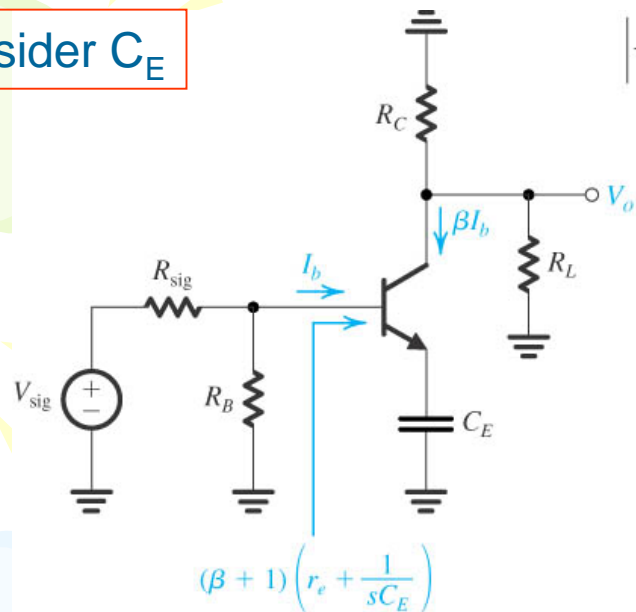

$$f_{P2} = 1/2\pi C_E \left[r_e + \frac{R_B // R_{sig}}{\beta + 1} \right]$$


$$I_{(b)} = v_s \frac{R_B}{R_B + R_s} \frac{1}{(R_B // R_s) + (\beta + 1)(r_e + 1/sC_E)}$$

$$v_o = -\beta I_b (R_C // R_L)$$



$$\frac{v_o}{v_s} = -\frac{R_B}{R_B + R_s} \frac{\beta(R_C // R_L)}{(R_B // R_s) + (\beta + 1)(r_e + 1/sC_E)}$$

$$= -\frac{R_B}{R_B + R_s} \frac{\beta(R_C // R_L)}{(R_B // R_s) + (\beta + 1)r_e} \left\{ \frac{s}{s + \frac{1}{C_E[(\frac{R_B // R_s}{\beta + 1}) + r_e]}} \right\}$$
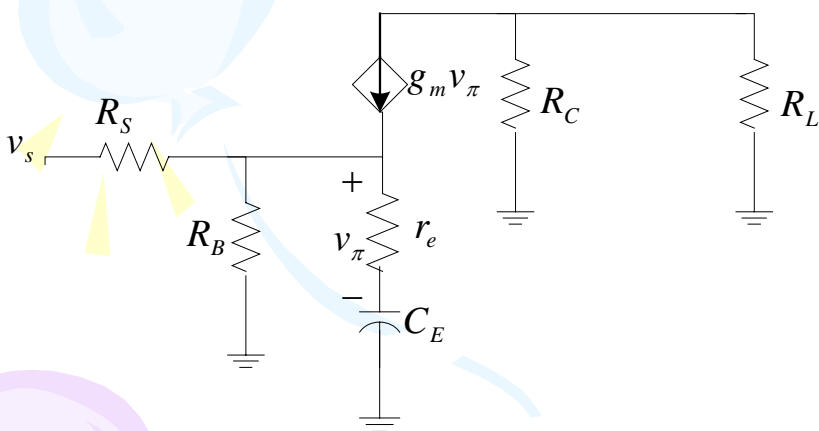
$$\omega_{p2} = \frac{1}{C_E[(\frac{R_B // R_s}{\beta + 1}) + r_e]}$$



Consider C_{C2}

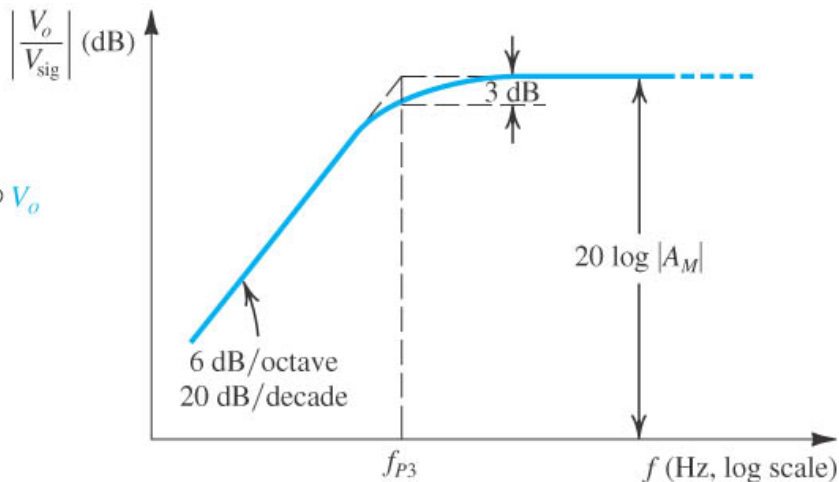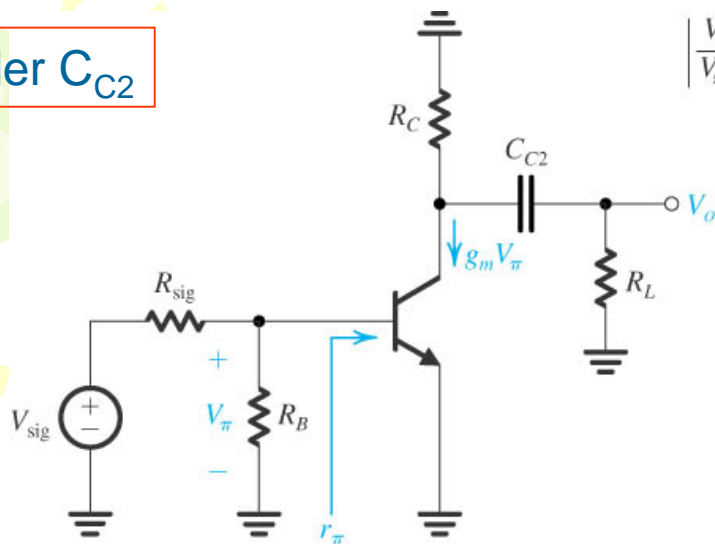


$$f_{P3} = 1/2\pi C_{C2} (R_C + R_L)$$


$$v_{\pi} = v_s \frac{R_B // r_{\pi}}{(R_B // r_{\pi}) + R_s}$$

$$v_o = -g_m v_{\pi} \frac{R_C}{R_C + R_L + \frac{1}{sC_{C2}}} R_L$$

$$\frac{v_o}{v_s} = \frac{-(R_B // r_{\pi})}{(R_B // r_{\pi}) + R_s} g_m (R_C // R_L) \frac{s}{s + \frac{1}{C_{C2}(R_C + R_L)}}$$
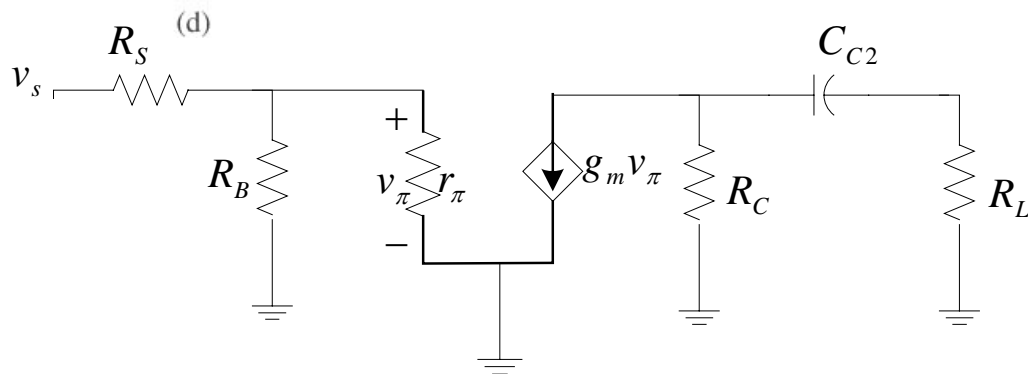
$$\omega_{p3} = \frac{1}{C_{C2}(R_C + R_L)}$$



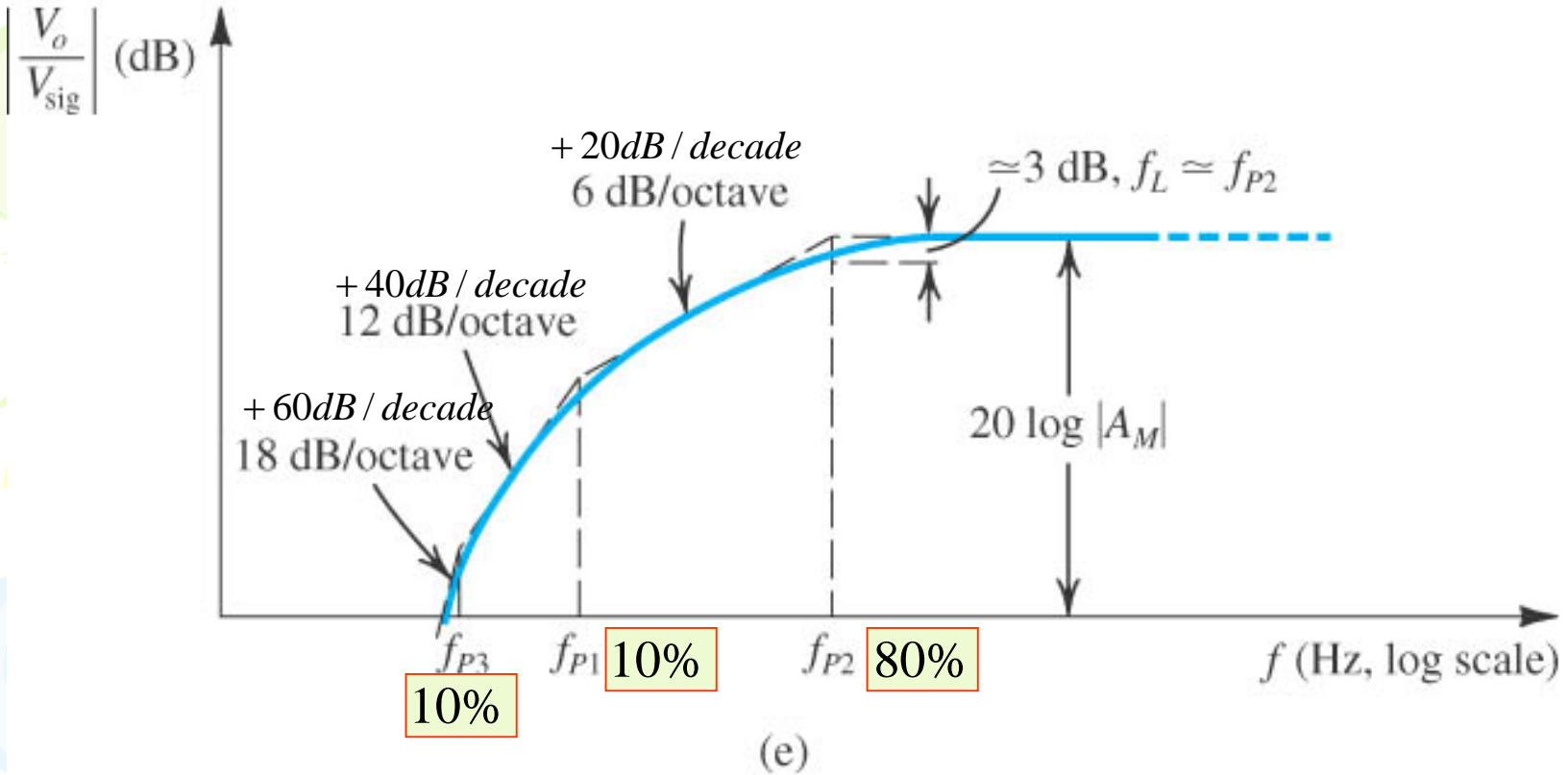

$$\frac{v_o}{v_s} = -A_M \left(\frac{s}{s + \omega_{p1}} \right) \left(\frac{s}{s + \omega_{p2}} \right) \left(\frac{s}{s + \omega_{p3}} \right)$$

$$\omega_{p1} = \frac{1}{C_{C1}[(R_B // r_\pi) + R_s]}$$

R_{C1}

$$\omega_{p2} = \frac{1}{C_E \left[\left(\frac{R_B // R_s}{\beta + 1} \right) + r_e \right]}$$

dominant R_E

$$\omega_{p3} = \frac{1}{C_{C2}(R_C + R_L)}$$

R_{C2}

Example 5.19 Find the C_{C1} , C_{C2} and C_E the CE amplifier of the example 5.18.

$$\omega_{p1} = \frac{1}{C_{C1}[(R_B // r_\pi) + R_s]}$$

$$\omega_{p2} = \frac{1}{C_E[(\frac{R_B // R_s}{\beta + 1}) + r_e]}$$

$$\omega_{p3} = \frac{1}{C_{C2}(R_C + R_L)}$$

$$C_E[(\frac{R_B // R_s}{\beta + 1}) + r_e] = 0.8 \times 2\pi f_L \Rightarrow C_E = 27.6\mu F$$

$$C_{C1}[(R_B // r_\pi) + R_s] = 0.1 \times 2\pi f_L \Rightarrow C_{C1} = 2.1\mu F$$

$$C_{C2}(R_C + R_L) = 2\pi \omega f_L \Rightarrow C_{C2} = 1.2\mu F$$

$$V_{CC} = V_{EE} = 10V$$

$$I = 1mA$$

$$R_B = 100k\Omega, R_C = 8k\Omega$$


$$R_s = 5k\Omega, R_L = 5k\Omega$$

$$\beta = 100, g_m = 40$$

$$r_\pi = 2.5k\Omega$$


$$f_L = 100Hz$$

MOSFET high frequency model

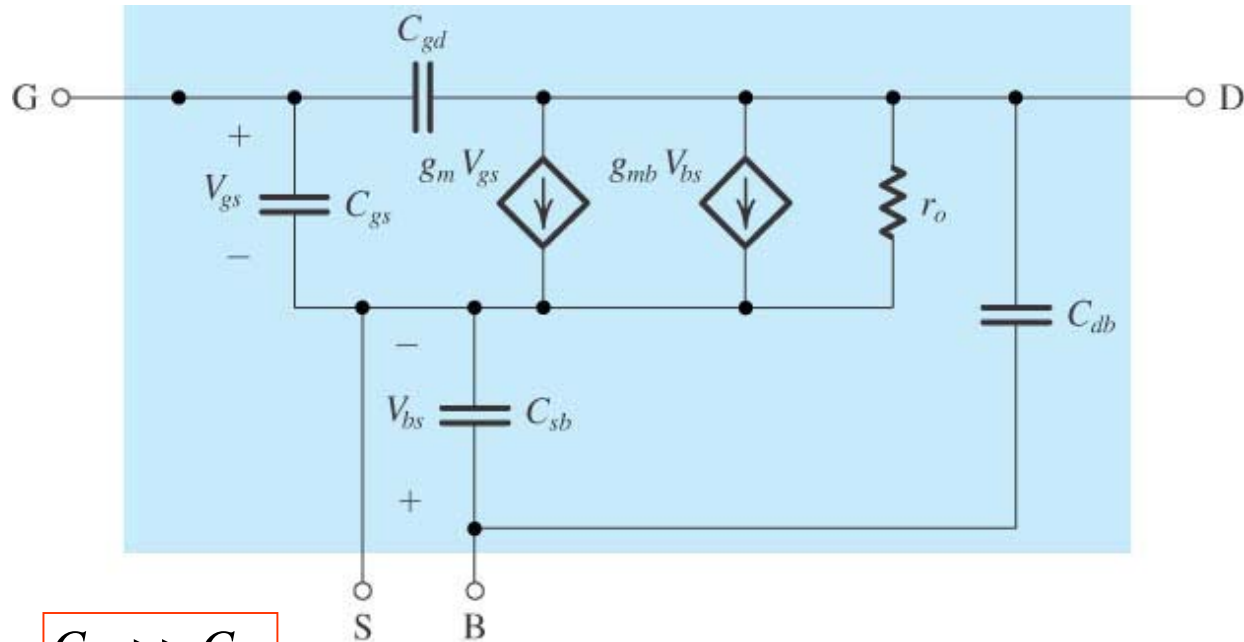


$$C_{gs} \gg C_{gd}$$


(a)

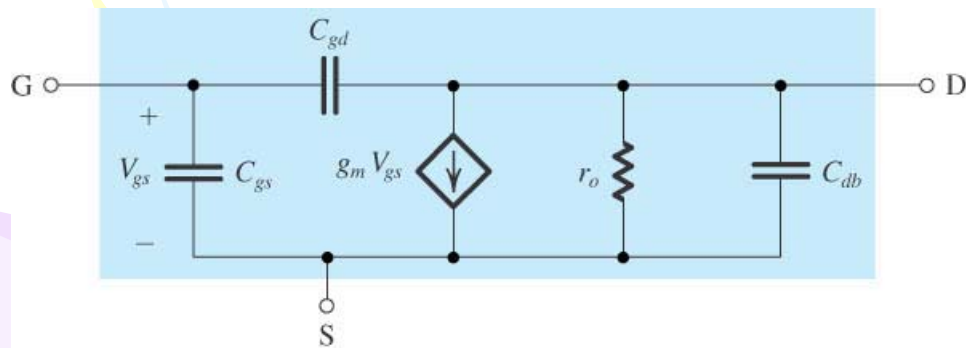

(b)

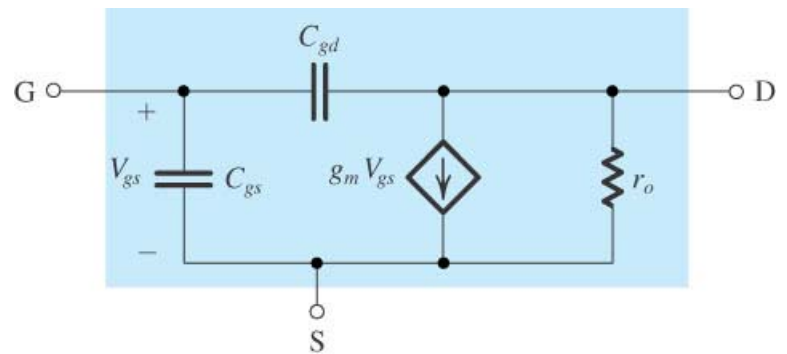

(c)

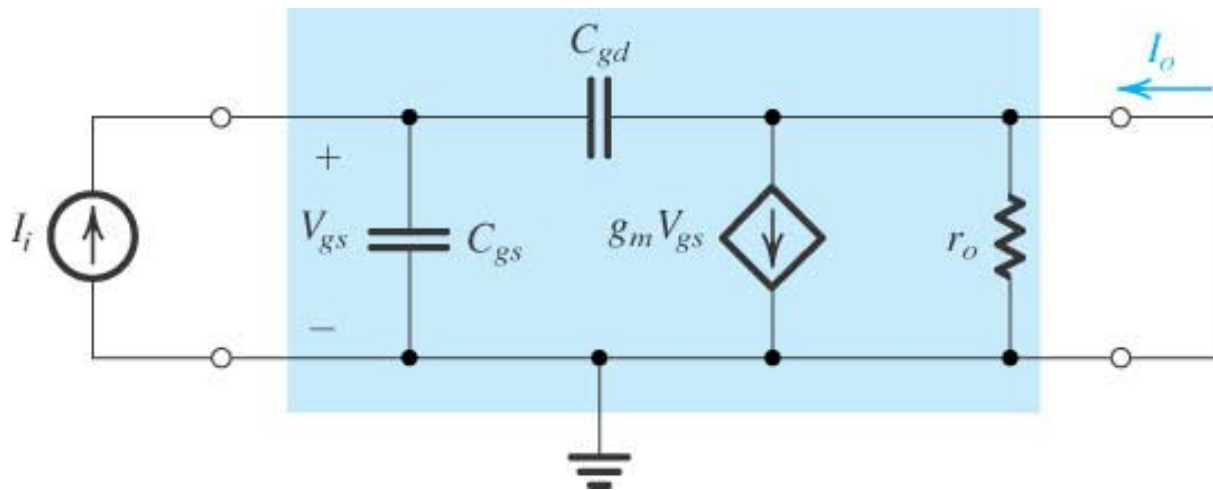


$$I_o = g_m v_{gs} - sC_{gd} v_{gs} \approx g_m v_{gs}$$

$$v_{gs} = \frac{I_i}{s(C_{gs} + C_{gd})}$$

$$\frac{I_o}{I_i} = \frac{g_m}{s(C_{gs} + C_{gd})} = \frac{g_m}{j\omega(C_{gs} + C_{gd})}$$

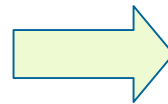
$$\text{if } \omega = \frac{g_m}{(C_{gs} + C_{gd})} \Rightarrow \frac{I_o}{I_i} = 1 \Rightarrow 0\text{dB}$$




$$\omega_T = \frac{g_m}{(C_{gs} + C_{gd})}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

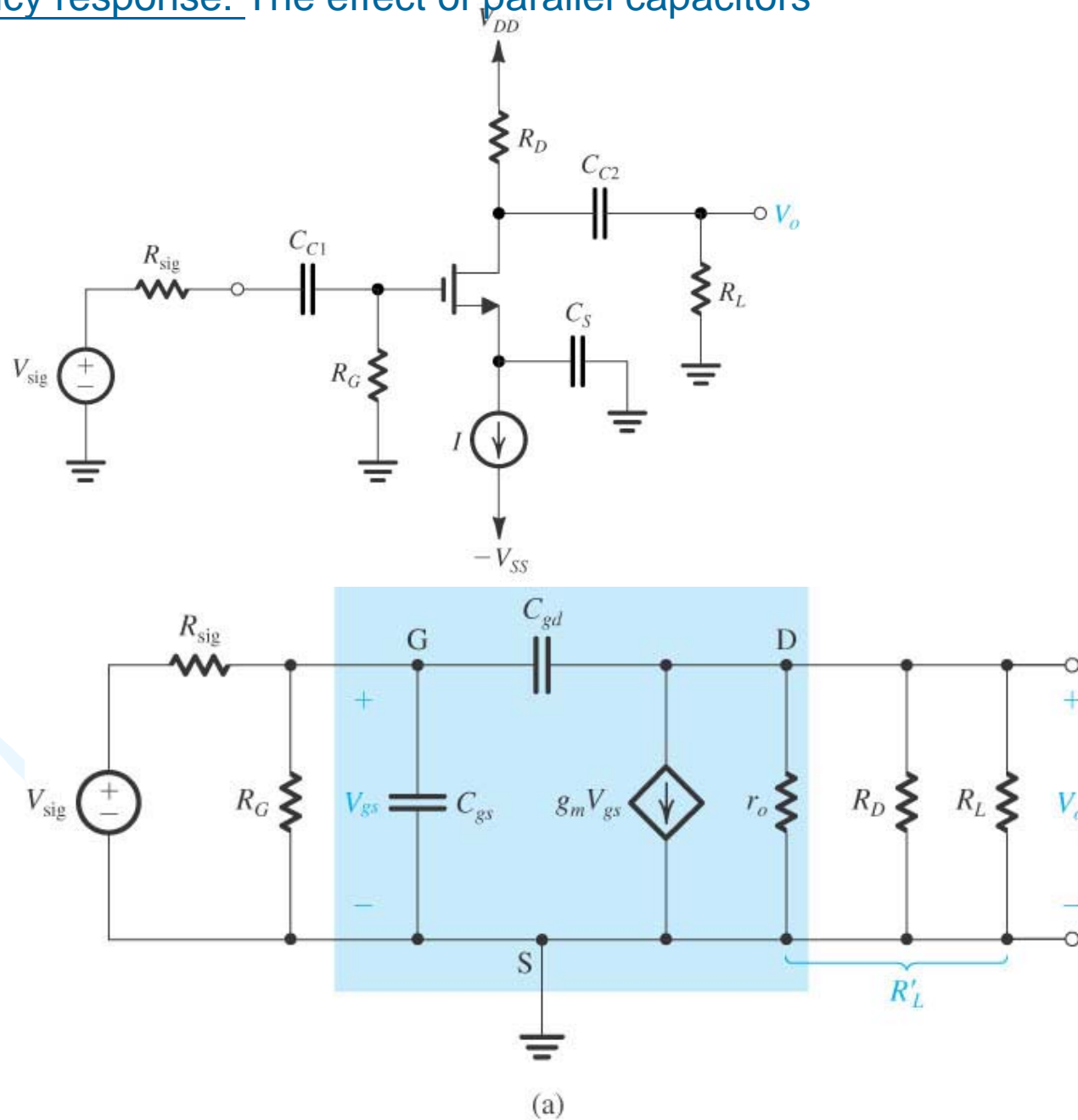
High frequency response: The effect of parallel capacitors



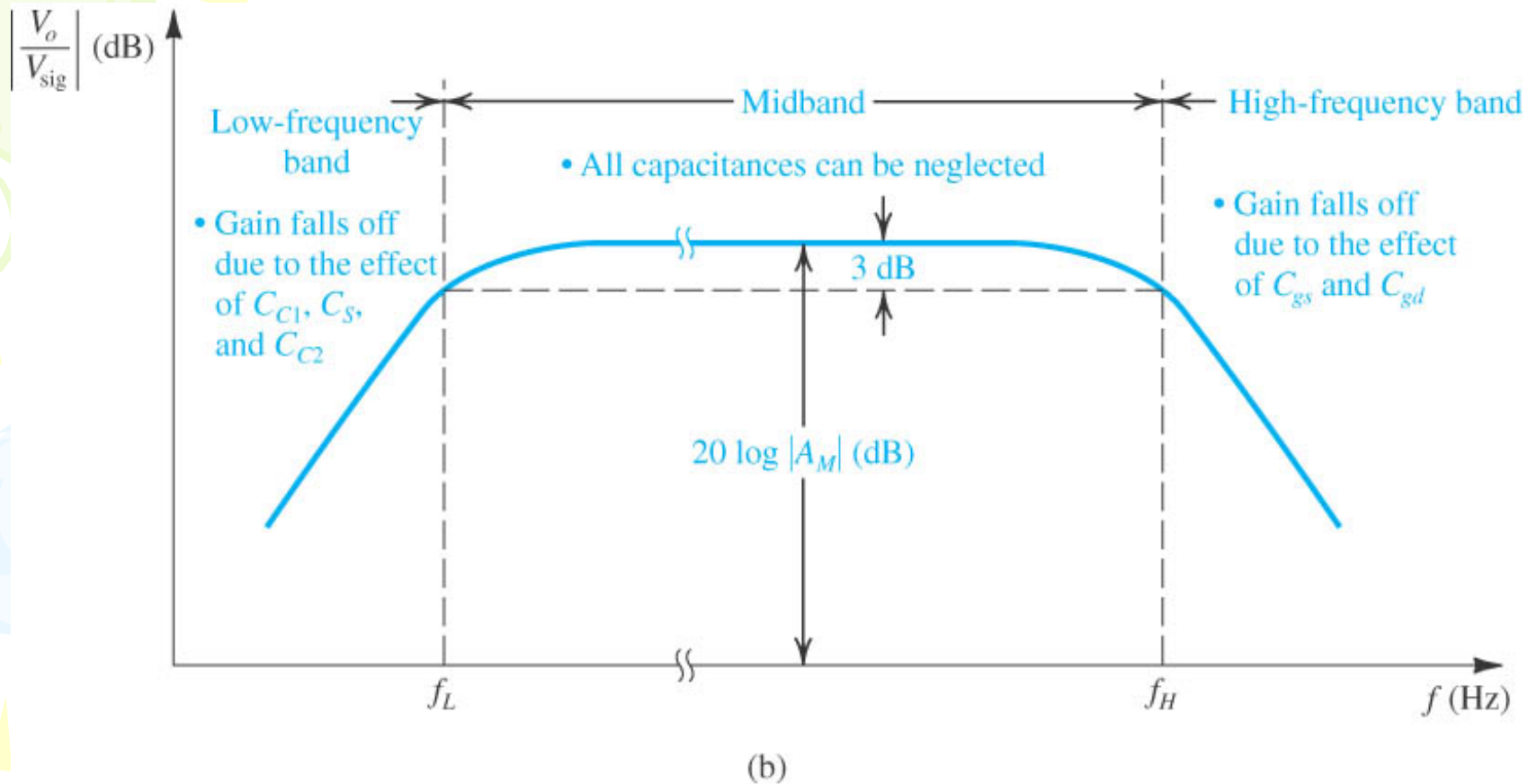


Bandwidth $BW \equiv f_H - f_L \approx f_H (\because f_L \ll f_H)$

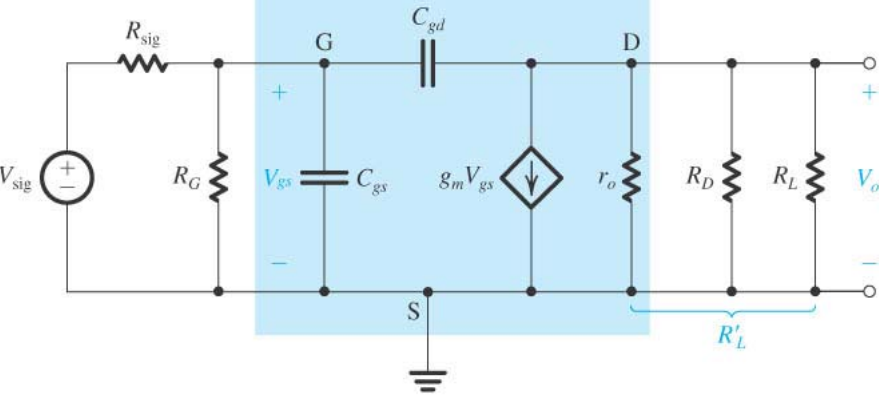
Midband amplitude $A_M = \frac{v_o}{v_{sig}} = -\frac{R_G}{R_G + R_s} g_m (r_o \parallel R_D \parallel R_L)$



(a)

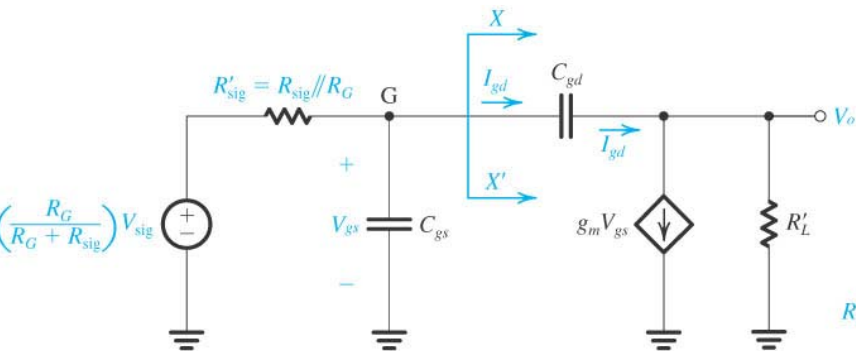

(b)

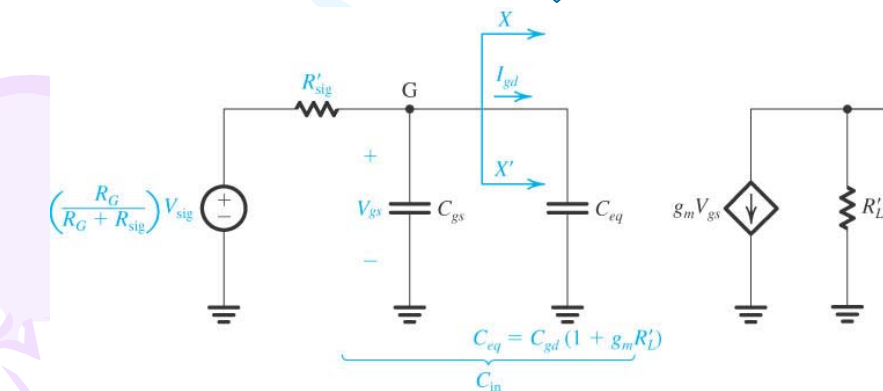

(c)

$$I_{gd} = sC_{gd}(v_{gs} - v_o)$$

$$v_o \approx -g_m R'_L v_{gs}$$

$$I_{gd} = sC_{gd}(1 + g_m R'_L)v_{gs} = sC_{eq}v_{gs}$$

$$C_{eq} = C_{gd}(1 + g_m R'_L)$$


$$v_{gs} = \frac{R_G}{R_G + R_s} v_s \frac{1}{1 + s/\omega_0}$$

$$A_M = \frac{v_o}{v_s} = -\frac{R_G}{R_G + R_s} g_m R'_L$$

$$\omega_0 = \frac{1}{RC} = \frac{1}{(R_G // R_s)[C_{gs} + C_{gd}(1 + g_m R'_L)]}$$

$$f_H = \frac{1}{2\pi(R_G // R_s)[C_{gs} + C_{gd}(1 + g_m R'_L)]}$$

circuit by
Miller

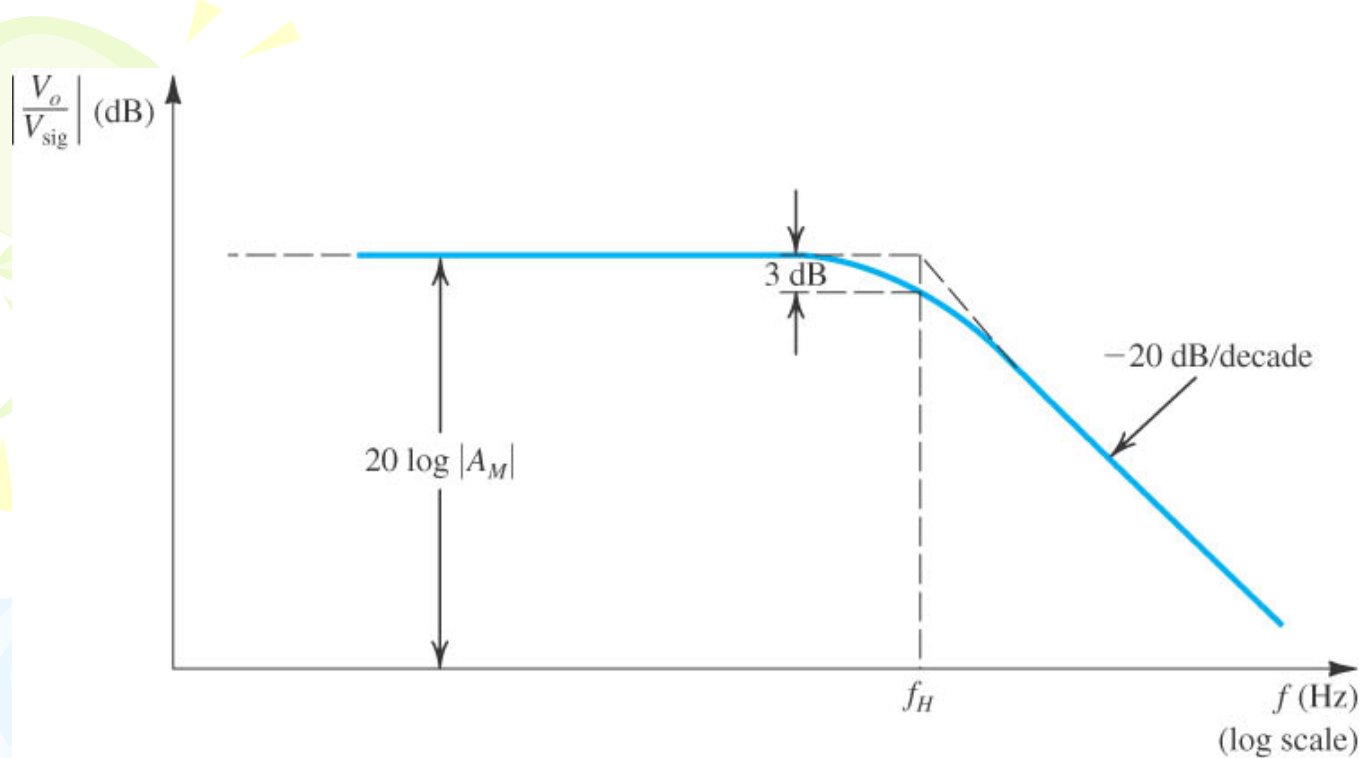


(d)

$$A_M = -\frac{R_G}{R_G + R_s} g_m R'_L$$

$$\omega_0 = \frac{1}{RC} = \frac{1}{(R_G // R_s)[C_{gs} + C_{gd}(1 + g_m R'_L)]}$$

$$f_H = \frac{1}{2\pi(R_G // R_s)[C_{gs} + C_{gd}(1 + g_m R'_L)]}$$

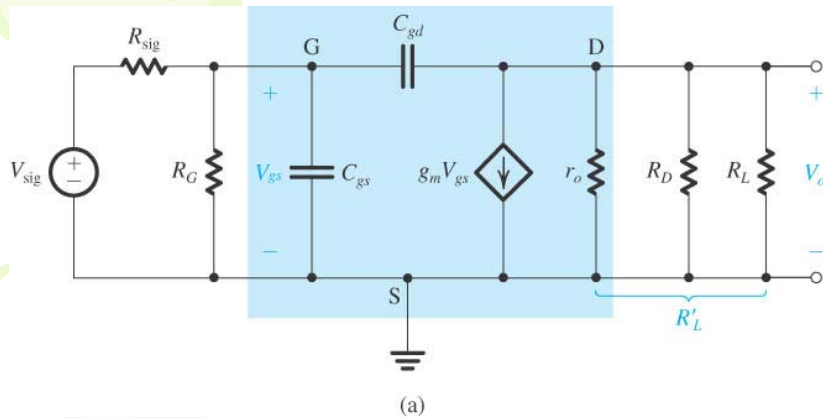
Example 4.12 Find the Midband gain and upper 3 dB frequency of CS amplifier.



$$A_M = -\frac{R_G}{R_G + R_s} g_m R'_L$$

$$\omega_0 = \frac{1}{RC} = \frac{1}{(R_G \parallel R_s)[C_{gs} + C_{gd}(1 + g_m R'_L)]}$$
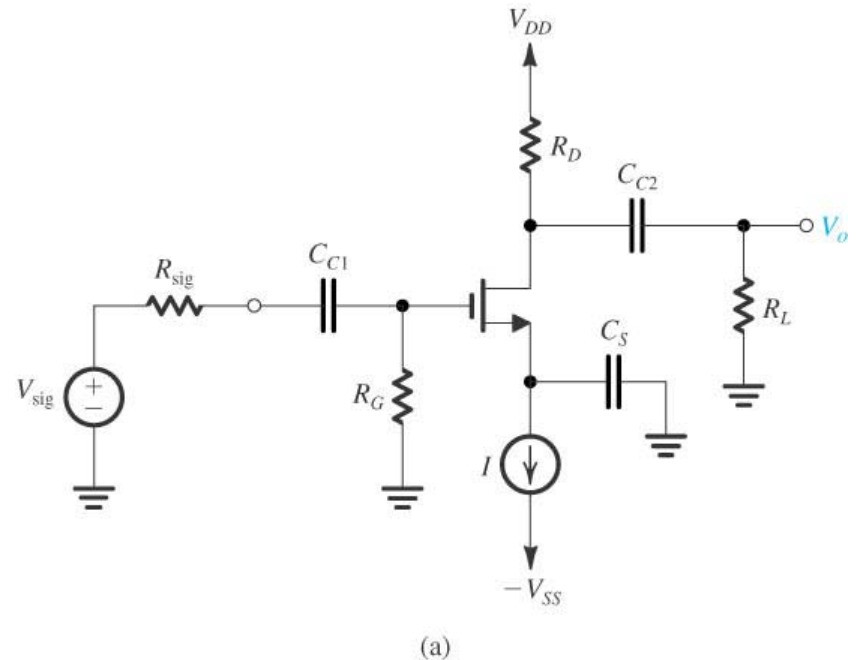
$$f_H = \frac{1}{2\pi(R_G \parallel R_s)[C_{gs} + C_{gd}(1 + g_m R'_L)]}$$



$$I = mA$$


$$R_S = 100k\Omega, R_G = 4.7M\Omega$$

$$R_D = 15k\Omega, R_L = 15k\Omega$$

$$g_m = 1, r_o = 150k\Omega$$

$$C_{gs} = 1pF, C_{gd} = 0.4pF$$


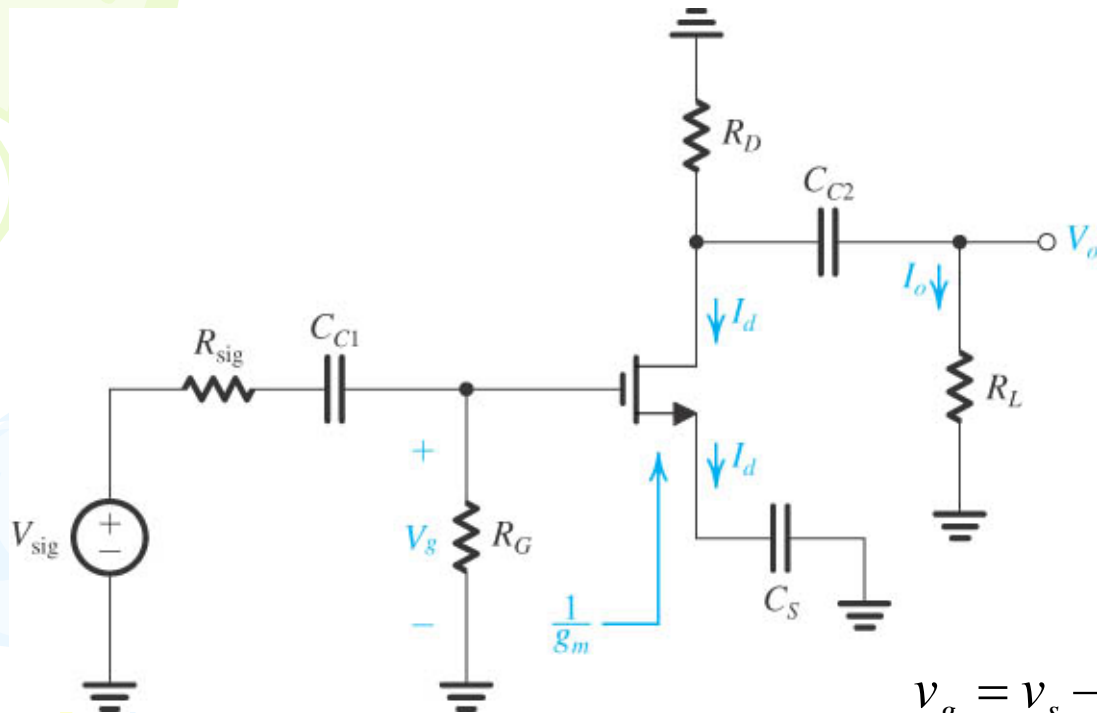
Low frequency response: The effects of the series capacitors



$$v_g = v_s \frac{R_G}{R_G + \frac{1}{sC_{C1}} + R_s}$$

$$v_g = v_s \frac{R_G}{R_G + R_s} \frac{s}{s + \frac{1}{C_{C1}(R_G + R_s)}}$$
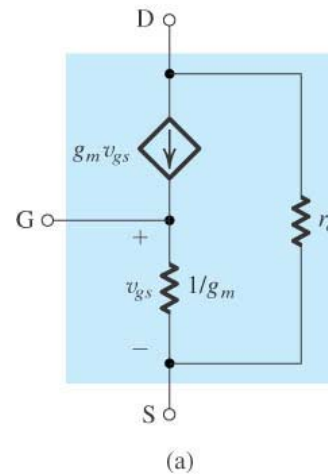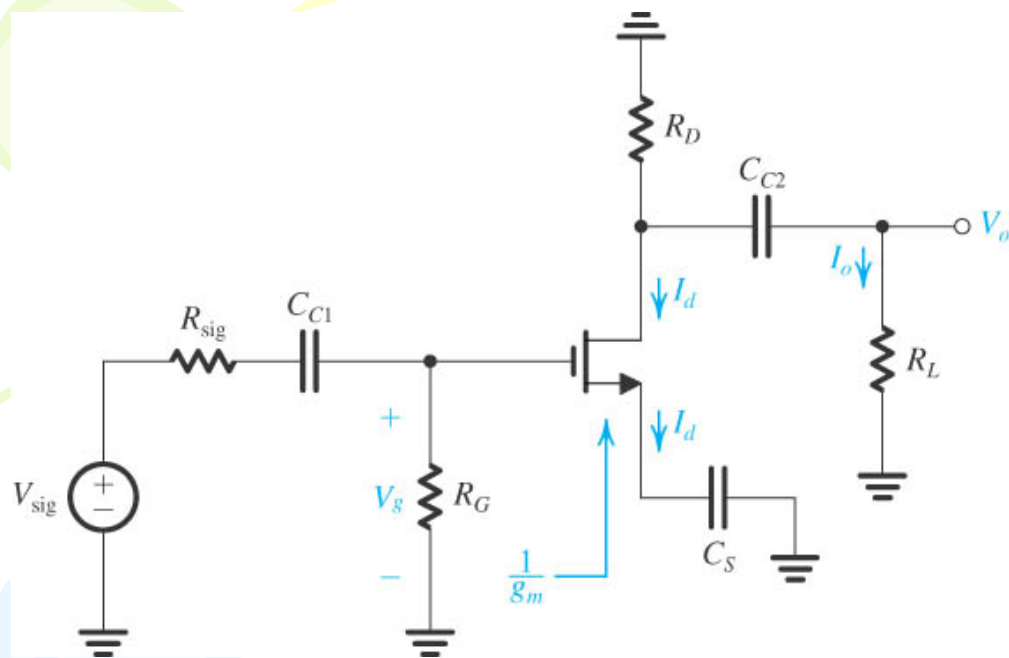
$$\omega_{p1} = \frac{1}{C_{C1}(R_G + R_s)}$$



$$i_d = \frac{v_g}{\frac{1}{g_m} + \frac{1}{sC_s}}$$


$$= g_m v_g \frac{s}{s + g_m / C_s}$$

$$\omega_{p3} = g_m / C_s$$

$$i_o = -i_d \frac{R_D}{R_D + \frac{1}{sC_{C2}} + R_L}$$

$$v_o = i_o R_L = -i_d (R_D // R_L) \frac{s}{s + \frac{1}{C_{C2}(R_D + R_L)}}$$
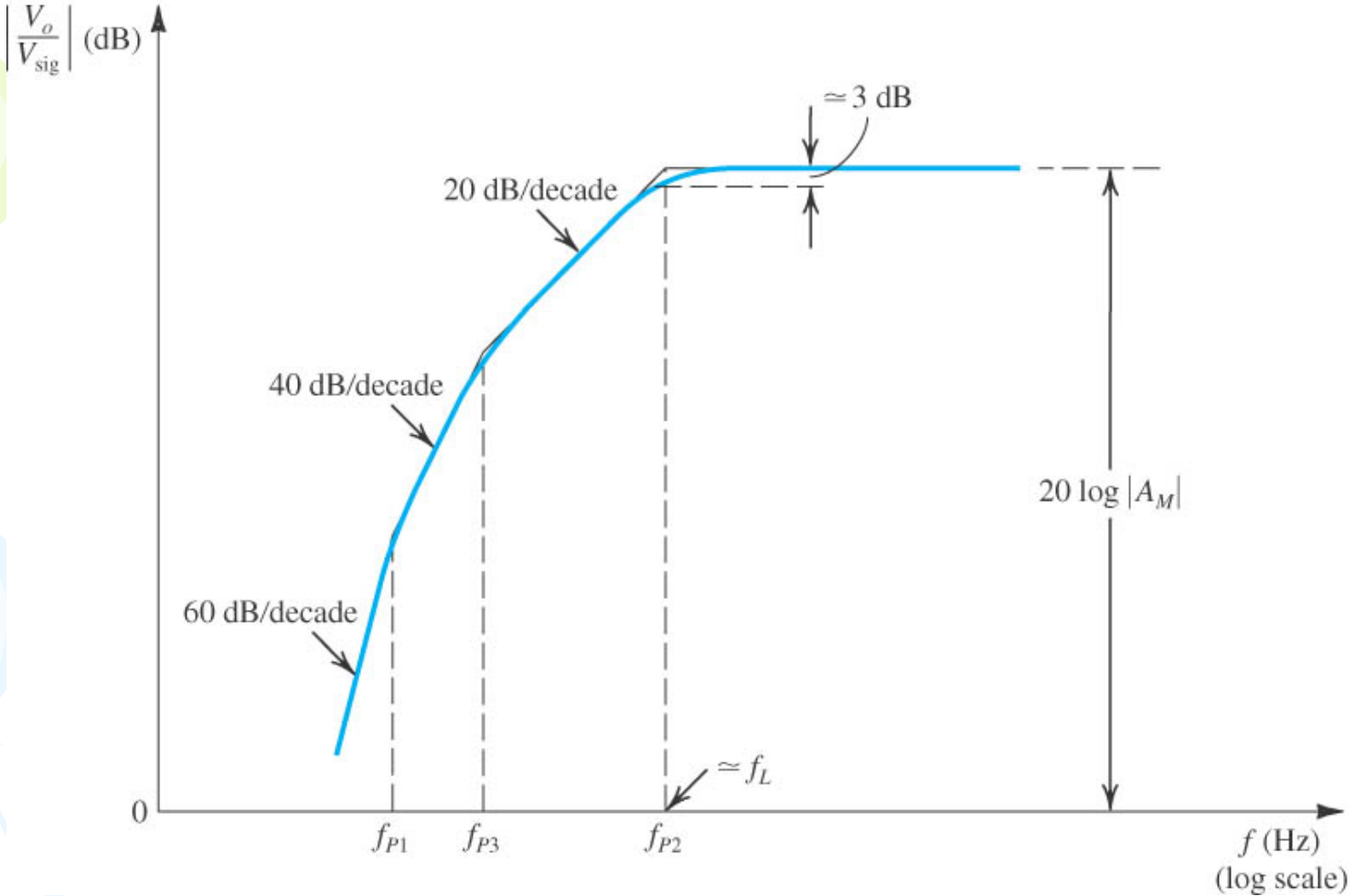
$$\omega_{p2} = \frac{1}{C_{C2}(R_D + R_L)}$$



$$\omega_{p1} = 1 / C_{C1} (R_G + R_s)$$

$$\omega_{p3} = 1 / C_{C2} (R_D + R_L)$$

$$\omega_{p2} = g_m / C_s$$

$$\frac{v_o}{v_s} = - \frac{R_G}{R_G + R_s} g_m (R_D // R_L) \left(\frac{s}{s + \omega_{p1}} \right) \left(\frac{s}{s + \omega_{p2}} \right) \left(\frac{s}{s + \omega_{p3}} \right)$$

Example 4.13 Find the C_{C1} , C_{C2} and C_s the CS amplifier of the example 4.12.

$$f_L = f_{p2} = \frac{1}{2\pi(C_s/g_m)}$$

$$\Rightarrow C_s = \frac{g_m}{2\pi f_L} = 1.6\mu F$$

$$f_{p1} = 10Hz = \frac{1}{2\pi C_{C1}(R_G + R_s)}$$

$$\Rightarrow C_{C1} = \frac{1}{2\pi f_{p1}(R_G + R_s)} = 3.3nF$$

$$f_{p3} = 10Hz = \frac{1}{2\pi C_{C2}(R_D + R_L)}$$

$$C_{C2} = \frac{1}{2\pi f_L(R_D + R_L)} = 0.53\mu F$$

$$I = mA$$

$$R_s = 100k\Omega, R_G = 4.7M\Omega$$

$$R_D = 15k\Omega, R_L = 15k\Omega$$

$$g_m = 1$$

$$C_{gs} = 1pF, C_{gd} = 0.4pF$$

$$f_L = 100Hz$$

$$f_{p1} = f_{p3} = \frac{100Hz}{10}$$